

Q9

→ when saturated the power dissipated by the transistor is given by

$$P_D = V_{CE(sat)} I_{DC}$$

→ Since $V_{CE(sat)}$ (as 0.3V) is closer to zero, the power dissipation is very low.

