

DC operation:

$$I_{BQ} = \frac{V_{CE} - V_{BE}}{R_b}$$

$$I_{BQ} = \frac{V_{CE} - 0.7}{R_b}$$

$$I_{CQ} = \beta I_{BQ} \Rightarrow \beta = \frac{I_{CQ}}{I_{BQ}}$$

$$\beta = I_{CQ} \left( \frac{R_b}{V_{CE} - 0.7} \right)$$

$$I_{CQ} = \beta \left( \frac{V_{CE} - 0.7}{R_b} \right)$$

$$V_{CEQ} = V_{CC} + I_{CQ} R_c$$

Hence Q is defined at point Q( $V_{CEQ}, I_{CQ}$ )

DC power input:

when AC input signal is applied, the base current varies sinusoidally.

$I_C$  current varies around its Quiescent point will the output voltage  $V_{CC}$  get varies. Varying current and output voltage delivers AC power to the load.