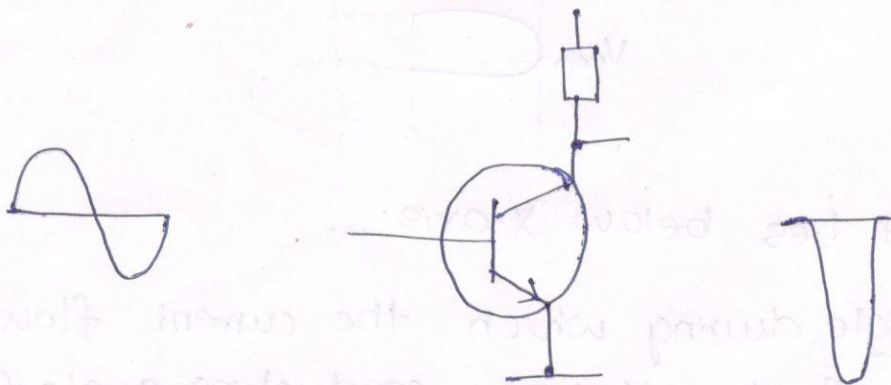


Class C Amplifiers:

32

- * Only half of the i/p signal is given. i.e. class C amplifiers conduct less than 50% of i/p signal.
- * Distortion at o/p is high
- * It has higher efficiencies i.e. 100% when compared to Class A and Class B.
- * Applications:
 - RF transmitters.
 - Mega phones.
- * I/p signal is used to roughly switch the amplifying device on and off, which causes pulses of current to flow through a tuned circuit.



Definition:

A amplifier is said to be class C; if the Q point and i/p signal selected such that o/p signal is obtained for less than half cycle, for a full i/p cycle.