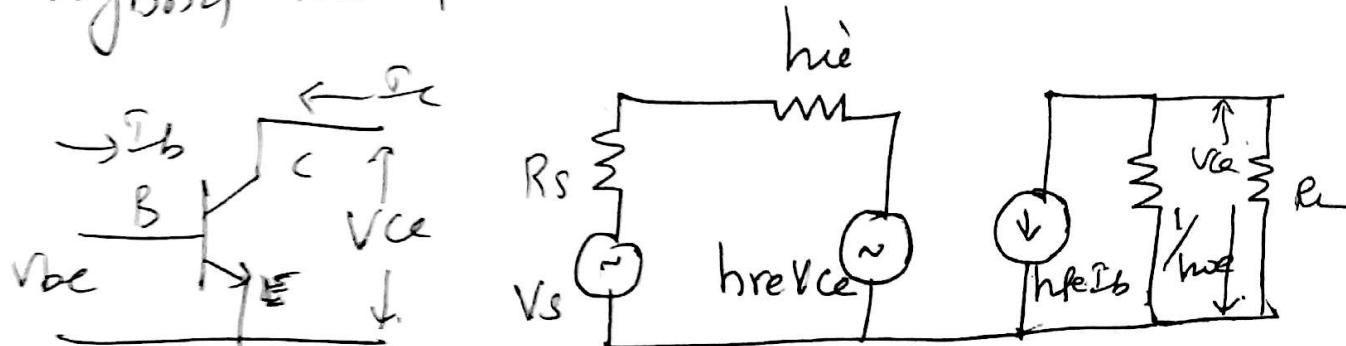


UNIT-II

(1)

Small signal equivalent of CE amplifier
on Hybrid model



Hybrid parameter (or) h-parameter

- * The dimensions of the hybrid parameters are not alike, they are hybrid in nature so - they are called hybrid parameters.
- * Transistor is a two port network

$$\begin{array}{ccc} \rightarrow i_i & & \leftarrow s_o \\ \boxed{\quad} & & \boxed{\quad} \\ v_i & & v_o \end{array} \quad \begin{aligned} v_i &= h_{11} i_i + h_{12} v_o \\ i_o &= h_{21} i_i + h_{22} v_o \end{aligned}$$

$$\Rightarrow h_{11} = \left[\frac{v_i}{i_i} \right]_{v_o=0} = h_{ie} \rightarrow \text{Input impedance}$$

$$h_{12} = \left[\frac{v_i}{v_o} \right]_{i_i=0} = h_{re} \rightarrow \text{Reverse voltage gain}$$

$$h_{21} = \left[\frac{i_o}{i_i} \right]_{v_o=0} = h_{fe} \rightarrow \text{Forward current gain}$$

$$h_{22} = \left[\frac{i_o}{v_o} \right]_{i_i=0} = h_{oe} \rightarrow \text{Output admittance}$$



Salient features of h-parameters are.

1. h-parameters are real numbers
2. Easy to measure
3. Convenient to use in circuit analysis & design
4. easily convertible from configuration to other

Small signal analysis of CE Configuration


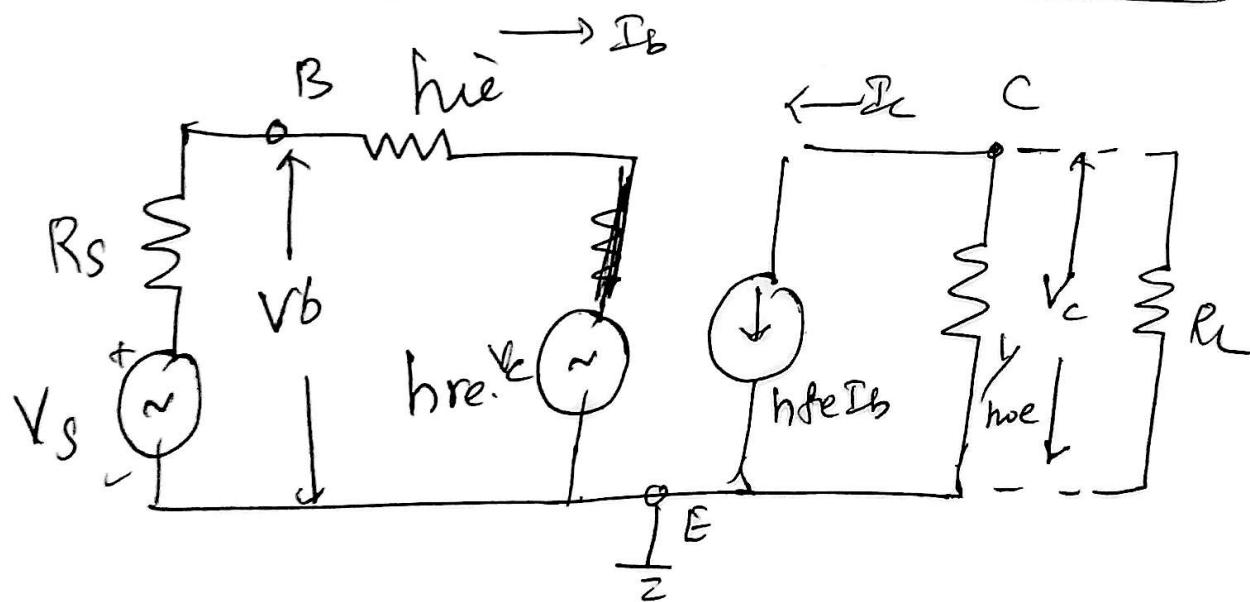


Fig (1) - h-parameters equivalent circuit for
CE Amplifier

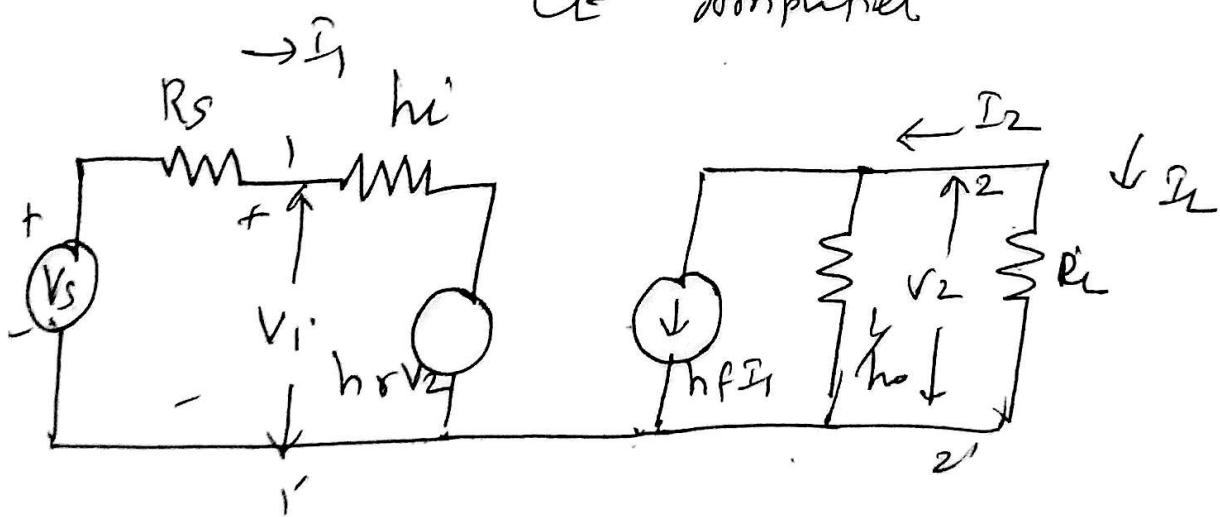

(2)

Current Gain (A_i)

$$A_i = \frac{I_L}{I_1} = -\frac{I_2}{I_1} \quad [\because I_L = -I_2]$$

$$I_2 = h_f I_1 + h_o V_2$$

$$\text{Sub } V_2 = -I_2 R_L$$

$$I_2 = h_f I_1 - h_o I_2 R_L$$

$$I_2 + h_o I_2 R_L = h_f I_1$$

$$I_2 (1 + h_o R_L) = h_f I_1$$

$$\frac{I_2}{I_1} = \frac{h_f}{1 + h_o R_L}$$

$$A_i = -\frac{I_2}{I_1} = \frac{-h_f}{1 + h_o R_L}$$

$$A_i = \frac{-h_f}{1 + h_o R_L}$$

For CE Amp

$$A_i = \frac{-h_{fe}}{1 + h_{oe} R_L}$$

Input Impedance (Z_i)

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$V_1 = h_i I_1 + h_{r1} V_2$$

$$Z_i = \frac{V_1}{I_1} = h_i + h_{r1} \frac{V_2}{I_1}$$

$$\text{Sub } V_2 = -\frac{I_2}{R_L} R_L = A_i I_1 R_L$$

$$Z_i = h_i + h_{r1} \frac{A_i I_1 R_L}{I_1}$$

$$\left[A_i = \frac{I_2}{I_1} \right]$$

$$Z_i = h_i + h_{r1} A_i R_L$$

$$\text{Sub } A_i = \frac{-h_f}{1 + h_o R_L}$$

$$Z_i = h_i - \frac{h_{r1} h_f R_L}{1 + h_o R_L}$$

÷ Nr & Dr by R_L

$$Z_i = h_i - \frac{h_{r1} h_f}{h_o + 1/R_L}$$

$$Z_i = h_i - \frac{h_{r1} h_f}{h_o + Y_L} \quad \text{where } Y_L = 1/R_L$$

(3)

Voltage Gain (Av)

$$Av_e = \frac{V_2}{V_1}$$

$$\text{WKT: } V_2 = -I_2 R_L = A_i I_1 R_L$$

$$Av_e : \frac{A_i I_1 R_L}{V_1} = \frac{A_i R_L}{Z_1}$$

Voltage Gain with Source:

$$Av_{es} = \frac{V_2}{V_s} = \frac{V_2}{V_1} \cdot \frac{V_1}{V_s}$$

$$\therefore Av_{es} = Av_e \cdot \frac{V_1}{V_s}$$

Power Gain: (Ap)

$$Ap = P_2 / P_1 = \frac{V_2 I_2}{V_1 I_1} = Av_e \cdot A_i = A_i^2 \frac{R_L}{Z_1}$$

$$\therefore Av_e = \frac{A_i R_L}{Z_1}$$

$$Ap = \frac{A_i^2 R_L}{Z_1}$$

Output Admittance (y_o).

$$y_o = \frac{1}{h_o} = \frac{I_2}{V_2} \text{ with } V_S = 0$$

$$I_2 = -h_f I_P + h_o V_2.$$

\therefore above eqn by V_2 .

$$\frac{I_2}{V_2} = h_f \frac{I_P}{V_2} + h_o$$

$V_S = 0$, we can write...

$$R_S I_1 + h_i I_1 + h_r V_2 = 0.$$

$$\therefore (R_S + h_i) I_1 = -h_r V_2$$

$$\frac{I_1}{V_2} = \frac{-h_r}{R_S + h_i}$$

$$y_o = \frac{-h_f h_r}{R_S + h_i} + h_o$$

$$y_o = h_o - \frac{h_f h_r}{R_S + h_i}$$

(4)

Power Gain (Ap)

$$A_p = \frac{P_2}{P_1} = -\frac{V_2 I_2}{V_1 I_1} = A_{le} \cdot A_i$$

$$[P_2 = V_2 I_L = -V_2 I_2]$$

$$A_p = A_i^2 \frac{R_L}{Z_i} \quad [\because A_{le} = \frac{A_i R_L}{Z_i}]$$

Summary:

$$A_i = \frac{-h_f}{j + h_{fe}}$$

$$A_{is} = \frac{A_f R_s}{Z_i + R_s}$$

$$Z_i = h_i + h_r A_i R_L = h_i - \frac{h_f h_r}{h_o + h_L}$$


$$A_{le} = \frac{A_i R_L}{R Z_i}$$

$$A_{les} = \frac{A_{is} R_L}{R_s}$$

$$Y_o = h_o - \frac{h_f h_r}{h_i + R_s}$$

$$A_p = A_i^2 \cdot \frac{R_L}{Z_i}$$

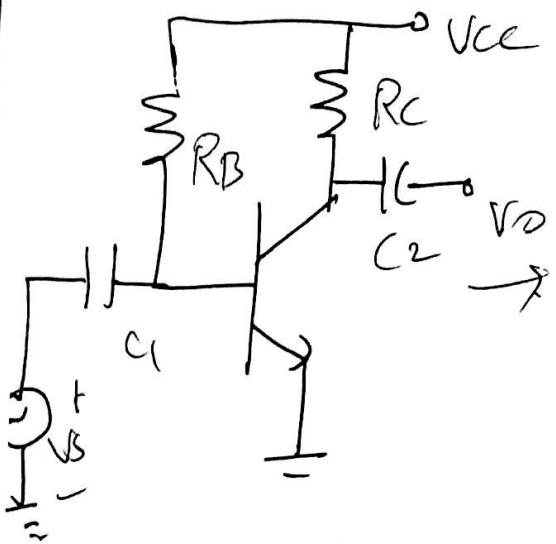Transistor Amplifiers Analysis Wrong re-model



re-model is also sensitive to the dc operating point of the amplifiers circuit.
re model is used for low frequency analysis

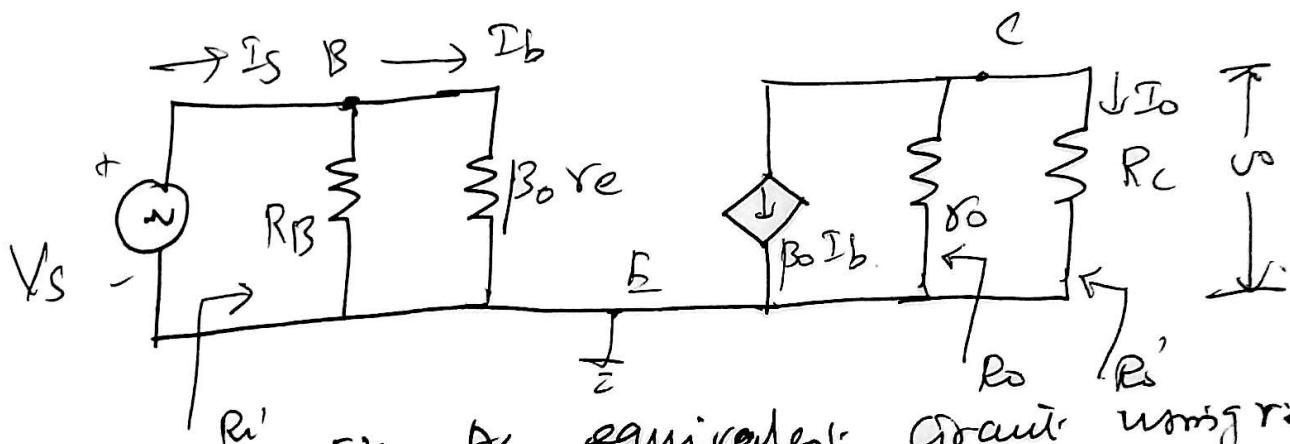


Fig: AC equivalent circuit using re-model

DC Analysis

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_E = (\beta + 1) I_B$$

$$r_e = \frac{26 \text{ mV}}{I_E}$$

R_{in} resistance

$$R_i = \beta r_e$$

$$R_i' = R_i \parallel R_B$$

o/p resistance.






$$R_o = r_o$$

$$R_o' = R_C \parallel r_o$$

(5)

The r_e Transistor Model:

C.G Configuration

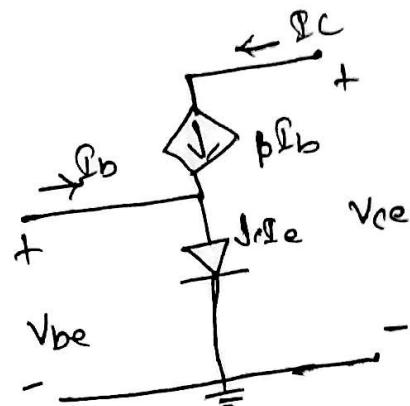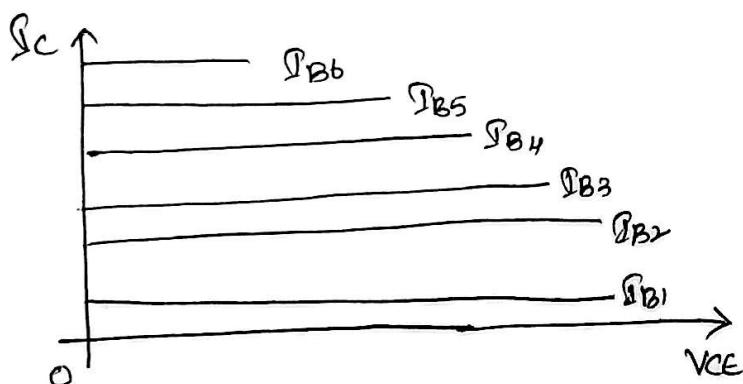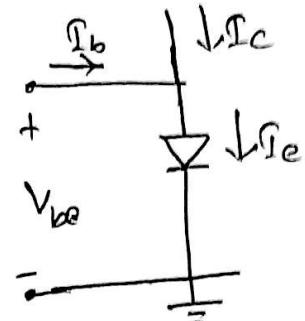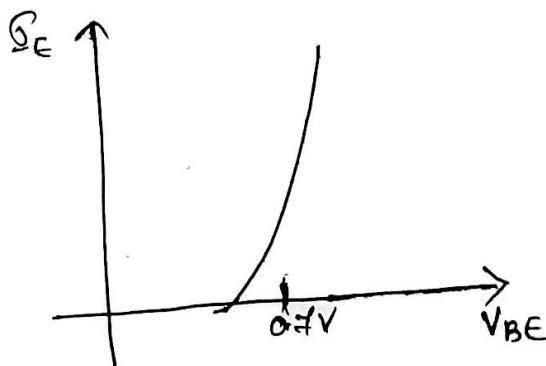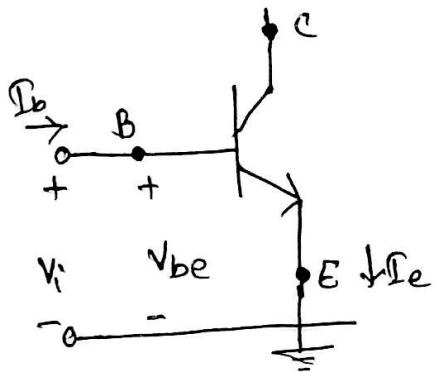


$$Z_i = \frac{V_i}{I_b} = \frac{V_{be}}{I_b}$$



$$\begin{aligned} V_{be} &= I_{ere} = (I_c + I_b)r_e = (\beta I_b + I_b)r_e \\ &= (\beta + 1)I_b r_e \end{aligned}$$


$$r_e = \frac{26mV}{I_c}$$
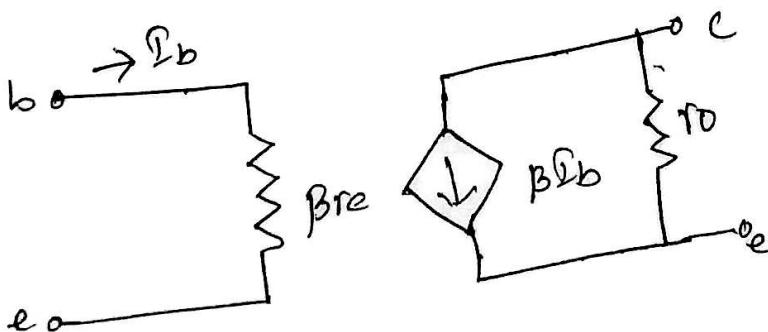
$$Z_i = \frac{V_{be}}{I_b} = \frac{(\beta + 1)I_b r_e}{I_b} = (\beta + 1)r_e \approx \beta r_e$$



Common Base Configuration:

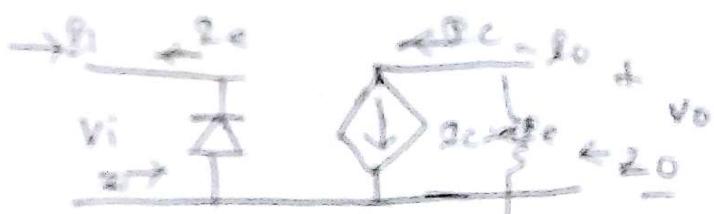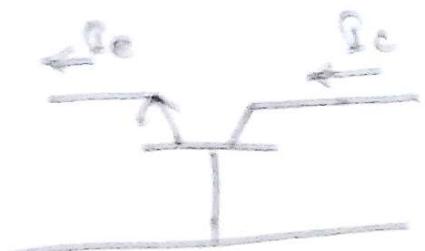

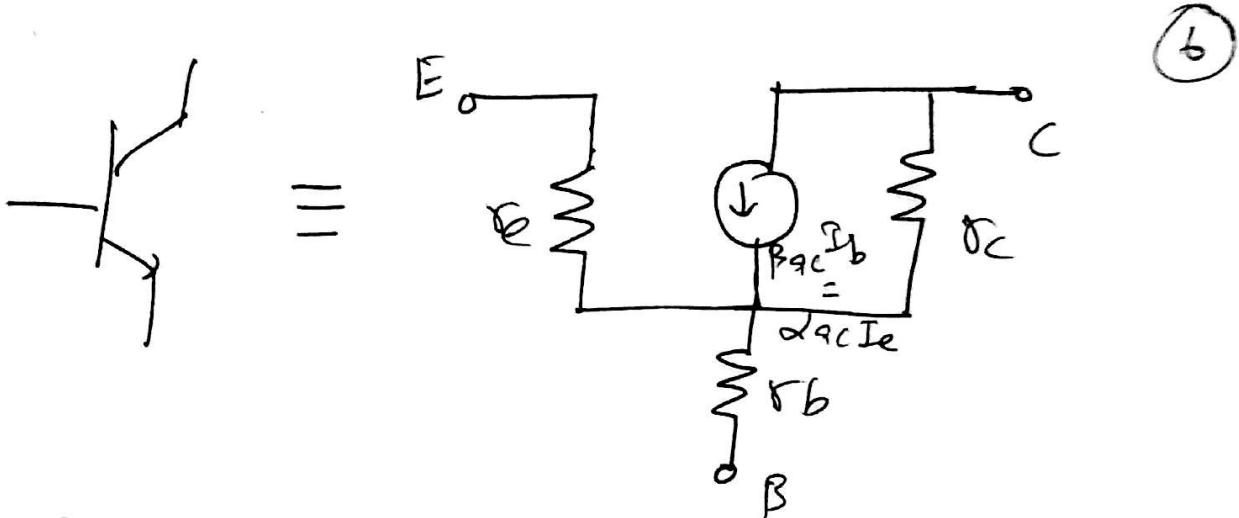

R-parameter	Description
α_{ac}	ac alpha (I_c/I_e)
β_{ac}	ac beta (I_c/I_b)
r_e	ac emitters resistance.
r_c	ac collector "
r_b	ac base "

Relationships of R-parameters & h-parameters

$$\alpha_{ac} = h_{fb}$$

$$\beta_{ac} = h_{fe}$$

$$r_e = \frac{h_{re}}{h_{oe}}$$

$$r_c = \frac{h_{rc} + 1}{h_{oe}}$$

$$r_b = h_{ie} - h_{re} (1 + h_{fe})$$

$$r_e = \frac{KT}{qIE}$$

$$K = 1.38 \times 10^{-23} \text{ J/K}$$


$$T = 273^\circ\text{C}$$

$$q = 1.602 \times 10^{-19} \text{ C}$$

$$r_e = 26 \text{ m}\Omega$$

The r_e model is sufficiently accurate and only requires one parameter h_{fe} . δ_{lp} impedance is derived from just one parameter h_{fe} . However, the π model does not have parameters for output admittance (ω versus voltage ratio). It is only suitable at dc & mid frequencies.

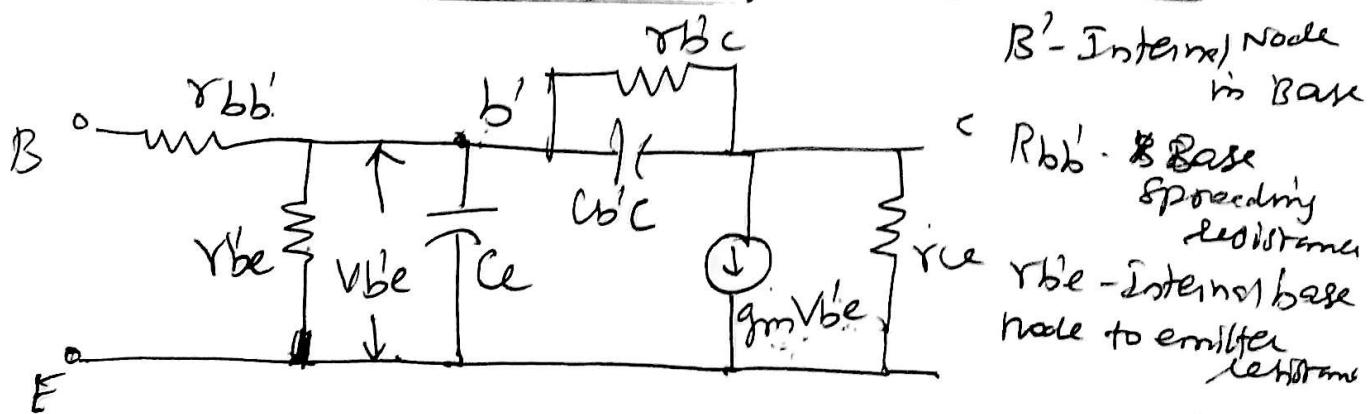Common Emitter Short Circuit Current Gain of Transistor at high frequency using hybrid- π model



The hybrid- π model with resistive load
hybrid- π model is used to analyze the BJT
in high frequency range.

r_{ce} = Collector to emitter resistance

C_{be} = diffusion capacitance of emitter base J_b

$r_{bb'}$ = feedback resistance from internal
base node to collector node

g_m = transconductance


The main advantage of hybrid-II model is that it can be simplified to obtain low frequency model of BJT. This is done by eliminating capacitance. So that BJT responds without any significant delay to the input signal.

Elements of hybrid-II - model.

$C_{be} \approx C_{bc}$: Forward biased pN junction exhibits a capacitive effect called the diffusion capacitance. This is represented as $C_{be} \approx C_e$.

W^hile the reverse bias pN junction exhibits capacitive effect called the transition capacitance. It is represented by $C_{bc} \approx C_c$.

$r_{bb'}$:

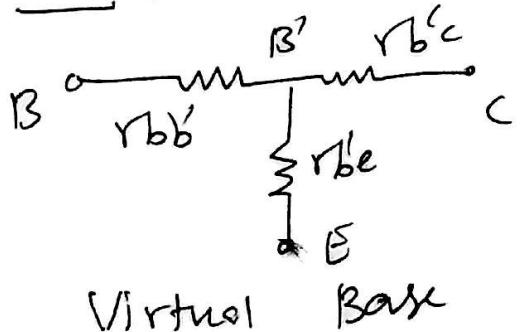

The internal node b' is physically not accessible; bulk node b represents external base terminal. base spreading resistance

$r_{bb'}$ is called as

$r_{b'c}$: Due to early effect, the voltage across the collector to emitter junction results in base-width modulation. A change in the effective base width causes the emitter current to change. This feedback effect

between O/p to Z/p is represented by $r_{b'c}$.
 $r_{b'e}$: This resistance is in series with the collector junction.


g_m : Due to small changes in voltage $V_{b'e}$ across the emitter junction, there is excess minority carrier concentration injected into the base which is proportional to $V_{b'e}$.

Hybrid Σ Parameters value.

Parameter	meaning	value.
g_m	Mutual conductance	50 mA/V
r_{bb}	Base spreading resistance	10 k Ω
r_{ce}	O/p resistance	80 k Ω
$r_{b'e}$	Resistance between b' & e	1 k Ω
$r_{b'c}$	Reverse biased p-n junction between base & collector	4 M Ω
C_e	junction capacitance	100 pF
C_c	junction capacitance	3 pF


Gains using hybrid- π -model.

(8)

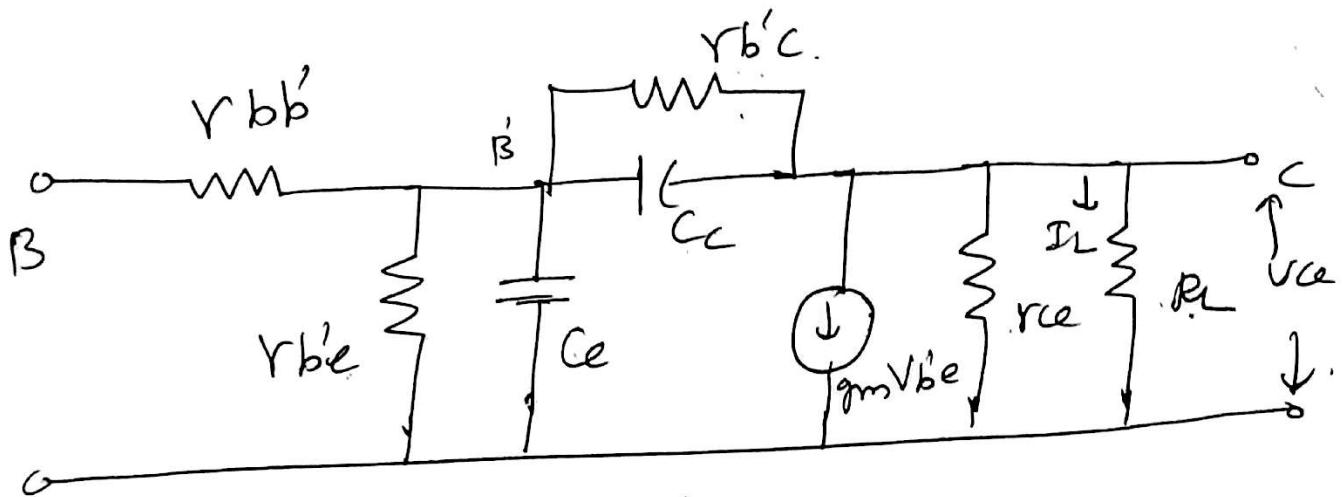

E Let us assume $R_L = 0$
 If $R_L = 0$, op short circuited V_{CE} becomes zero, $C_e \gg C_{b'c}$ becomes parallel. If $\frac{C_{b'c}}{C_e}$ known appears between base & emitters, it is Miller capacitance. (C_M)
 as Miller capacitance. (C_M)

$$jw C_M = C_{b'c} (1 + g_m R_L)$$

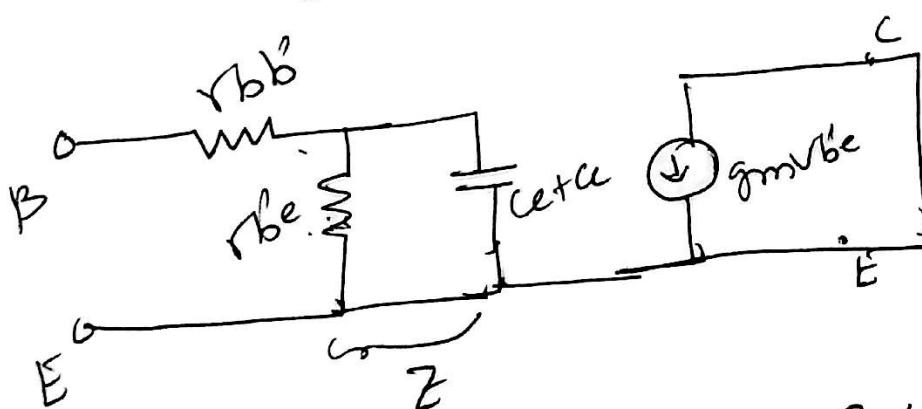

Fig(2)
 Simplified hybrid- π model for short circuit


Here $R_L = 0$; $C_M = C_{b'c}$.

As $r_{bc}' \gg r_{be}'$, r_{be}' is neglected.
 With these approximation, we get simplified hybrid- π -model for short circuit CB transistor as shown in Fig

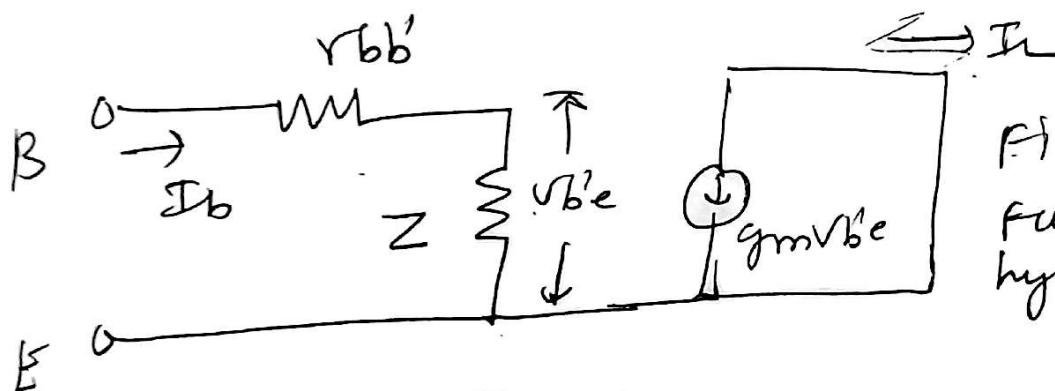1) 1st combination of $r_{b'e} \propto (C_e + C_C)$ is given as

$$Z = r_{b'e} + \frac{1}{j\omega(C_e + C_C)}$$

$$Z = \frac{r_{b'e}}{1 + j\omega r_{b'e}(C_e + C_C)}$$



Fig(3)
further simplified
hybrid- π -model

$$V_{b'e} = I_b \cdot Z$$

$$\Rightarrow Z = \frac{V_{b'e}}{I_b}$$

Current gain $A_i = \frac{I_c}{I_b} = -\frac{g_m V_{b'e}}{I_b}$ [since $I_c = -g_m V_{b'e}$]

$$A_i = -g_m \cdot Z$$


$$A_i = -g_m \cdot \frac{r_{b'e}}{1 + j\omega r_{b'e}(C_e + C_C)}$$

Already we know $g_m V_{b'e} = V_{be}$ here

$$A_i = \frac{-h_{fe}}{1 + j\omega r_b b' e(C_e + C_c)}$$

(9)

Current Gain

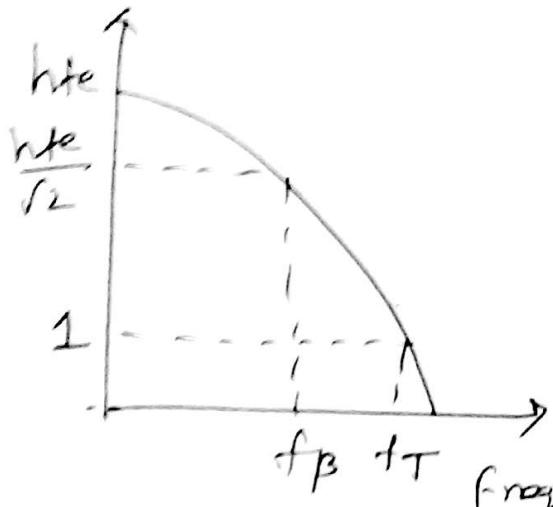

Current is not constant in the above equation. It depends on frequency. When frequency is small, the term containing f is very small compared to 1 so hence at low frequency $A_i = -h_{fe}$. But as frequency increases

A_i reduces as shown in Fig.

Let us take

$$f_B = \frac{1}{2\pi r_b b' e(C_e + C_c)}$$

$$A_i = \frac{-h_{fe}}{1 + j\frac{f}{f_B}}$$

$$|A_i| = \frac{h_{fe}}{\sqrt{1 + \left(\frac{f}{f_B}\right)^2}}$$

$$\text{As } f = f_B$$

$$A_i = \frac{h_{fe}}{\sqrt{2}}$$

f_{β} (cut off frequency)

It is the frequency at which the transistor's short circuit CE current gain drops by 3 dB or $\frac{1}{\sqrt{2}}$ times from its value at low frequency.

$$f_{\beta} = \frac{1}{2\pi r_b'e (c_e + c_o)} = \frac{g_b'e}{2\pi (c_e + c_o)}$$

$$f_{\beta} = \frac{1}{h_{fe}} \cdot \frac{g_m}{2\pi (c_e + c_o)}$$

$$\left[g_b'e = \frac{1}{r_b'e} = \frac{g_m}{h_{fe}} \right]$$

f_{α} (Cut-off frequency)

It is the frequency at which the transistor's short circuit CB current gain drops by 3 dB or $\frac{1}{\sqrt{2}}$ times from its value at low frequency.

$$A_i = \frac{-h_{fb}}{1 + j(f/f_2)}$$

$$\text{where } f_2 = \frac{1}{2\pi r_b'e (1/h_{fe}) \cdot c_e} = \frac{1 + h_{fe}}{2\pi r_b'e c_e}$$

$$\approx \frac{h_{fe}}{2\pi r_b'e c_e}$$

$$|A_i| = \frac{h_{fb}}{\sqrt{1 + (f/f_2)^2}} \quad \text{when } f = f_2$$

$$A_i = \frac{h_{fb}}{\sqrt{2}}$$

The parameter f_T :

It is the frequency at which short circuit CE current gain becomes unity

(10)

$$\text{at } f = f_T$$

$$1 \neq \frac{h_{fe}}{f_T f_B}$$

$$1 = \frac{h_{fe}}{\sqrt{1 + (f_T/f_B)^2}}$$

$$f_T/f_B \gg 1, \text{ then}$$

$$1 = \frac{h_{fe}}{f_T/f_B}$$

$$\Rightarrow f_T = f_B \cdot h_{fe}$$

$$f_T = \frac{h_{fe} \cdot g_m}{h_{fe} \cdot 2\pi(C_e + C_c)}$$

$$f_T = \frac{g_m}{2\pi(C_e + C_c)}$$


$$\therefore f_B = \frac{1}{h_{fe}} \cdot \frac{g_m}{2\pi(C_e + C_c)}$$

$$\text{for } C_e \gg C_c$$

$$f_T = \frac{g_m}{2\pi C_e}$$

(11)

Current Gain with Resistive load

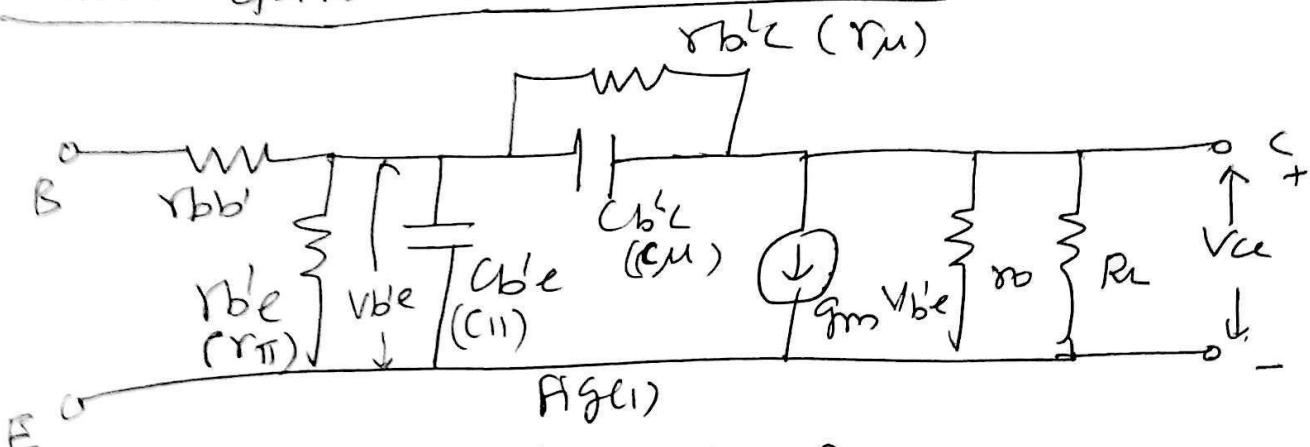


Fig(1)

\$r_o\$ is in parallel with \$R_L\$

for high frequencies \$R_L\$ is high, neglect \$r_o\$.

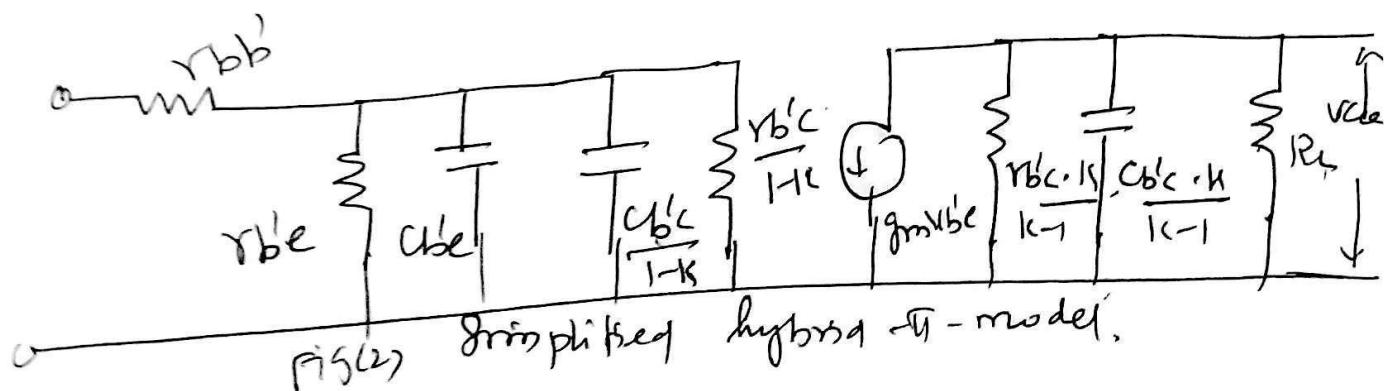Using Miller theorem, we can split \$r_{bc'L} \approx r_{bc'C}\$



Further simplification of Input Circuit

$$K = \frac{r_o}{V_{BE}} \quad \text{where} \quad r_o = -g_m V_{BE} R_L$$

$$K = -\frac{g_m V_{BE} R_L}{V_{BE}} = -g_m R_L$$

$$\text{Assume } R_L = 2K \times g_m = 50 \text{ mA/V}$$

$$\text{we get } K = -100$$

$$\frac{r_{b'c}}{1-k} = \frac{4Mr}{1 - (-100)} = 40k$$

$\frac{r_{b'c}}{1-k} \gg r_{b'e}$ so hence $\frac{r_{b'c}}{1-k}$ which is parallel with $r_{b'e}$ can be neglected.


$C_{b'c}$ also resolved by Miller theorem


$$\frac{C_{b'c}}{1-k} = \frac{1}{j\omega C_{b'c}} : \frac{1}{j\omega C_{b'c}(1+gmR_L)}$$

$$\therefore \frac{C_{b'c}}{1-k} = C = C_{b'c}(1+gmR_L)$$

as $C_{b'e}$ & C are in parallel, the total equivalent capacitance is given as

$$C_{eq} = C_{b'e} + C_{b'c}(1+gmR_L)$$

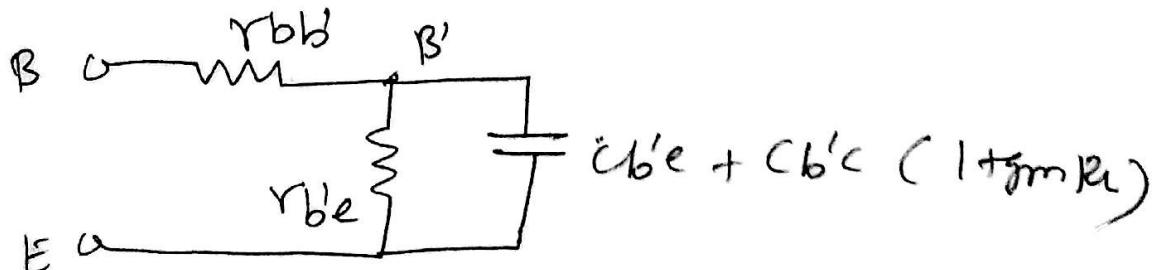

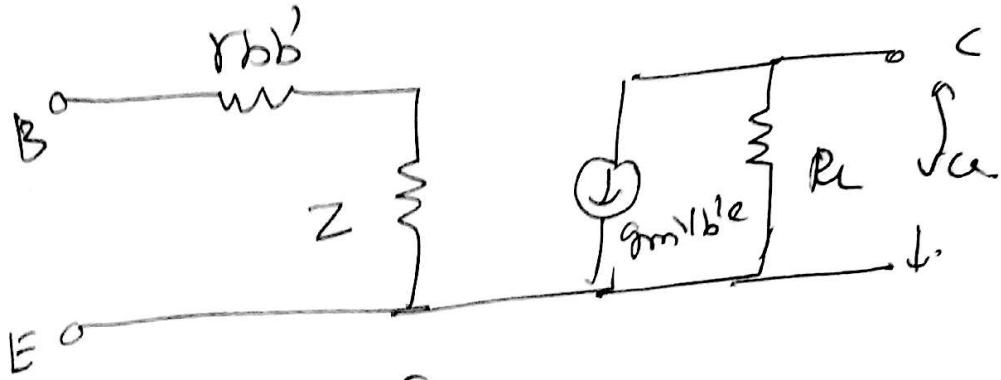

$$V_{b'e} = I_b Z$$

$$\therefore Z = V_{b'e} / I_b$$

Current gain $A_i = \frac{I_L}{I_b} = -\frac{g_m V_{b'e}}{I_b}$

$$A_i = -g_m \cdot Z$$

$$A_i = \frac{-g_m \cdot r_{b'e}}{1 + j 2\pi f r_{b'e} C_{eq}} = \frac{-h_{fe}}{1 + j 2\pi f r_{b'e} C_{eq}}$$

Set $f_H = \frac{1}{2\pi \cdot r_{b'e} C_{eq}}$

$$A_i = \frac{-h_{fe}}{1 + j(f/f_H)}$$

$$|A_i| = \frac{h_{fe}}{\sqrt{1 + (f/f_H)^2}}$$

at $f = f_H$

Further Simplification for Output Circuit

O/p capacitance $C_{b'c}$ can be calculated as


$$\frac{C_{b'c} \cdot k}{k-1}$$

$$\frac{\frac{1}{j\omega C_{b'c}}}{\frac{k-1}{R}} \approx \frac{1}{j\omega C_{b'c}} \quad [\because R = -100]$$

$$\therefore \frac{C_{b'c} \cdot k}{k-1} = C_{b'c}$$

||| by $\frac{C_{b'c} \cdot k}{k-1} = r_{b'c} \approx 1 \text{ M}\Omega$

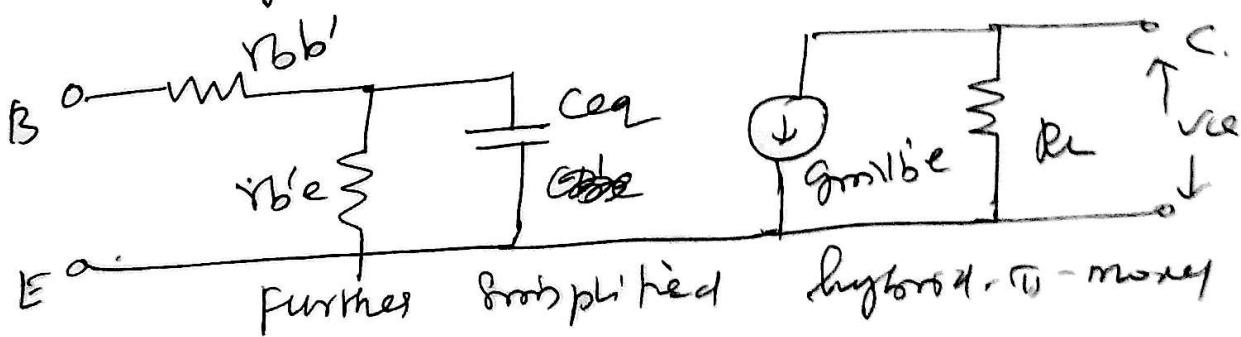$r_{b'c}$ is very high to compare with load resistance which is parallel with ~~es~~ or r_{be} . Hence r_{be} can be neglected.



|||^{el} combination of $r_{b'c}$ so C_{eq} is given as

$$Z = \frac{r_{b'c} \times \frac{1}{j\omega C_{eq}}}{r_{b'c} \times \frac{1}{j\omega C_{eq}}} = \frac{r_{b'c}}{1 + j\omega r_{b'c} \cdot C_{eq}}$$


(13)

$$A_{11} = \frac{hfe}{\sqrt{2}}$$

$$f_H = \frac{1}{2\pi r b' e [C_b' e + C_b' c (1 + g_m R_L)]}$$

At $R_L = 0$
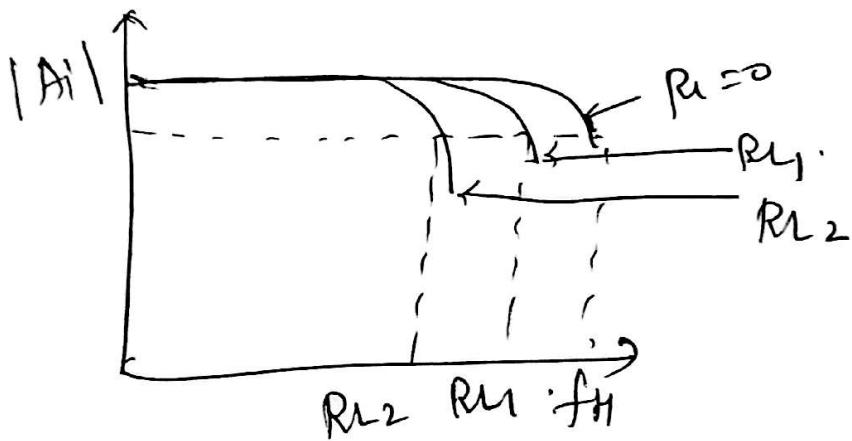
$$f_H = \frac{1}{2\pi r b' e [C_b' e + C_b' c]} \approx f_\beta.$$



(14)

Short circuit CE current gain of transistor is 25 at a frequency of 2MHz if $f_{\beta} = 200\text{MHz}$. calculate i) f_T ii) h_{fe} iii) Find $|A_i|$ at 10 MHz and 100 MHz.

Solution: i) $f_T = |A_i| \times f = 25 \times 2 \times 10^6$
 $= \underline{\underline{50\text{MHz}}}.$

ii) $h_{fe} = f_T / f_{\beta} = \frac{50\text{MHz}}{200\text{MHz}} = \underline{\underline{250}}$.

iii) $|A_i| = \frac{h_{fe}}{\sqrt{1 + (\frac{f}{f_{\beta}})^2}}$

at $f = \underline{\underline{10\text{MHz}}}$

$$|A_i| = \frac{250}{\sqrt{1 + \sqrt{\frac{(10 \times 10^6)^2}{(200 \times 10^6)^2}}}} = \underline{\underline{5}}$$


at $f = \underline{\underline{100\text{MHz}}}$

$$|A_i| = \frac{250}{\sqrt{1 + \left(\frac{100 \times 10^6}{200 \times 10^6}\right)^2}} = \underline{\underline{0.5}}$$



Determine the bandwidth of the amplifier shown in fig. $R_b = 100\Omega$; $r_{JT} = 1.1k$; $C_{JT} = 3\text{ pF}$

$$C_M = 100\text{ pF}; h_{ie} = 2.25$$

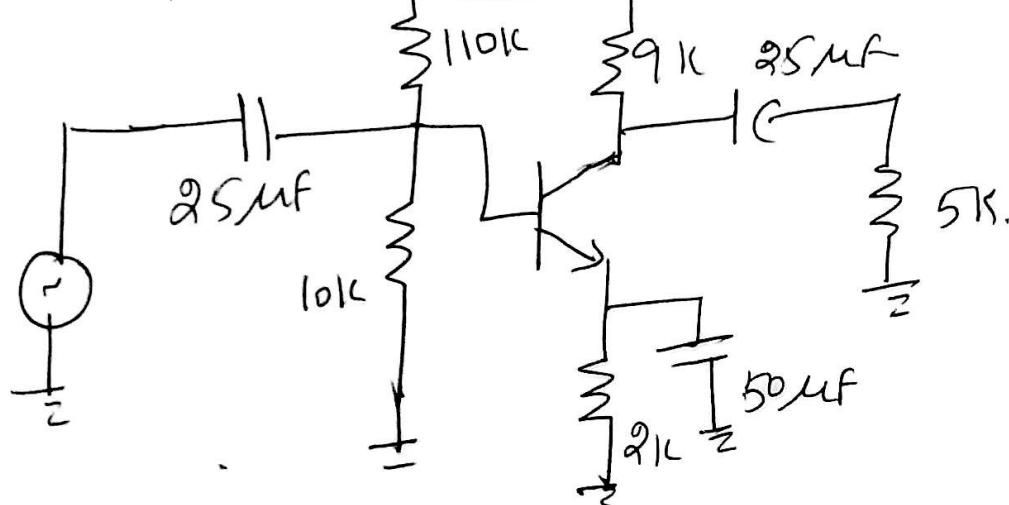

$$h_{ie} = R_b + r_{JT} = 100\Omega + 1.1k = 1.2k$$

$$f_{C \text{ input}} = \frac{1}{2\pi [R_b + (R_1 || R_2 || h_{ie})] C_1}$$

$$= \frac{1}{2\pi [0 + (110k || 10k || 1.2k)] \times 25 \times 10^{-6}}$$

$$= \underline{\underline{6 \text{ Hz}}}$$

$$f_C \text{ (output)} = \frac{1}{2\pi [R_C + R_L] C_2}$$

$$= \frac{1}{2\pi [9k + 5k] \times 25 \times 10^{-6}}$$

$$f_C =$$

$$= \underline{\underline{0.454 \text{ Hz}}}$$

(15)

$$f_C \text{ (by pass)} = \frac{1}{2\pi \left[\frac{R_m + h_{ie}}{13} \right] (R_{LE}) \cdot C_E}$$

$$R_{TH} = R_1 \parallel R_2 \parallel R_S = 110k \parallel 10k \parallel 0 = \underline{\underline{0}}$$

$$= \frac{1}{2\pi \left[\frac{1.2 \times \omega^3}{225} \right] / 2 \times 10^3} \times 50 \times \omega^{-6} = \underline{\underline{598 \text{ Hz}}}$$

$$f_H = \frac{1}{2\pi r_{IT} [C_T + C_M (1 + g_m R_L)]}$$

where


$$C_T = 3 \text{ pF}$$

$$C_M = 100 \text{ pF}$$

$$g_m = h_{fe} / r_{IT} = \frac{225}{1.4 \times \omega^3} = \underline{\underline{204.5 \text{ mA/V}}}$$

$$f_H = \frac{1}{2\pi \times 1.4 \times \omega^3 \left[3 \times \omega^{-12} + 100 \times \omega^{-12} (1 + 204.5 \times \omega^3 \times 5 \times \omega^3) \right]} \\ = 1.4131 \text{ kHz.}$$
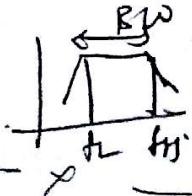
$$\text{Bandwidth} = f_H - f_L = 1.4131 \times \omega^3 - 0.453$$



$$\text{Answer} = \boxed{1.4131 \text{ kHz}}$$

If the rise time of a BJT is 35 nano second, what is the bandwidth that can be obtained using this BJT.

$$t_r = \frac{0.35}{B_W}$$

$$B_W = \frac{0.35}{t_r} = \frac{0.35}{35 \times 10^{-9}} = \underline{\underline{10 \text{ MHz}}}$$

If $I_C = 2 \text{ mA}$, and $V_{CE} = 10V$, a certain transistor data shows $\mu = C_\mu = 3 \text{ pf}$, $h_{FE} = 200$, & $\omega_T = -500 \text{ rad/sec}$. calculate g_m , r_{T1} , C_{T1} & W_B .

$$\textcircled{1} \quad g_m = \frac{I_C}{V_T} = \frac{2 \text{ mA}}{26 \text{ mV}} = \underline{\underline{76 \frac{\text{mA}}{\text{mV}} / \text{v}}}$$

$$\textcircled{2} \quad r_{T1} = \frac{h_{FE}}{g_m} = \frac{200}{76 \cdot 9 \times 10^{-3}} = \underline{\underline{2.6 \text{ k}\Omega}}$$

$$\textcircled{3} \quad (C_{T1} + C_\mu) = \frac{g_m}{2\pi f_T} = \frac{g_m}{\omega_T} = \frac{76 \cdot 9 \times 10^{-3}}{500 \cdot 10^6}$$

$$C_{T1} + C_\mu = -\cancel{C_\mu} 18.4 \text{ pF}$$

$$C_{T1} = 15.4 \text{ pF} \rightarrow 3 \text{ pF} \\ = 12.4 \text{ pF}$$

(16)


(iv) We know that

$$f_T = h_{fe} f_B$$



$$2\pi f_T = h_{fe} 2\pi f_B$$

$$\omega_T = h_{fe} \omega_B$$
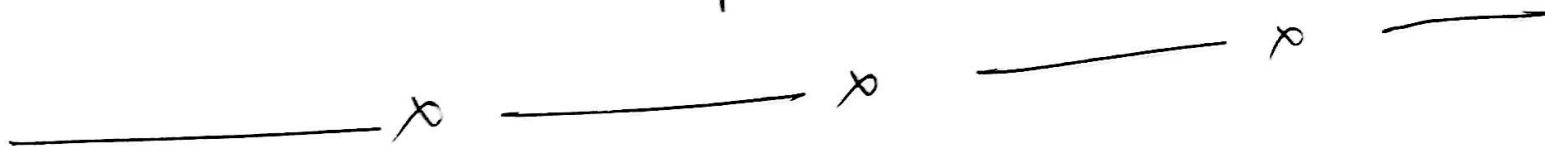
$$\omega_B = \frac{\omega_T}{h_{fe}} = \frac{500 \times 10^6}{200} = 2.5 \text{ M rad/sec}$$



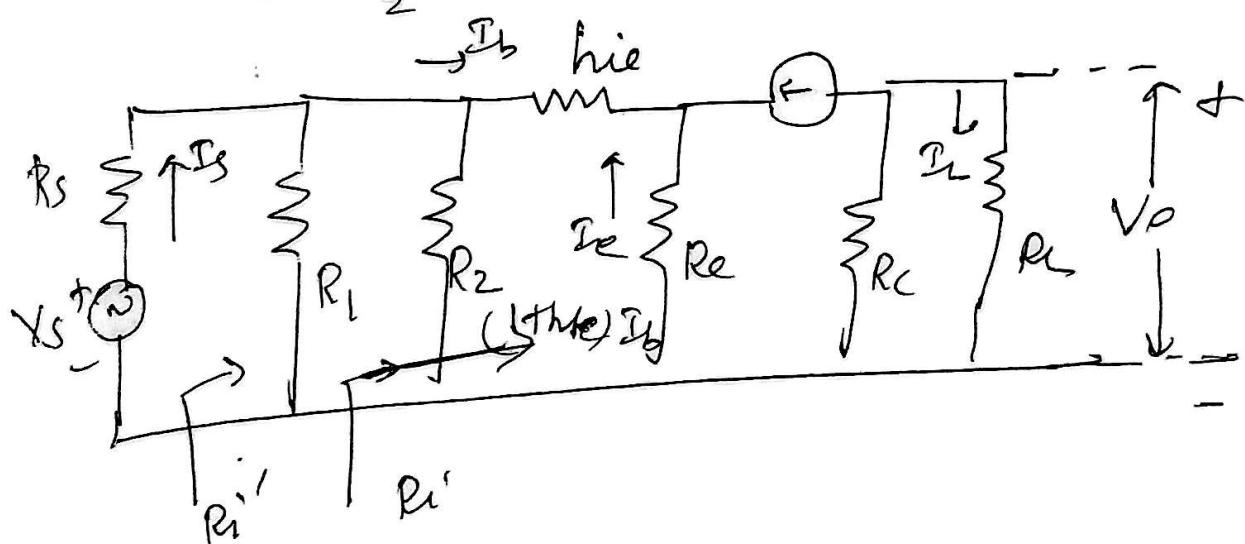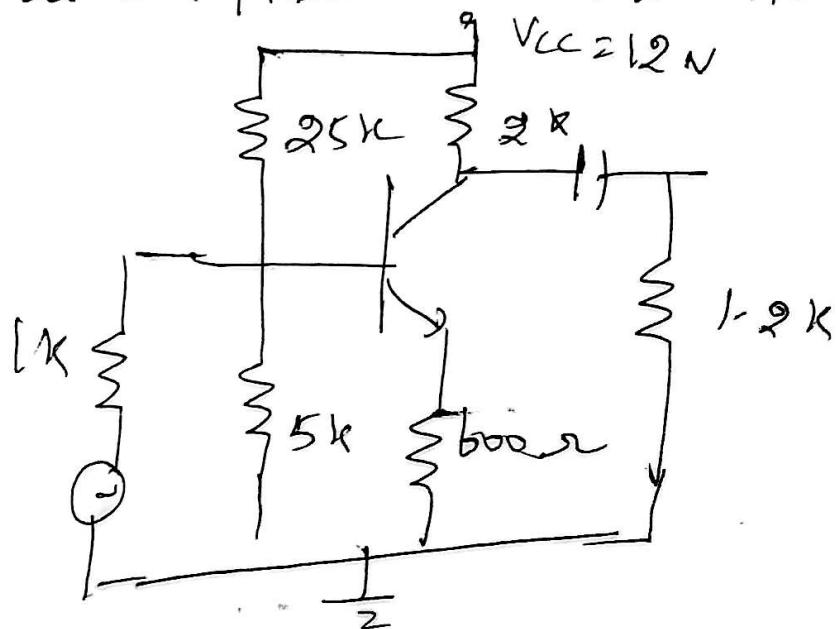Consider the single stage amp with the given values. The hybrid values of h-parameter are $h_{fe} = 100$, $h_{oe} = 25 \mu A/V$, $h_{re} = 2.5 \times 10^{-4}$ & $h_{ie} = 1.1 k\Omega$. Calculate A_v , A_i , R_i , R_{os} & R_{is}



$$\text{Current Gain } A_i = -\frac{I_c}{I_b} = -h_{fe} = -100$$

$$\begin{aligned} \text{Input resistance } R_{in} & , \frac{Vi}{I_b} = h_{ie} + (1+h_{fe}) R_E \\ & = 1.1k + (1+100) \cdot 600 = 61.7k \end{aligned}$$

$$\text{Overall Voltage Gain } A_V = \frac{A_{i1} R_L}{R_i'}$$

$$= \frac{-100 \times (1.2k \parallel 2k)}{61.7k}$$

$$= -1.21556$$

$$\text{Overall Input Resistance } (R_i') = R_i' \parallel R_1 \parallel R_2$$

$$= 61.7k \parallel 25k \parallel 5k$$

$$= 3.9k$$

$$\text{Overall Voltage Gains (A}_{VS\}) = \frac{A_{i1} R_i'}{R_i' + R_S}$$

$$= \frac{-1.21556 \times 3.9k}{3.9k + 1k}$$

$$= -0.967$$

$$\text{Overall Current Gains } A_{IS} = \frac{\overline{I_L}}{\overline{I_S}} = \frac{\overline{I_L}}{\overline{I_C}} \times \frac{\overline{I_C}}{\overline{I_B}} \times \frac{\overline{I_B}}{\overline{I_S}}$$

$$\frac{\overline{I_L}}{\overline{I_C}} = \frac{-R_C}{R_C + R_L} = \frac{-2k}{2k + 1.2k} = -0.625$$

$$\frac{\overline{I_B}}{\overline{I_S}} = \frac{R_S}{R_S + R_i'} = \frac{25k \parallel 5k}{(25k \parallel 5k) + 61.7k} = 0.063$$

$$A_{IS} = \frac{\overline{I_L}}{\overline{I_S}} = -0.625 \times 600 \times 0.063 \\ = -3.95$$