

218

Power dissipation:

η is equal to difference b/w output to dc power input

$$P_d = P_{dc} - P_{ac}$$

$$= \frac{2}{\pi} V_{cc} I_m - \frac{V_m I_m}{2}$$

$$= \frac{2}{\pi} V_{cc} - \frac{V_m}{R'_L} - \frac{V_m^2}{2R'_L} \quad \text{--- ①}$$

by differentiating w.r. to V_m

we get.

$$V_m = \frac{2}{\pi} V_{cc}$$

Put V_m in ①

$$P_{d(max)} = \frac{2}{\pi^2} \cdot \frac{V_{cc}^2}{R'_L}$$

for maximum efficiency $V_m = V_{cc}$

If $V_m = V_{cc}$, $P_{d(max)}$ cannot be observed simultaneously.

Power dissipated per transistor:

$$P_{ac} = V_m \times I_m / 2 = \frac{V_m^2}{2R'_L}$$

$$(P_{ac})_{max} = \frac{V_{cc}^2}{2R'_L}$$

$$\frac{P_d(max)}{P_{ac(max)}} = \frac{2(P_{ac(max)})}{\pi^2}$$

$$\text{Now } P_d(max) = \frac{2}{\pi^2} \cdot \frac{V_{cc}^2}{R'_L}$$

$$= \frac{4}{\pi^2} (P_{ac})_{max}$$