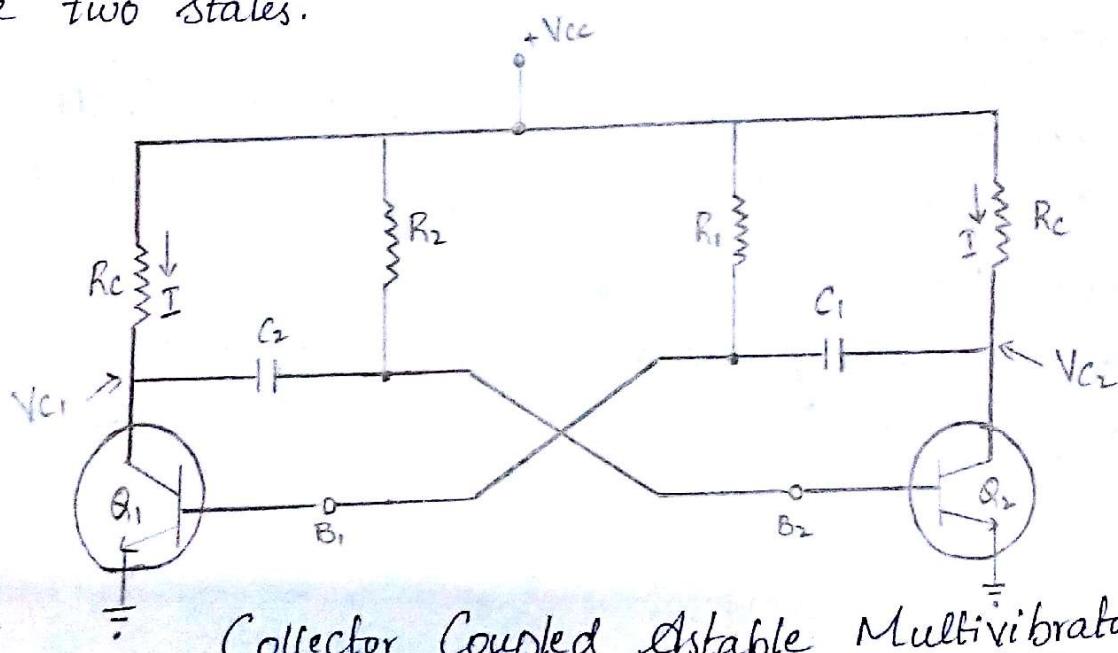


(1)

Astable Multi-vibrator

- * The astable multivibrator has two states, both are quasi-stable. None of the states is stable.
- * Without external trigger, multivibrator keeps on alternating the states.
- * It cannot remain indefinitely (i.e) stable in any of these two states.



Collector Coupled Astable Multivibrator.


Construction: The Q_1 and Q_2 are identical npn transistors.

- * The two collector resistances are equal to R_c .
- * The collector Q_1 is coupled to the base of Q_2 through capacitor C_2 while the collector of Q_2 is coupled to the base of Q_1 through capacitor C_1 .

- * The capacitive coupling is used between the two transistors due to which neither transistor (both the transistors) can remain permanently cut-off.
- * The circuit has two quasi-stable states and it makes periodic switching between these states, without any external trigger signal.


Working:

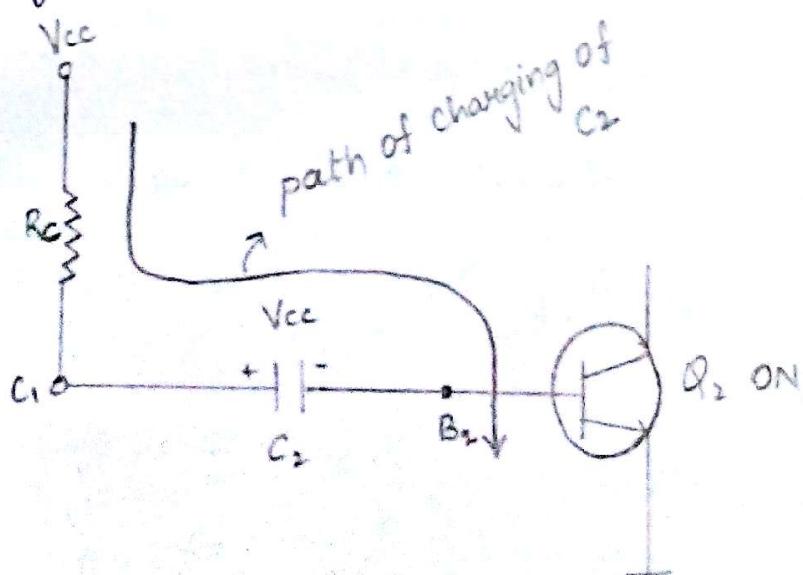- * Assume that the state is Q_2 ON and Q_1 OFF.
- * The capacitor C_2 starts charging towards V_{cc} through path R_C , C_2 and ON Q_2 .
- * Finally voltage across C_2 becomes equal to V_{cc} with proper polarity.




- * At the same time capacitor C_1 which is charged to V_{cc} in earlier state, starts discharging through path Q_1 , V_{cc} , R_1 , C_1 .

(2)

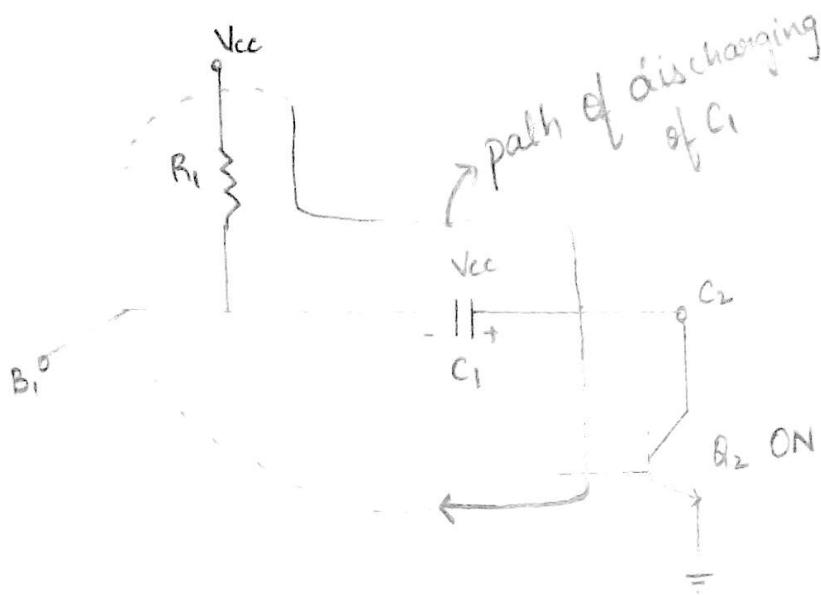


- * The base of Q_1 is at $-V_{CC}$ at the beginning.
- * As C_1 starts discharging, it becomes less and less negative (i.e) becomes more positive.
- * It becomes equal to V_T , the cut-in voltage of transistor Q_1 .
- * When it becomes greater than V_T , the transistor Q_1 starts conducting, so Q_1 becomes ON at the same time Q_2 becomes OFF
- * The negative potential applied at B_2 , due to charged C_2 ensures that Q_2 becomes indeed OFF
- * When this happens, the capacitor C_1 starts charging through R_C , C_1 and ON transistor Q_1

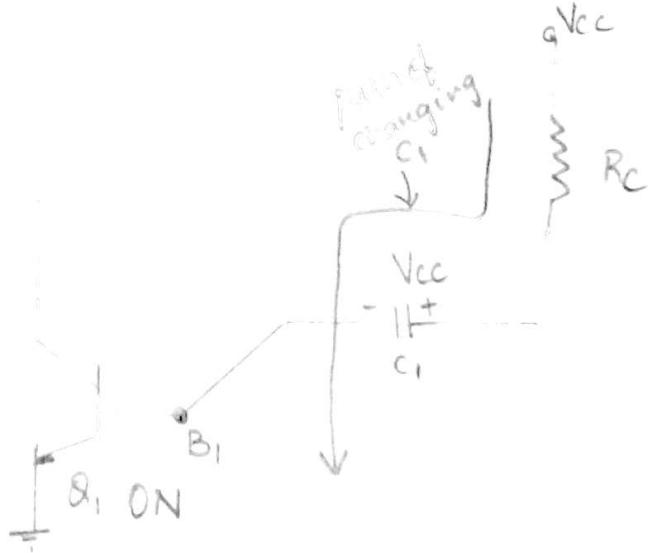

refers to
when Q_1
and voltage
with the
 V_{cc}
 Q_1

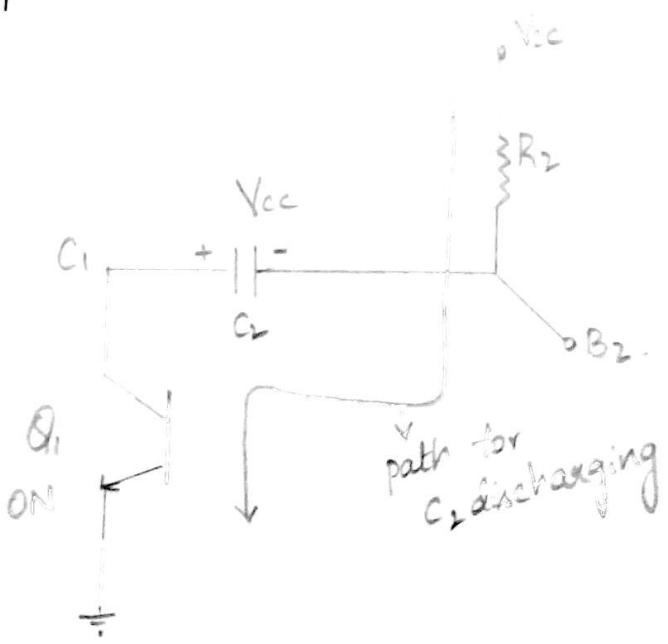- * C_2 starts discharging, through the path V_{cc} , R_2 , C_2 and ON transistor Q_1 .





- * As C_2 discharges, B_2 potential becomes less negative (i.e.) it increases towards positive.
- * When V_{B2} becomes just greater than cut-in voltage V_T of Q_2 , the Q_2 starts conducting.
- * Thus now Q_2 becomes ON and Q_1 OFF.
- * Thus changes in two states is automatic and without any external triggering signal.

Waveforms of Astable Multivibrator.

When Q_1 is OFF and Q_2 is ON, the C_1 discharges, and voltage at B_1 , i.e. V_{B1} increases. This increases exponentially with the time constant $R_1 C_1$. This voltage was initially at $-V_{cc}$. When this voltage increases beyond cut-in voltage of Q_1 , Q_1 starts conducting when Q_1 is in saturation
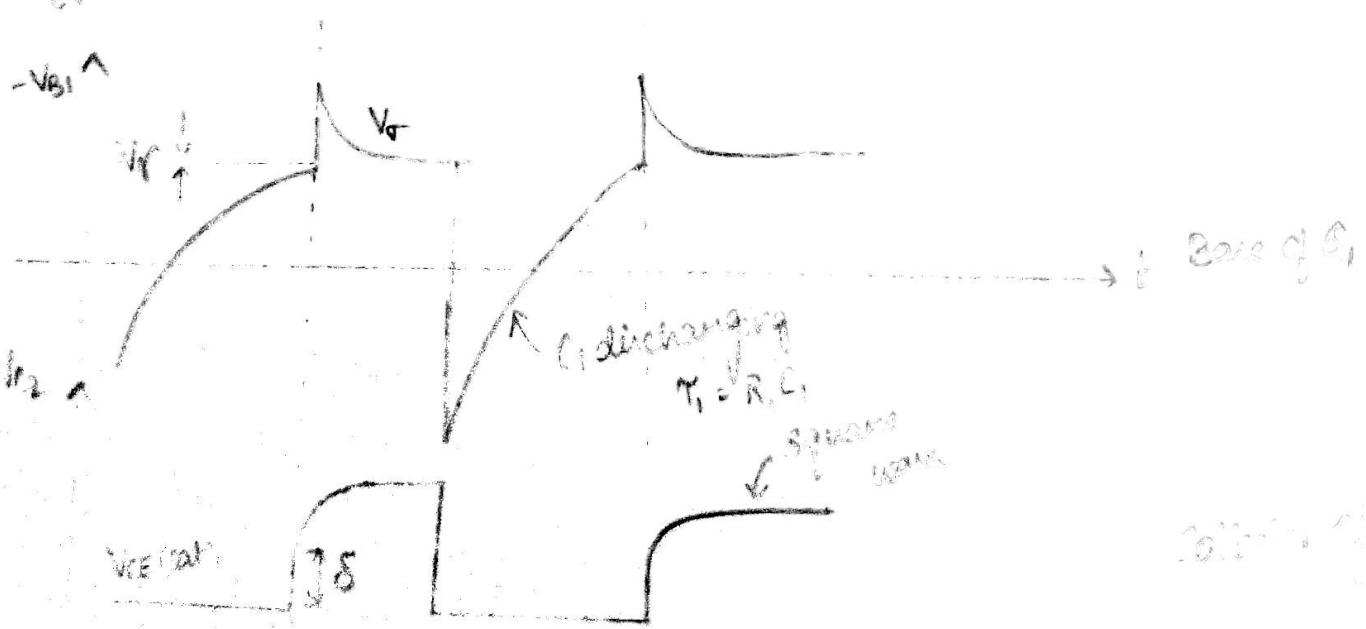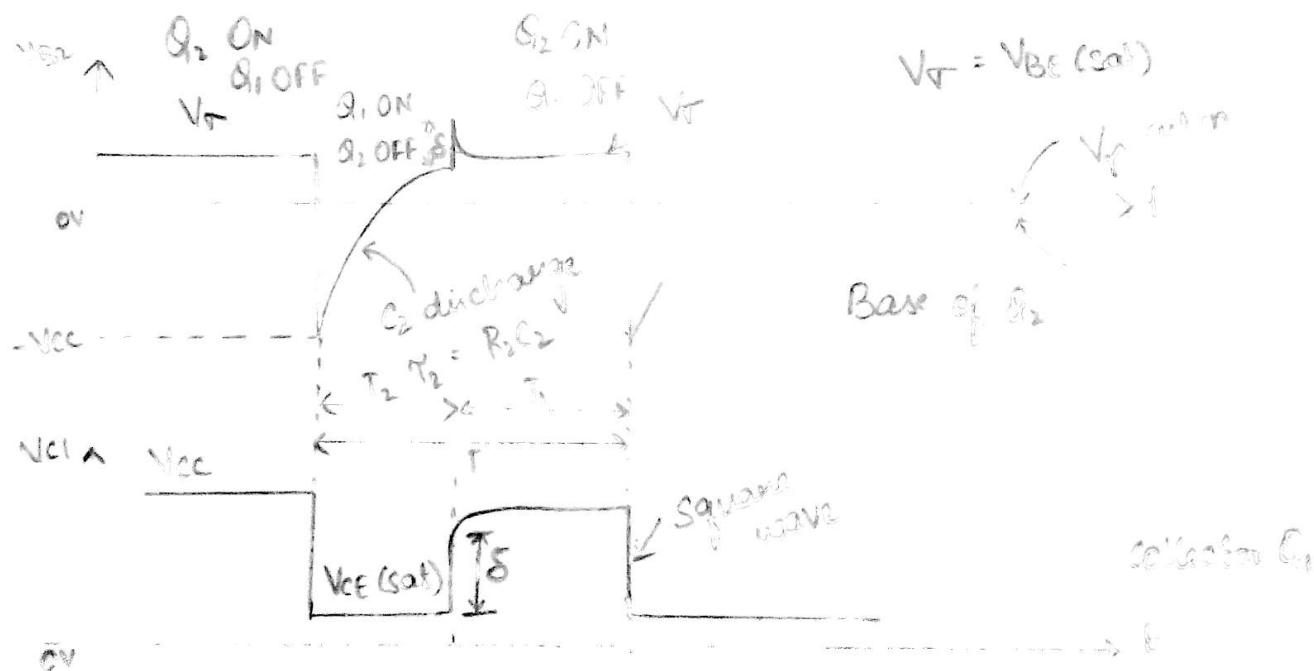
$$V_{B1} = V_{BE(\text{sat})} \quad V_{C_1} = V_{CE(\text{sat})} \quad V_{C_2} = V_{cc}$$



When Q_1 is ON and Q_2 is OFF, the C_2 discharges and the voltage at B_2 i.e. V_{B2} increases. This increases exponentially with time constant $R_2 C_2$. This voltage was initially at $-V_{CC}$ previous state. When this voltage increases beyond cut-in voltage of Q_2 , Q_2 conducts and goes in saturation.

$$V_{B2} = V_{BE(\text{sat})}, \quad V_{C2} = V_{CE(\text{sat})}$$


$$V_{C1} = V_{CC}$$

The analytical expression for δ is same as derived earlier for monostable multivibrator.

While the base current I_B at overshoot is given by

$$I_B' = \frac{V_{CC} - V_{CE(\text{sat})} - V_T + V_R}{R_C + r_{bb}}$$

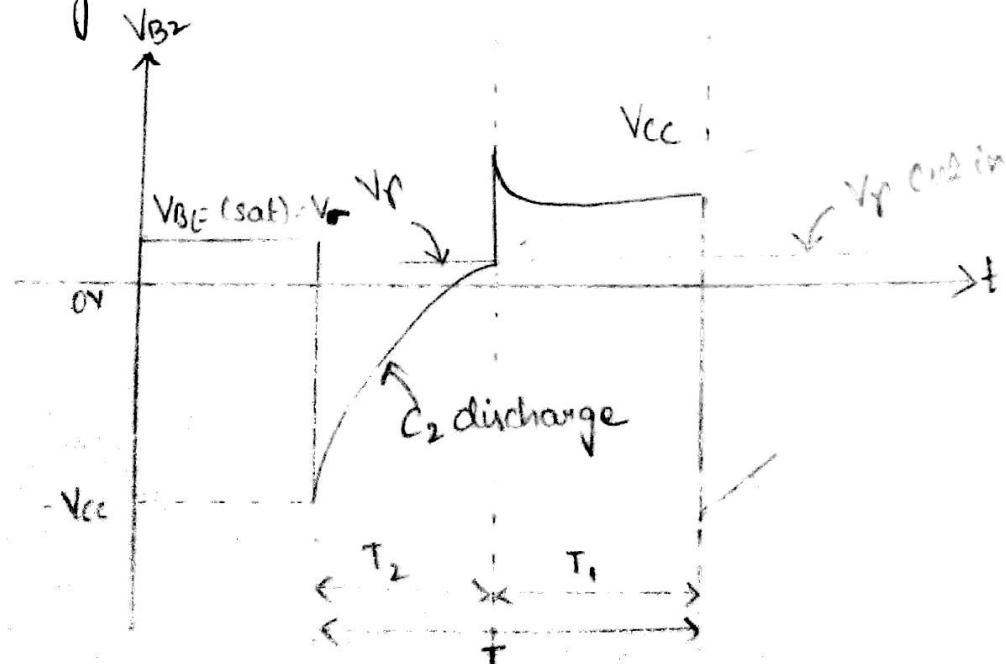Expression for Time period T :- For deriving the expression for time period T which is $T_1 + T_2$, consider the wave form at base of any transistor.



(4)

charges and with the capacitor C_2 discharges exponentially and the voltage V_{B2} increases exponentially.

$$V_i = \text{Initial value of } V_{B2} = -V_{cc} \quad \text{--- (1)}$$

$$V_f = \text{Final value of } V_{B2} = +V_{cc} \quad \text{--- (2)}$$

Though it stops increasing beyond V_p (cut-in) voltage, its rise is towards $+V_{cc}$, which is its final steady state value, with the time constant $\tau_2 = R_2 C_2$.

For the capacitor we can write the basic equation as,

$$V_o = V_f - (V_f - V_i) e^{-t/\tau}$$

Here V_o means the base voltage,

$$V_{B2} = V_{cc} - (V_{cc} - (-V_{cc})) e^{-t/R_2 C_2} \quad \text{--- (3)}$$

$$\therefore V_{B2} = V_{cc} - 2V_{cc} e^{-t/R_2 C_2} \quad \text{--- (4)}$$

$$V_{B2} = V_{cc} (1 - 2e^{-t/R_2 C_2}) \quad \text{--- (4)}$$

We know that at switching time,

$$t = T_2 \text{ and } V_{B2} = V_p \quad \text{--- (5)}$$

Substituting in equation (4)

$$V_p = V_{cc} (1 - 2e^{-T_2/R_2 C_2})$$

The best approximation to obtain T_2 is, $V_p = 0V$.

$$\therefore 0 = V_{cc} (1 - 2e^{-T_2/R_2 C_2})$$

$$\therefore 1 - 2e^{-T_2/R_2 C_2} = 0$$

$$e^{-T_2/R_2 C_2} = 0.5$$

$$\therefore \ln(e^{-T_2}/R_2 C_2) = \ln(0.5)$$

$$-\frac{T_2}{R_2 C_2} = -0.69$$

$$\boxed{T_2 = 0.69 R_2 C_2} \quad - \textcircled{7}$$

Similarly we can write the eqn at $t = T_1$ and find out expression for T_1 which same as for T_2 .

$$\boxed{T_1 = 0.69 R_1 C_1} \quad - \textcircled{8}$$

$$T = T_1 + T_2$$

$$T = 0.69(R_1 C_1 + R_2 C_2) \quad - \textcircled{9}$$

if $R_1 = R_2 = R$; $C_1 = C_2 = C$ then


$$\boxed{T = 0.69(2RC)} = 1.38RC \quad - \textcircled{10}$$

For this case we get square wave at the output which is symmetrical.

Distortion and its Elimination


It can be seen that, in the collector waveforms, there is certain distortion present. Instead of exact square wave we get vertical rising edges little bit rounded. This is called rounding. For square wave output such a rounding is undesirable and must be eliminated.

(5)

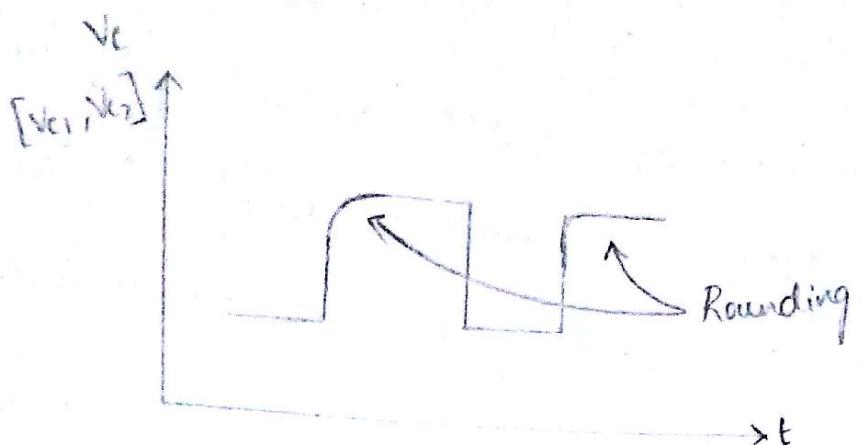

Rounding in collector waveforms

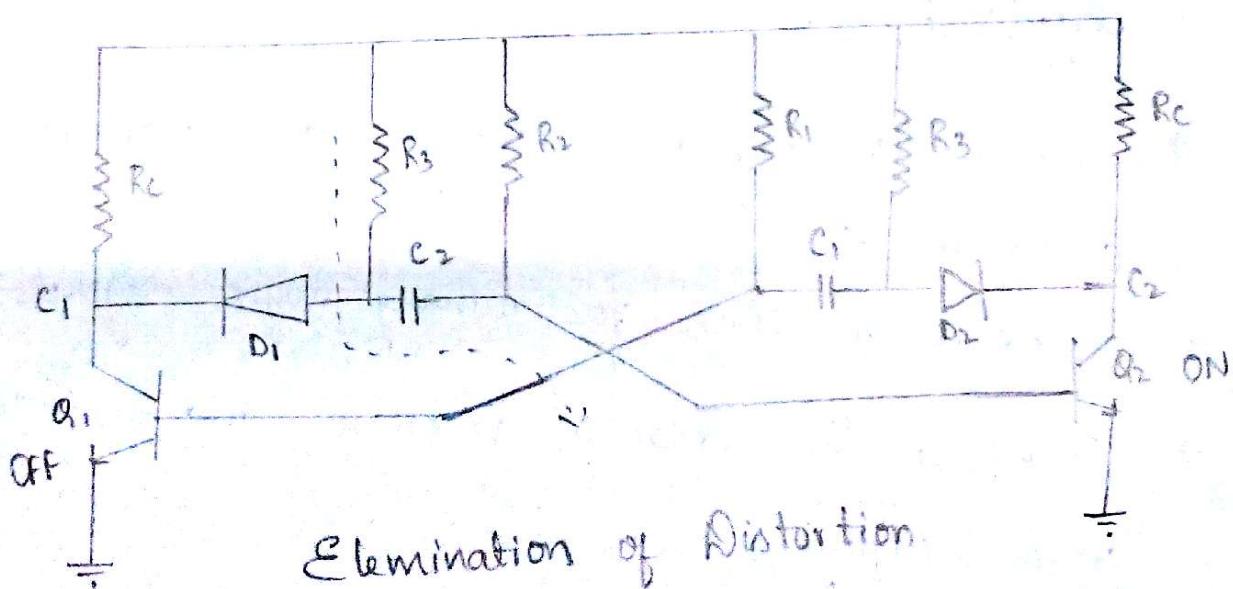
Such a rounding can be eliminated to obtain the vertical edges square wave by adding two collector diodes and two resistors. The collector coupled astable multi vibrator with collector diodes and auxiliary resistors.



Elimination of Distortion.

If Q_1 is OFF, then its collector voltage increases suddenly to V_{cc} thus making D_1 reverse biased.

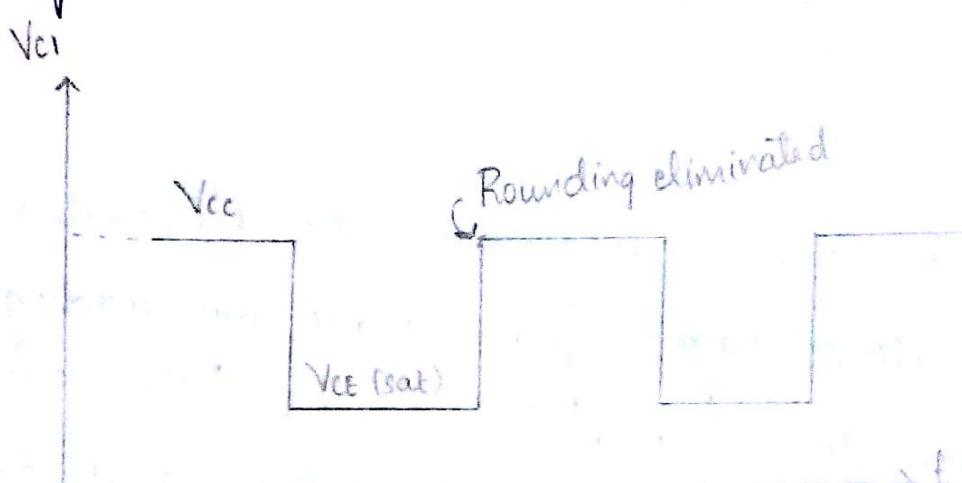Thus the charging of C_2 now takes place through R_3 rather than R_C . As current does not flow through R_C the collector voltage can rise suddenly to V_{CC} and the rounding at collector completely gets eliminated.



Elimination of Rounding.

Applications:

- * Used as square wave generator, voltage to frequency converter etc.
- * Used as a clock for binary logic signals.
- * Used in the digital voltmeter and switched mode power supply.
- * As an oscillator to generate wide range of audio and radio frequencies.


UNIT - 5

TUNED AMPLIFIER


High I/P current Practice
High O/P Voltage

Hi I/P
Low O/P
Voltage
Ladder - RC

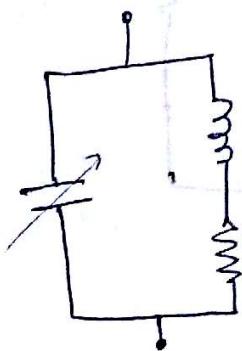- * Tuned amplifier (a) Narrow band amplifier:



$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

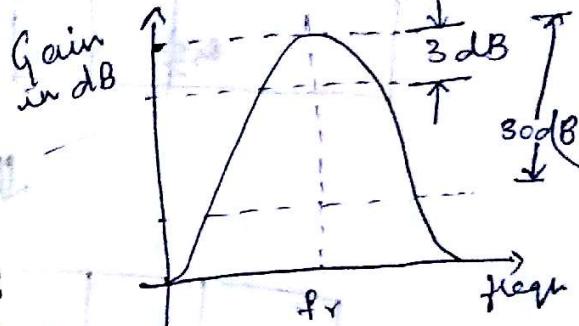

Ratio of 30dB B_w to 3dB
 B_w is called skirt selectivity

Q factor = $\frac{2\pi \times \text{Maximum energy stored per cycle}}{\text{Energy dissipated per cycle.}}$

- * Loaded and unloaded Q:

unloaded:

$Q_u = \frac{2\pi \times \text{Maximum energy stored per cycle}}{\text{Energy dissipated per cycle}}$




loaded:

$Q = \frac{2\pi \times \text{Maximum energy stored per cycle}}{\text{Energy dissipated per cycle} + \text{Energy dissipated due to presence of load}}$

Quality factor determines the 3dB bandwidth
for the reference circuit

$$B.W = \frac{f_0}{Q}$$

* Small Signal Tuned Amplifier

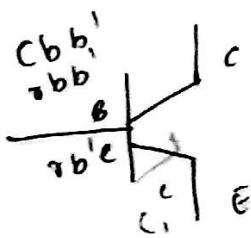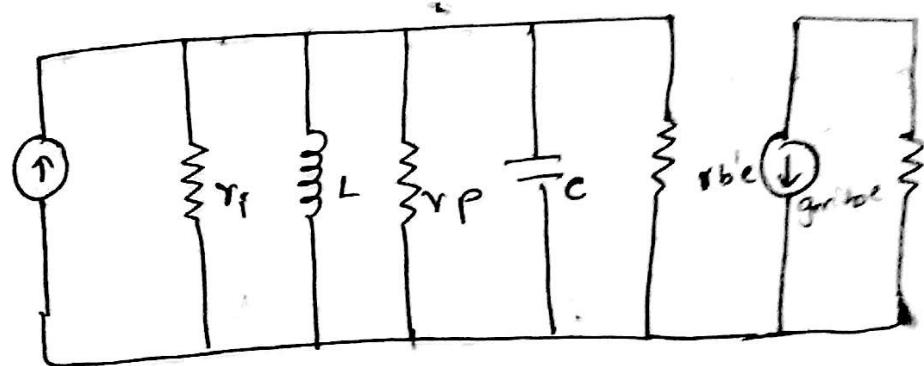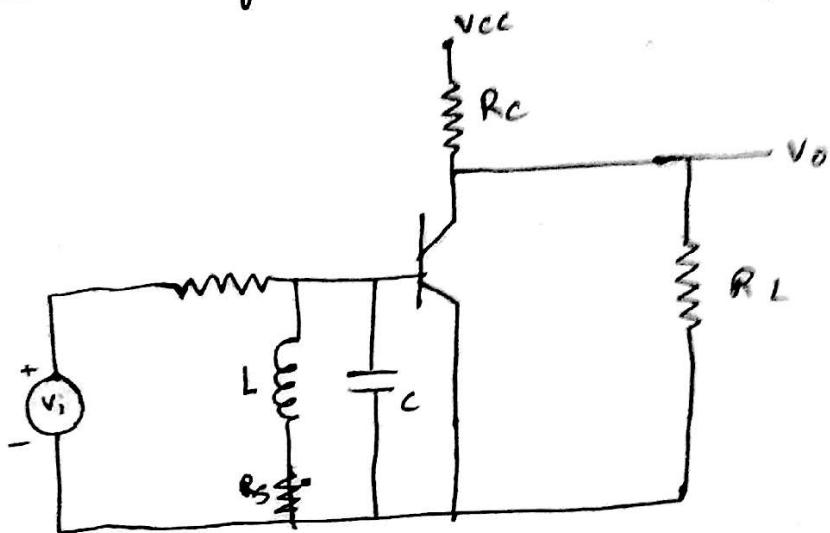

$$\text{where } C = c' + c b' e \parallel (1 + g_m R_L) \cdot c b' c$$

* Assumption:

- 1) $R_s \ll R_C$
- 2) $r_{bb'} = 0$.

- 3) $C = c' + c b' e \parallel (1 + g_m R_L) \cdot c b' c$

c' = external capacitance used to tune the ~~capacitor~~ tank circuit


$$(1 + g_m R_L) c b' c = \text{Miller capacitance}$$

R_s = loss in the coil

- 4) Assume coil losses are low, ω is very high

$$\Omega_L = \frac{\omega_L}{\gamma_s} \gg 1$$

$$Y_1 = \frac{1}{\gamma_s + j\omega L}$$

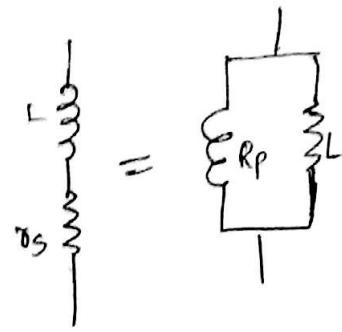

$$= \frac{1}{\gamma_s + j\omega L} \times \frac{\gamma_s - j\omega L}{\gamma_s - j\omega L}$$

$$= \frac{\gamma_s - j\omega L}{\gamma_s^2 + \omega^2 L^2} = \frac{\gamma_s}{\gamma_s^2 + \omega^2 L^2} - \frac{j\omega L}{\gamma_s^2 + \omega^2 L^2}$$

$$\omega_L \gg \gamma_s \quad (1)$$

for series circuit $Y_1 = \frac{\gamma_s}{\gamma_s^2 + \omega^2 L^2} + \frac{1}{j\omega L}$

for parallel circuit $Y_2 = \frac{1}{R_p} + \frac{1}{j\omega L} \quad (2)$

Equate Y_1 and Y_2

$$\frac{\gamma_s}{\gamma_s^2 + \omega^2 L^2} + \frac{1}{j\omega L} = \frac{1}{R_p} + \frac{1}{j\omega L}$$

$$\frac{1}{R_p} = \frac{\gamma_s}{\gamma_s^2 + \omega^2 L^2} \quad \left[\frac{\omega L}{\gamma_s} = \Omega \right]$$

$$\frac{1}{R_p} = \frac{\gamma_s}{\omega^2 L^2}$$

$$Y_{R_p} = \frac{\gamma_s^2}{\gamma_s \cdot \omega^2 L^2}$$

$$\frac{1}{R_p} = \frac{1}{\gamma_s \cdot \Omega^2}$$

$$R_p = \gamma_s \cdot \Omega^2$$

from the figure calculate $R = R_i || R_p || r_{b'e}$

Current gain of the amplifier:

$$A_i = \frac{-g_m R}{1 + j(\omega R C - \frac{R}{\omega L})} \quad (3)$$

$$= \frac{-g_m R}{1 + j\omega_0 R C \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)}, \text{ where } \omega_0^2 = \frac{1}{LC}$$

At resonant frequency :

$$\alpha_c = \frac{R}{\omega_0 L} = \omega_0 R C$$


$$A_i = \frac{-g_m R}{1 + j\alpha_c \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)}$$

At $\omega = \omega_0$ (maximum gain)

$$A_i (\max) = -g_m R \quad \text{gain}$$


At 3 dB condition ,




$$|A_i| = \frac{g_m R}{\sqrt{2}}$$

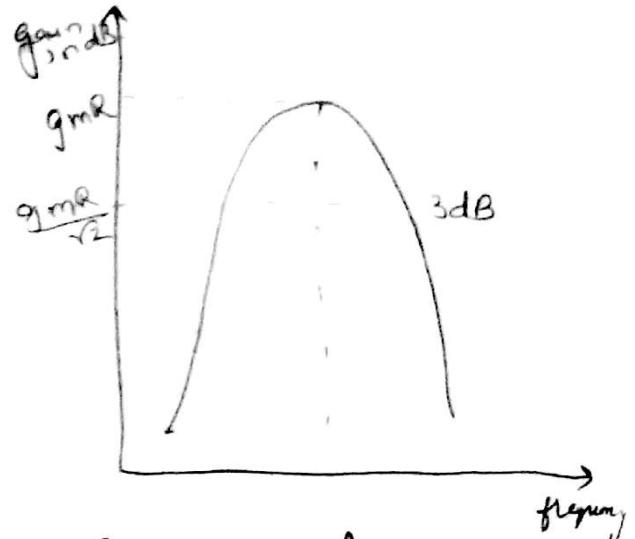

100%
**

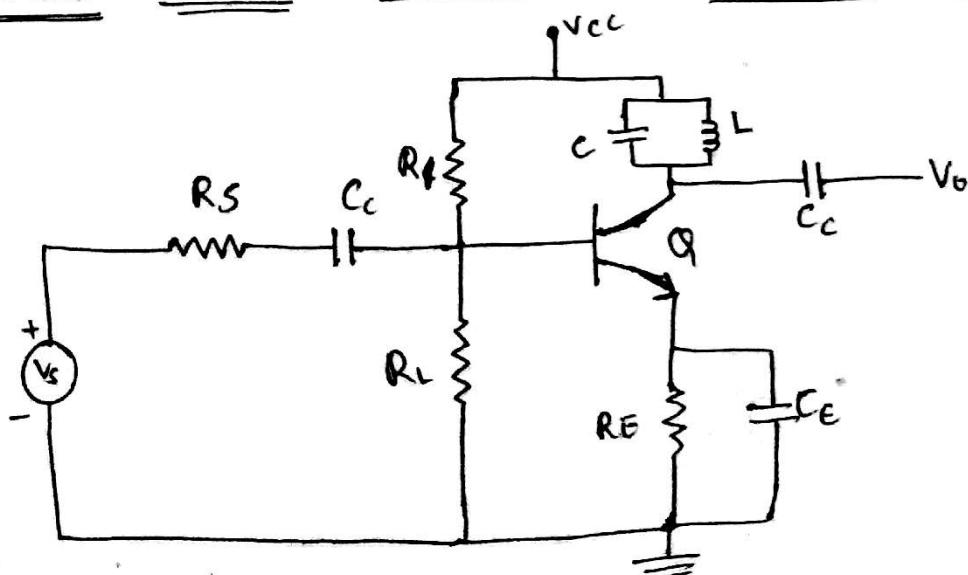SINGLE TUNED CAPACITIVE COUPLED AMPLIFIER;



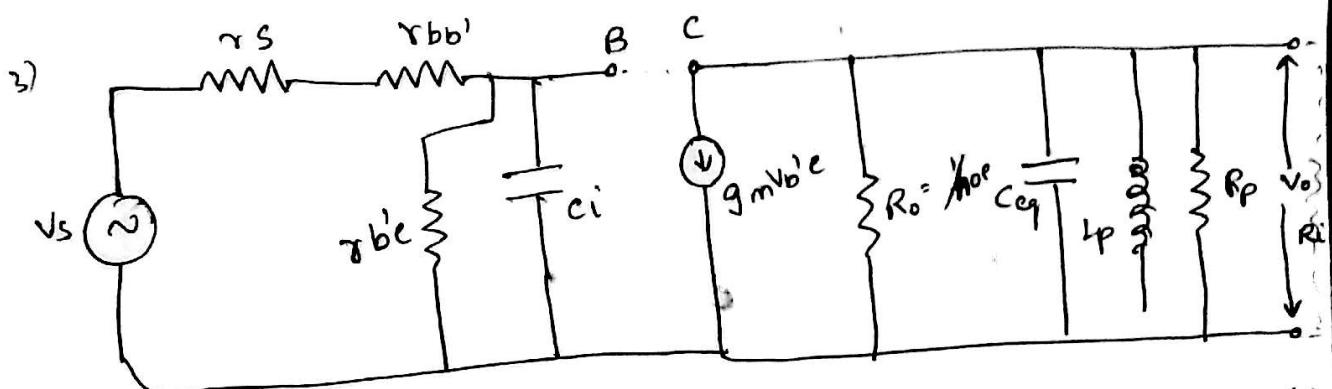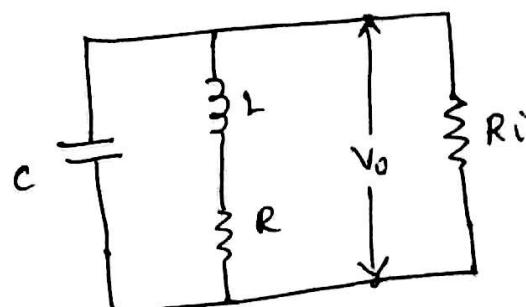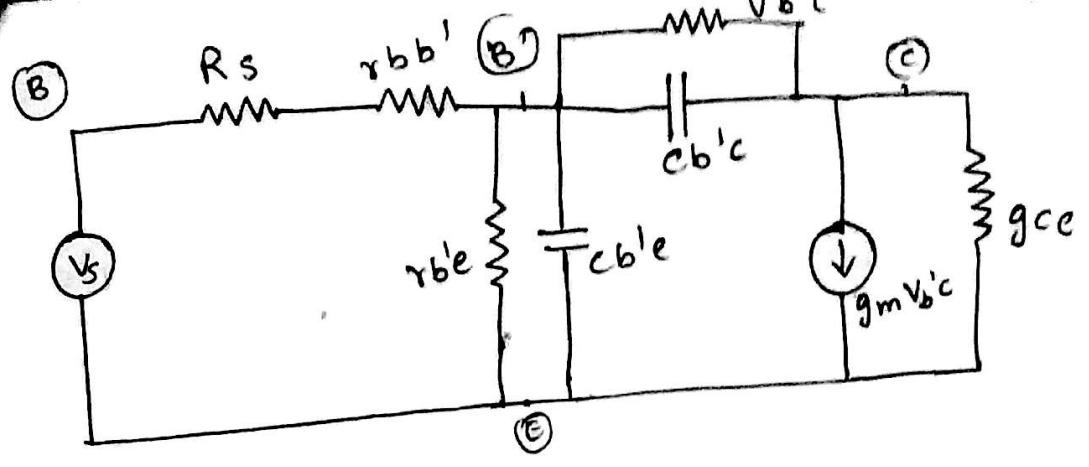

By Applying Miller theorem we have that
equivalent diagram

$$\text{Here, } C_i = C_{b'e} + C_{b'e} (1 - A)$$


$$C_{eq} = C_{b'e} \left(\frac{1 - A}{A} \right) + C$$

$$G_{ce} = \frac{1}{R_{ce}} = \frac{1}{R_{ce}} = \frac{1}{R_{ce}}$$

one series RL circuit represented at a
parallel circuit in the 3rd diagram

$$\gamma = \frac{1}{R + j\omega L}$$

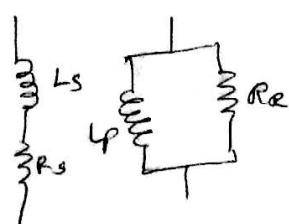multiply $(R - j\omega L)$ on numerator
and denominator



$$Y = \frac{R - j\omega L}{R^2 + j^2 \omega^2}$$

$$= \frac{R}{R^2 + L^2 \omega^2} - \frac{j\omega L}{R^2 + L^2 \omega^2}$$

$$= \frac{R}{R^2 + L^2 \omega^2} - \frac{j\omega^2 L}{\omega(R^2 + \omega^2 L^2)}$$

$$= \frac{1}{R_p} + \frac{1}{j\omega L_p}$$

where,

$$R_p = \frac{R^2 + \omega^2 L^2}{R}$$

$$L_p = \frac{R^2 + \omega^2 L^2}{\omega^2 L}$$

→ * Centre frequency :

~~Electronics~~

$$f_r = \frac{1}{2\pi \sqrt{L_p C_{eq}}}$$

$$\text{where, } L_p = \frac{R^2 + \omega^2 L^2}{\omega^2 L}$$

$$C_{eq} = \text{able to decrease } \left(\frac{1-A}{A}\right) + C$$

→ * Quality factor (α)

Quality factor ' α ' of the coil is given

by :

$$\alpha = \cancel{\omega_r} \frac{\omega_r L}{R}$$

the
Y high.
R

The tuned amplifier Q value is always very high. $Q \gg 1$, so $\omega_L \gg R$

$$R_p = \frac{R^2 + \omega^2 L^2}{R}$$

$$\frac{R + \omega^2 L^2}{R}$$

$$R_p = \frac{\omega^2 L^2}{R}$$

Similarly, $L_p = \frac{R^2 + \omega^2 L^2}{\omega^2 L}$


$$\frac{R^2}{\omega^2 L} + \frac{\omega^2 L^2}{\omega^2 L}$$

$$L_p = L$$

$$R_p = \frac{\omega_r^2 L^2}{R}$$

$$= \omega_0 \cdot Q_r \cdot L \quad [Q_r = \frac{\omega_0 L}{R}]$$

$$Q_r = \frac{R_p}{\omega_0 \cdot L}$$

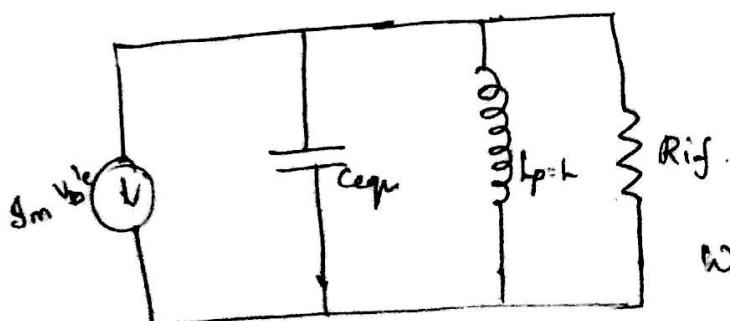

$$Q_{eff} = \frac{R_f}{\omega_0 L} \quad (1)$$

$$\omega_0 \cdot C_{eq} \cdot R_f$$

$$\text{when } R_s = R_o \parallel R_p \parallel R_i$$

Effective Quality factor,

$$Q_{eff} = \frac{\text{Susceptance of Inductance } (B_{L1}) \text{ Capacitance}}{\text{conductance of Shunt resistance } R_s}$$

→ * Voltage gain (A_v):

A_v for tuned amplifier is given by

$$A_v = -g_m \frac{r_{b'e}}{r_{bb'} + r_{b'e}} \times \frac{R_t}{1 + 2j\omega_{eff} \cdot \delta}$$

where,

$$R_t = R_o \parallel R_p \parallel R_i$$

δ = fraction variant in the resonant frequency

$$A_v (\text{at resonance}) = -g_m \frac{r_{b'e}}{r_{bb'} + r_{b'e}} \times R_t$$

$$\left| \frac{A_v}{A_v (\text{at resonance})} \right| = \frac{1}{\sqrt{1 + (2\delta\omega_{eff})^2}}$$

→ * 3dB Bandwidth:

The 3dB bandwidth of a single tuned amplifier is given by,

$$\Delta f = \frac{1}{2\pi R_t C_{eq}}$$

$$= \frac{\omega_r}{2\pi \omega_{eff}}$$

$$\therefore \omega_{eff} = \omega_r R E C_{eq}$$

$$= \frac{f_r}{\alpha_{eff}} \quad \therefore \omega_r = 2\pi f_r$$

$B_w = \frac{f_r}{\alpha_{eff}}$

of Cascaded Single tuned amplifier On Bandwidth

$$\left| \frac{A_V}{A_V(\text{at resonance})} \right| = \frac{1}{\sqrt{1 + (2\delta Q_{eff})^2}}$$

n - number of stages.

$$\left| \frac{A_V}{A_V(\text{at resonance})} \right|^n = \left[\frac{1}{\sqrt{1 + (2\delta Q_{eff})^2}} \right]^n$$

$$= \frac{1}{[(1 + (2\delta Q_{eff})^2)]^{n/2}}$$

At 3dB condition,

$$\left| \frac{A_V}{A_V(\text{at resonance})} \right|^n = \frac{1}{\sqrt{2}} = \left[\frac{1}{(1 + (2\delta Q_{eff})^2)} \right]^{n/2}$$

$$\frac{1}{[(1 + (2\delta Q_{eff})^2)]^{n/2}} = \frac{1}{\sqrt{2}}$$

$$[(1 + (2\delta Q_{eff})^2)]^{n/2} = 2^{1/2}$$

$$[(1 + (2\delta Q_{eff})^2)]^n = 2$$

$$1 + (2\delta Q_{eff})^2 = 2^{n/2}$$

$$(2\delta Q_{eff})^2 = 2^{n/2}$$

$$(2\delta Q_{eff}) = \sqrt{2^{n/2} - 1}$$

$$\text{Substitute } \delta = \frac{\omega - \omega_r}{\omega_r} = \frac{f - f_r}{f_r}$$

$$2 \left(\frac{f - f_r}{f_r} \right) Q_{eff} = \sqrt{2^{n/2} - 1}$$

$$2(f - f_r) \cdot Q_{eff} = \pm f_r \sqrt{2^{n/2} - 1}$$

$$(f - f_r) = \pm \frac{f_r}{2Q_{eff}} \sqrt{2^{n/2} - 1}$$

Let us assume f_1 and f_2 are the lower and upper cut off frequency

Higher cut-off frequency:

$$f_2 - f_r = \pm \frac{f_r}{2 Q_{eff}} \sqrt{2^{1/n} - 1}$$

Lower cut-off frequency:

$$f_r - f_1 = \pm \frac{f_r}{2 Q_{eff}} \sqrt{2^{1/n} - 1}$$

$$\begin{aligned} B\omega_n &= (f_2 - f_r) + (f_r - f_1) \\ &= f_2 - f_1 \end{aligned}$$


$$B\omega_n = \frac{f_r}{Q_{eff}} \sqrt{2^{1/n} - 1}$$

$$B\omega_n = B\omega_1 \sqrt{2^{1/n} - 1}$$




losses

- 1) copper loss
- 2) Eddy current loss
- 3) Hysteresis loss

* DOUBLE TUNED AMPLIFIER:

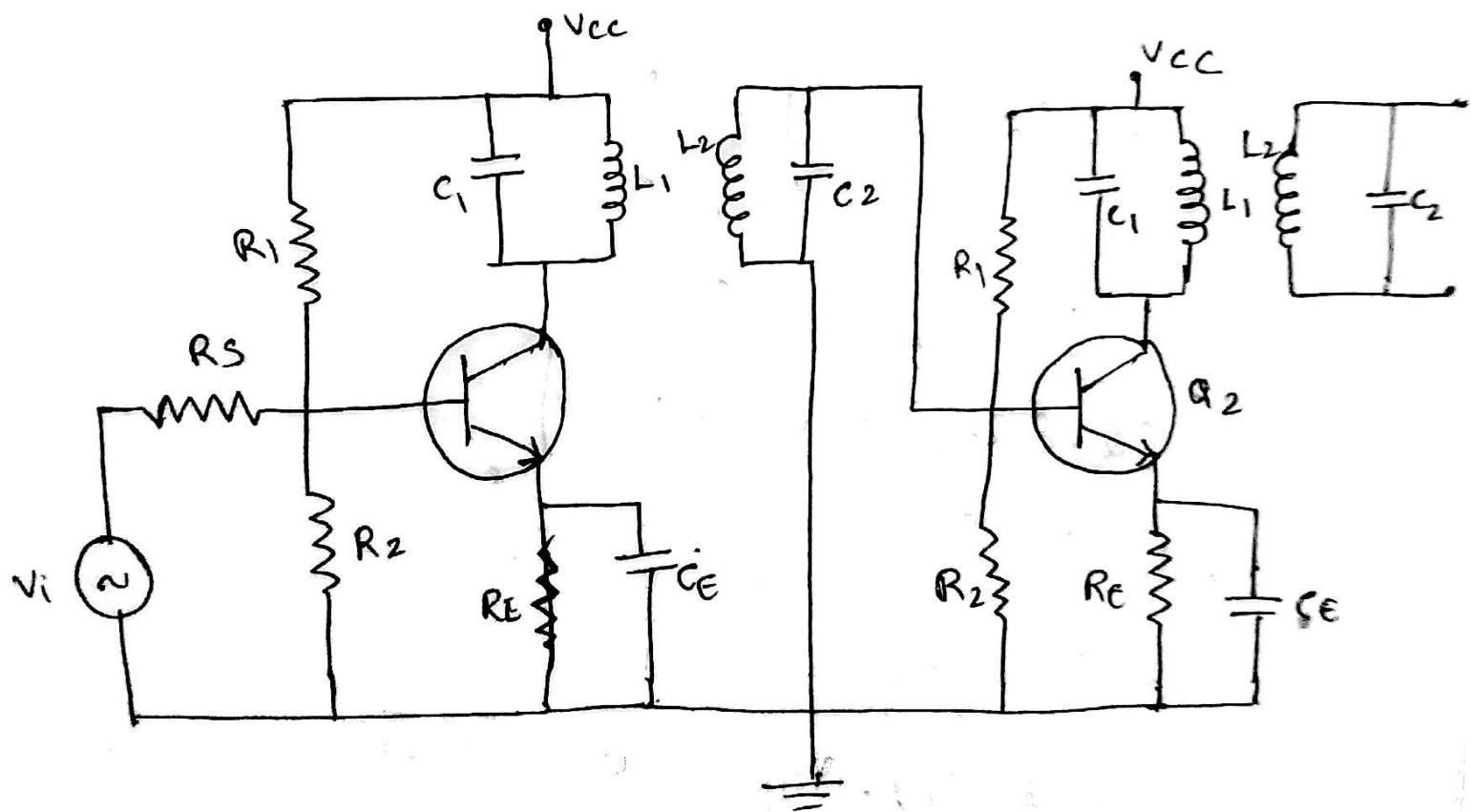

Equivalent circuits:

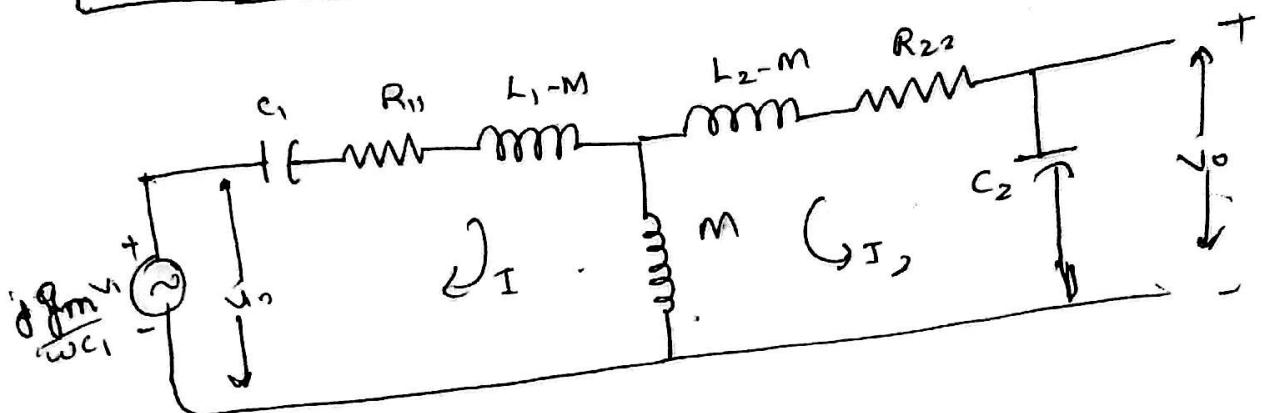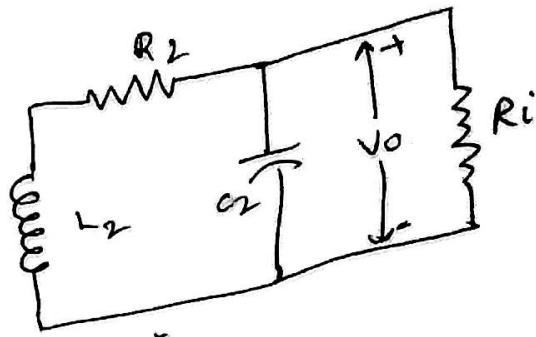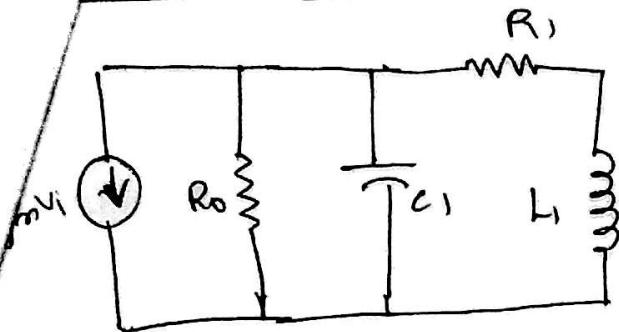

$$R_p = \frac{\omega^2 L^2}{R} \quad (\text{i.e.}) \quad R = \frac{\omega^2 L^2}{R_p}$$

From equivalent circuit,

$$R_{11} = \frac{\omega_0^2 L_1^2}{R_0} + R_1$$

$$R_{12} = \frac{\omega_0^2 L^2}{R_i} + R_2$$

$$\text{W.K.T.}, \quad Q = \frac{\omega_0 L}{R}$$

$$\therefore Q_1 = \frac{\omega_0 L}{R_{11}} \quad \text{and} \quad Q_2 = \frac{\omega_0 L_2}{R_{12}}$$

Q factor both circuits are kept same,

$$\therefore Q_1 = Q_2 = Q \quad \text{and}$$

resonant frequency,

$$\omega_r^2 = \frac{1}{L_1 C_1} = \frac{1}{L_2 C_2}$$

The o/p voltage,

$$V_o = \frac{-j}{\omega_r C_2} I_2$$

Y_T (transfer admittance)


$$Y_T = \frac{I_2}{V_1} = \frac{I_2}{I_1 Z_{11}} = \frac{A_i}{Z_{11}}$$

where,

$$Z_{11} = \frac{V_1}{I_1} = Z_i - \frac{Z_f^2}{Z_0 + Z_L}$$

and
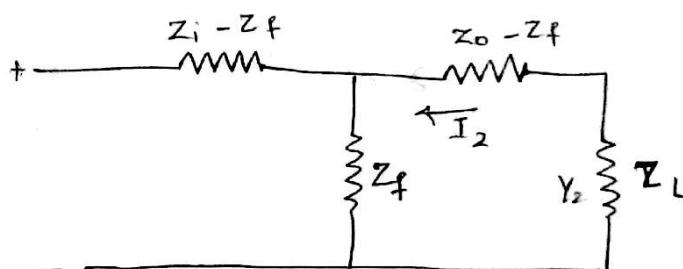
$$A_i = \frac{I_2}{I_1} = \frac{-Z_f}{Z_0 + Z_L}$$



$$Z_f = j\omega_s M$$

$$Z_i = R_{11} + j(\omega L_1 - \frac{1}{\omega c_1})$$

$$Z_0 + Z_L = R_{11} + j(\omega L_2 - \frac{1}{\omega c_2})$$

By Simplifying,

$$Z_f = j\omega_s M = j\omega_s K \sqrt{L_1 L_2}$$

Multiply numerator and denominator by $\omega_s L_1$ for Z_i ,

we get

$$Z_i = \frac{R_{11} \omega_s L_1}{\omega_s L_1} + j\omega_s L_1 \left(\frac{\omega L_1}{\omega_s L_1} - \frac{1}{\omega c_1 \omega_s L_1} \right)$$

$$= \frac{\omega_r L_1}{Q} + j\omega_r L_1 \left(\frac{\omega}{\omega_r} - \frac{\omega_r}{\omega} \right)$$

$$\left(\because Q = \frac{\omega_r L}{R_{11}} \text{ and } \frac{1}{\omega_s L} = \omega_s c \right)$$

$$= \frac{\omega_r L_1}{Q} + j\omega_0 L_1 (\alpha \delta)$$

$$\left(\because \frac{\omega}{\omega_r} - \frac{\omega_r}{\omega} = 1 + \delta - (1 - \delta) = 2\delta \right)$$

$$= \frac{\omega_r L_1}{Q_{11}} + (1 + j2\alpha\delta)$$

$$Z_0 + Z_L = R_{22} + j \left(\omega L_2 - \frac{1}{\omega C_2} \right)$$

By analysing, Z_i can be written as,

$$Z_0 + Z_L = \frac{\omega_r L_2}{Q} + (1 + j 2\alpha \delta)$$

Then,

$$Y_T = \frac{Z_f}{Z_f^2 - Z_i (Z_0 + Z_L)}$$

$$= \frac{1}{Z_f - Z_i (Z_0 + Z_L) / Z_f}$$

$$Y_T = \frac{1}{j \omega_r K \sqrt{4L_2} - \left[\frac{\omega_r L_1}{Q} (1 + j 2\alpha \delta) \left\{ \frac{\omega_r L_2}{Q} (1 + j 2\alpha \delta) \right\} \right] / j \omega_r K \sqrt{L_1 L_2}}$$

$$Y_T = \frac{K \alpha^2}{\omega_r \sqrt{L_1 L_2} [4\alpha \delta - j(1 + K^2 \alpha^2 - 4\alpha^2 \delta^2)]}$$

Substituting value of I_2 (i.e) $v_i \propto Y_T$,


$$\text{we get } v_o = \frac{-j}{\omega_r C_2} \frac{j g_m v_i}{\omega_r C_1} \left[\frac{K \alpha^2}{\omega_r \sqrt{L_1 L_2} [4\alpha \delta - j(1 + K^2 \alpha^2 - 4\alpha^2 \delta^2)]} \right]$$

$$\therefore v_i = \frac{j g_m}{\omega C_1} v_o$$

$$A_v = \frac{v_o}{v_i} = g_m \frac{\omega_r^2 L_1 L_2}{\omega_r \sqrt{L_1 L_2}} \left[\frac{K \alpha^2}{4\alpha \delta - j(1 + K^2 \alpha^2 - 4\alpha^2 \delta^2)} \right]$$


$$\therefore \left(\frac{1}{\omega_r C} = \omega_r L \right)$$
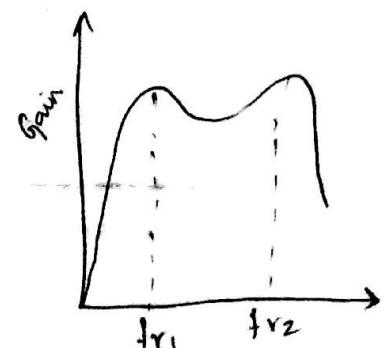
$$= \left[\frac{g_m \omega_r \sqrt{L_1 L_2} K \alpha^2}{4\alpha \delta - j(1 + K^2 \alpha^2 - 4\alpha^2 \delta^2)} \right]$$




* Staggered tuned amplifier.


(a) Response of individual stages

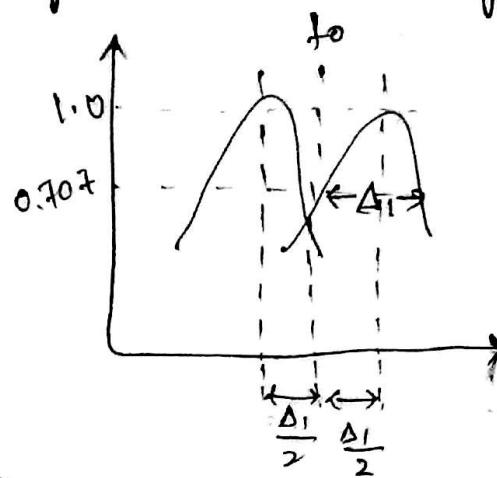

(b) Overall Response of staggered pair

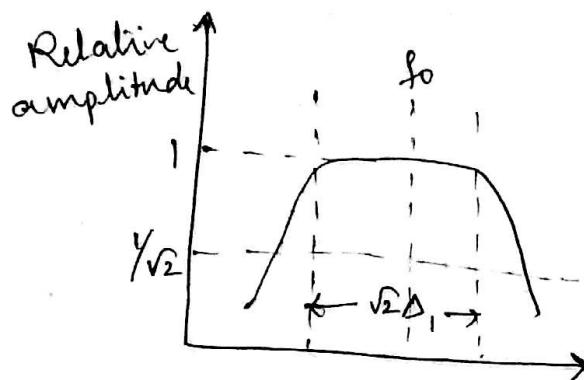

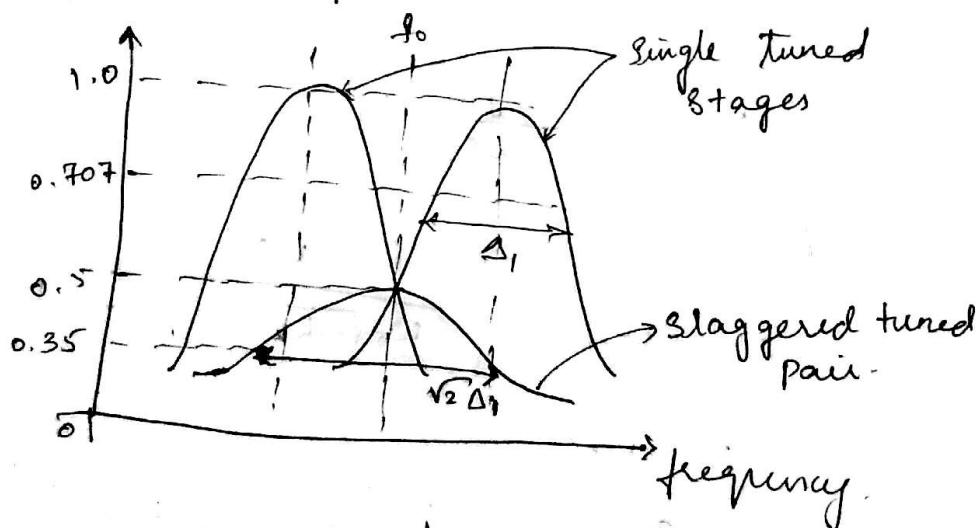Response of individually tuned and staggered tuned pair:



$$\frac{A_v}{A_v \text{ (resonance)}} = \frac{1}{1 + 2 \sqrt{\Omega_{eff} \delta}}$$

$$= \frac{1}{g x + 1}, \text{ where } x = \omega \Omega_{eff} \delta$$

$$f_{r_1} = f_r + \delta \quad \text{and} \quad f_{r_2} = f_r - \delta$$

According to tuned frequencies the selectivity junctions can be,

$$\frac{A_v}{A_v(\text{resonance})} = \frac{1}{1 + j(x+1)} \quad \text{and}$$

$$\frac{A_v}{A_v(\text{resonance})} = \frac{1}{1 + j(x-1)}$$

Overall gain of these 2 stages is product of individual stages

$$\therefore \frac{A_v}{A_v(\text{resonance})_{\text{cascaded}}} = \frac{A_v}{A_v(\text{at resonance})} \times \frac{A_v}{A_v(\text{at resonance})}$$

$$= \frac{1}{1 + j(x+1)} \times \frac{1}{1 + j(x-1)}$$

$$= \frac{1}{2 + 2jx - x^2} = \frac{1}{(2-x^2) + (2jx)}$$

$$\therefore \left| \frac{A_v}{A_v(\text{resonance})} \right|_{\text{cascaded}} = \frac{1}{\sqrt{(2-x^2)^2 + (2x)^2}}$$

$$= \frac{1}{\sqrt{4 - 4x^2 + x^4 + 4x^2}} = \frac{1}{\sqrt{4 + x^4}}$$


Substituting the value of x , we get.

$$\left| \frac{A_v}{A_v(\text{resonance})} \right|_{\text{cascaded}} = \frac{1}{\sqrt{4 + (2Q_{eff}\delta)^4}}$$

$$= \frac{1}{\sqrt{4 + 16 Q_{eff}^4 \delta^4}}$$

$$= \frac{1}{2 \sqrt{1 + 4 Q_{eff}^4 \delta^4}}$$

* Neutralization

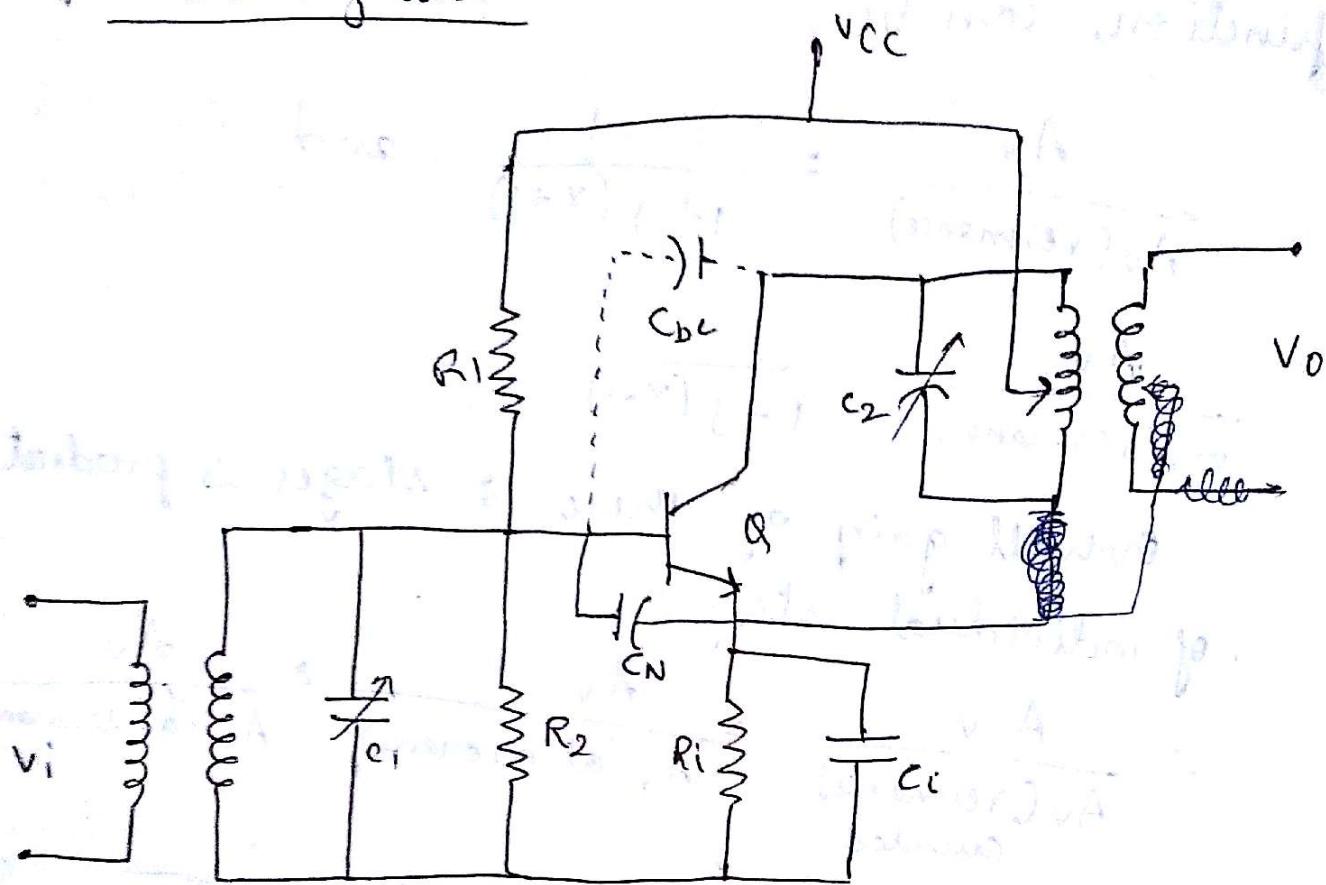

Types :


- (1) Magnetiline Neutralization
- (2) Modified Magnetiline Neutralization.
- (3) Neutralization using coil.

(b)

EMITTER COUPLED MONOSTABLE MULTIVIBRATOR :-

*combination of
regenerative circuit*

Circuit diagram :-

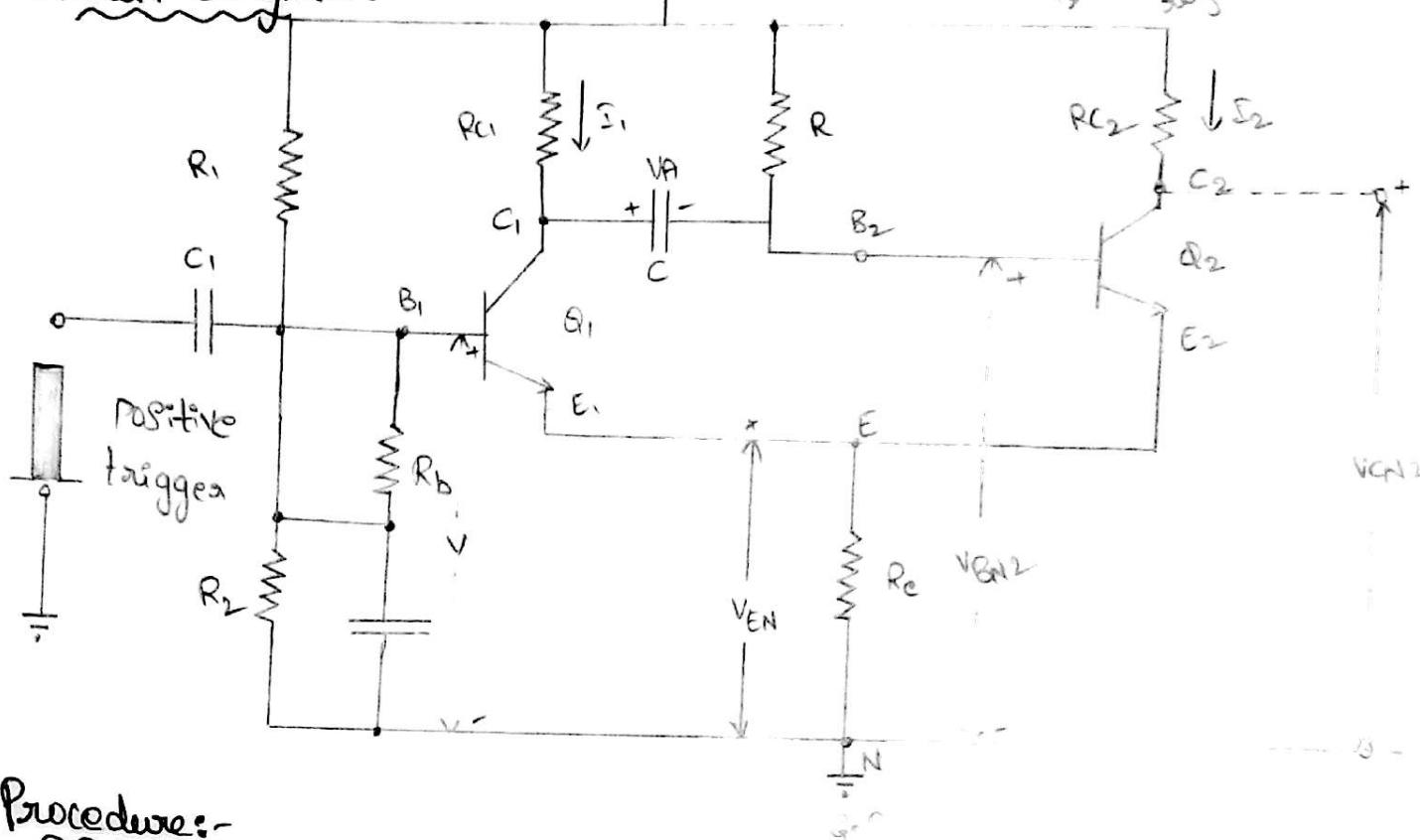

Procedure :-

The emitter terminals of both the transistors are coupled together hence called emitter coupled. The connection from collector C_2 to the base B_1 is absent. The feedback is provided through a common emitter resistance R_b . A negative supply is not required.

Key point :-

→ As collector C_2 is not involved in the regenerative loop, it is ideal to take output voltage from this terminal.

The input trigger is connected to terminal B_1 , which is also not connected to any other point. Thus trigger input source cannot load the circuit.

In collector coupled monostable, Q_1 controls the gate Q_2 .
It is not possible to maintain Q_1 stable. But in the emitter coupled monostable, Q_1 can be stabilized with emitter resistance R_E . Hence control of T with Q_1 can be achieved. This is possible because when Q_2 goes off, Q_1 goes on and operates with sufficient emitter resistance.

The Q_1 duration can be controlled by biasing voltage V and it is observed that T varies linearly with V .

Key points:-

Thus emitter coupled monostable is used as a perfect gate wave generator whose gate width can be controlled easily and linearly with the help of an electric signal.

Waveforms:-

The waveform at the emitters is more important in this monostable. Consider the mode of operation with Q_1 cut-off and Q_2 in saturation in the stable state.

In the stable state Q_1 is off and Q_2 is on. The Q_2 is in saturation. It derives base drive from V_{CC} and resistance R_E . Due to its emitter current, it produces a voltage V_{EN2} across the resistance R_E . This voltage is more than the base potential of Q_1 which ensures that Q_1 remains off.

When the positive trigger is applied to the base of Q_1 , then v_B becomes more than V_{EN2} which drives Q_1 into conduction. Due to

(7)

this, the collector voltage of Q_1 drops by $I_1 R_C$. This negative step is applied to the base of Q_2 , which makes Q_2 off. The capacitor C now charges through R from V_{CC} through ON transistor Q_1 . The ON Q_1 develops potential drop of V_{EN1} across R_E . This is the quasistable state with Q_1 ON and Q_2 OFF.

As the capacitor charges, the base B_2 of Q_2 becomes more positive. When the potential V_{BN2} becomes more than $V_{EN1} + V_f$ then the transistor Q_2 starts conducting. Due to the regenerative feedback, Q_2 goes into saturation while Q_1 is cut-off. Thus the stable state with Q_1 OFF and Q_2 ON is achieved.

The waveforms are shown in the figure.

Extreme limits of V :-

In stable state Q_1 must be OFF. Hence there is a limit V_{max} for bias voltage V to be applied to base of Q_1 .

while when Q_1 is ON, then $I_1 R_E$ drop must be large so as to cut-off Q_2 . This puts a minimum limit V_{min} for bias voltage V .

Key point :-





The bias voltage V must be between V_{max} and V_{min} , for proper operation of the circuit

for Q_1 OFF in stable state, $V_{EN2} > V_f$

$$\therefore V_{max} = V_{EN2} + V_f$$

①

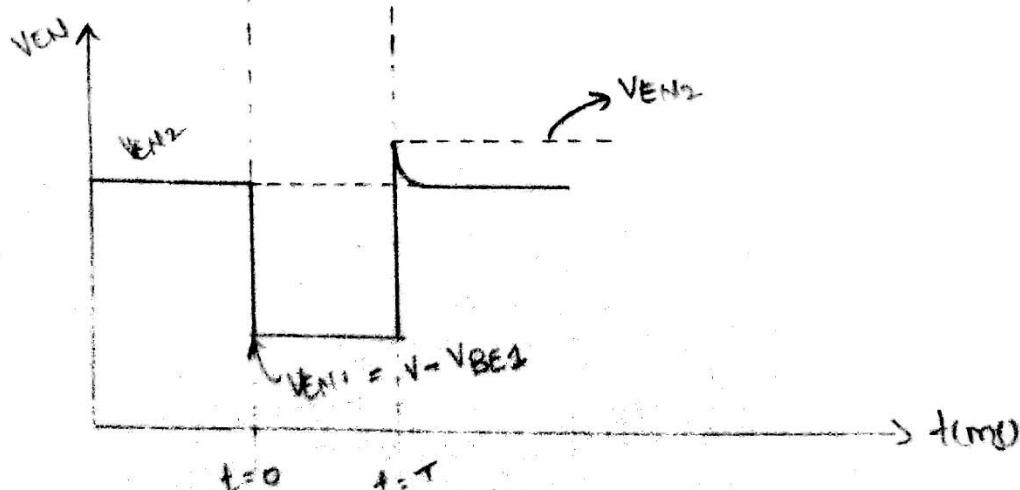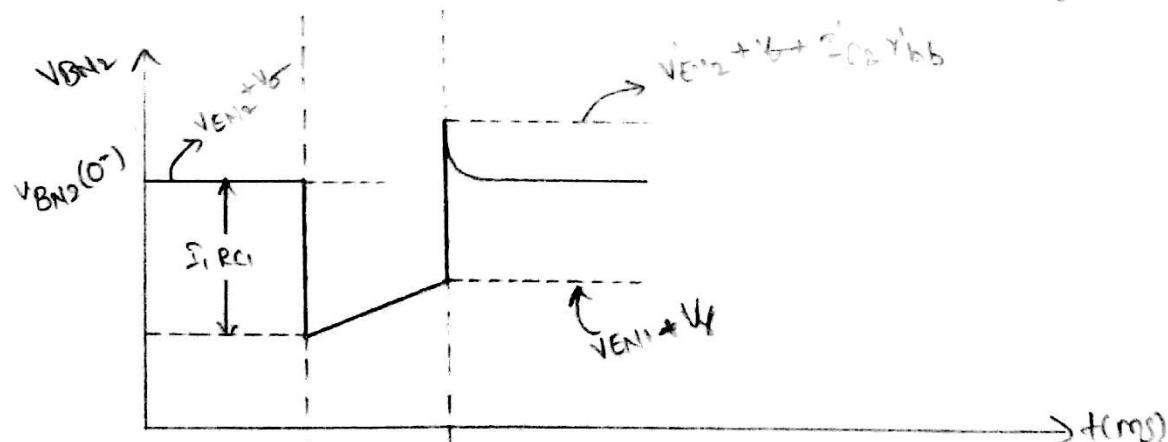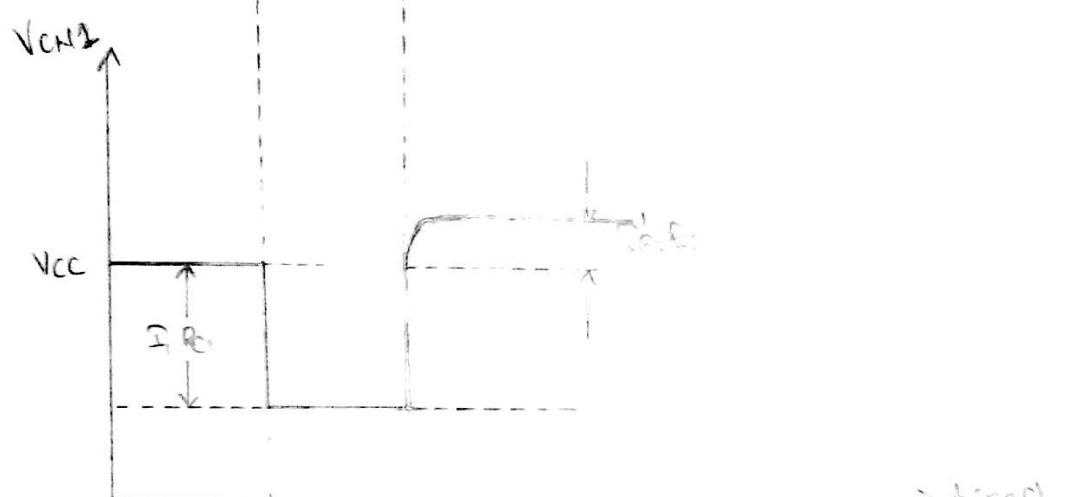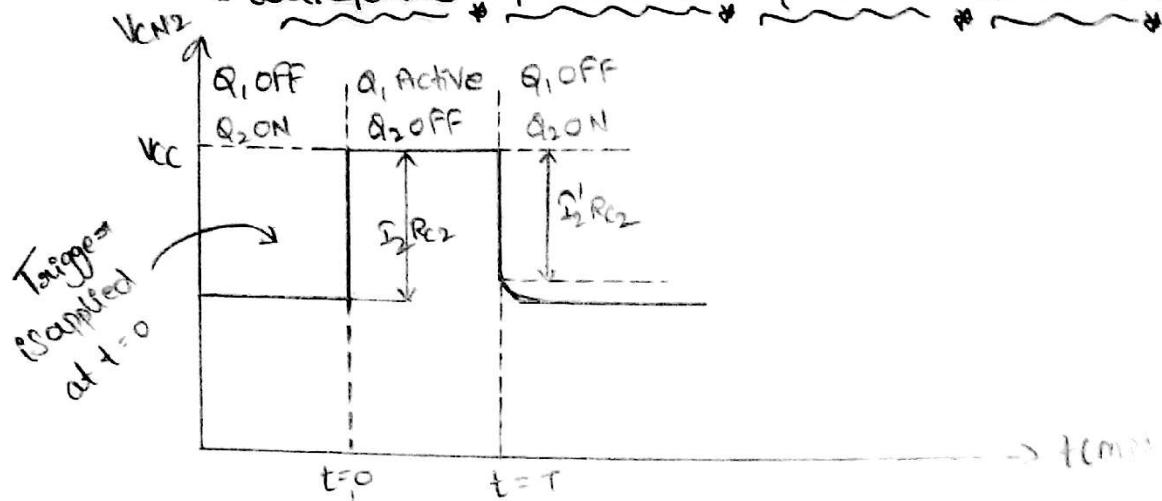* Waveforms of Emitter Coupled monostable multivibrator



(8)

stable for having minimum I_1 , to cut-off Q_2 is quasi-stable state, V_{min} is given by,

$$V_{min} = (V_{EN1})_{min} + V_{BE1} \quad \rightarrow ②$$

Thus equation ②, further can be rearranged as,

$$V_{min} = V_{BE1} + \frac{V_{BN2}(0^-) - V_{F2} + (R_{C1}/R)(V_{CC} - V_{F2})}{1 + \left(\frac{R_{C1}}{R}\right) + \left(\frac{R_{C1}}{R_C}\right) [h_{FE} / (1+h_{FE})]}$$

Gate width of emitter coupled monostable :-

The expression of gate width can be derived using the basic relation,

$$V_C = V_F + (V_i - V_F) e^{-t/\gamma} \quad ①$$

The voltage V_{BN2} just after trigger is applied is given by,

$$V_{BN2}(0^+) = V_{BN2}(0^-) - I_1 R_{C1} \quad ②$$

If Q_2 did not conduct, V_{BN2} would approach V_{CC} .

$\therefore V_{BN2}$ = Instantaneous voltage at B_2

$$\therefore V_{BN2} = V_{CC} - [V_{CC} - V_{BN2}(0^-) + I_1 R_{C1}] e^{-t/\gamma} \quad ③$$

$$\text{where } \gamma = C(R+R_{C1})$$

At $t = T^-$, just before pulse ends,

$$V_{BN2} = V_{EN1} + V_{F2} \quad ④$$

Equating equations ③ and ④,

$$V_{EN1} + V_{F2} = V_{CC} - [V_{CC} - V_{BN2}(0^-) + I_1 R_{C1}] e^{-t/\gamma} \quad \{t = T\}$$

Solving for T , the gate width is obtained as,

$$T = \gamma \ln \left\{ \frac{V_{CC} - V_{Gm2}(0) + I_1 R_{C1}}{V_{CC} - V_{EN1} - V_{Y2}} \right\} \quad (5)$$

Key point :-

This time T varies linearly with the bias voltage V . Due to this feature, it can be used as voltage to time converter.


⑨

①

Collector Coupled Monostable Multivibrator.

The monostable multivibrator has one stable state. When an external trigger is applied, the circuit changes its state from stable to quasi-stable state. And then automatically, after some time interval T , the circuit returns back to the original normal stable state. The time T is dependent on the circuit components.

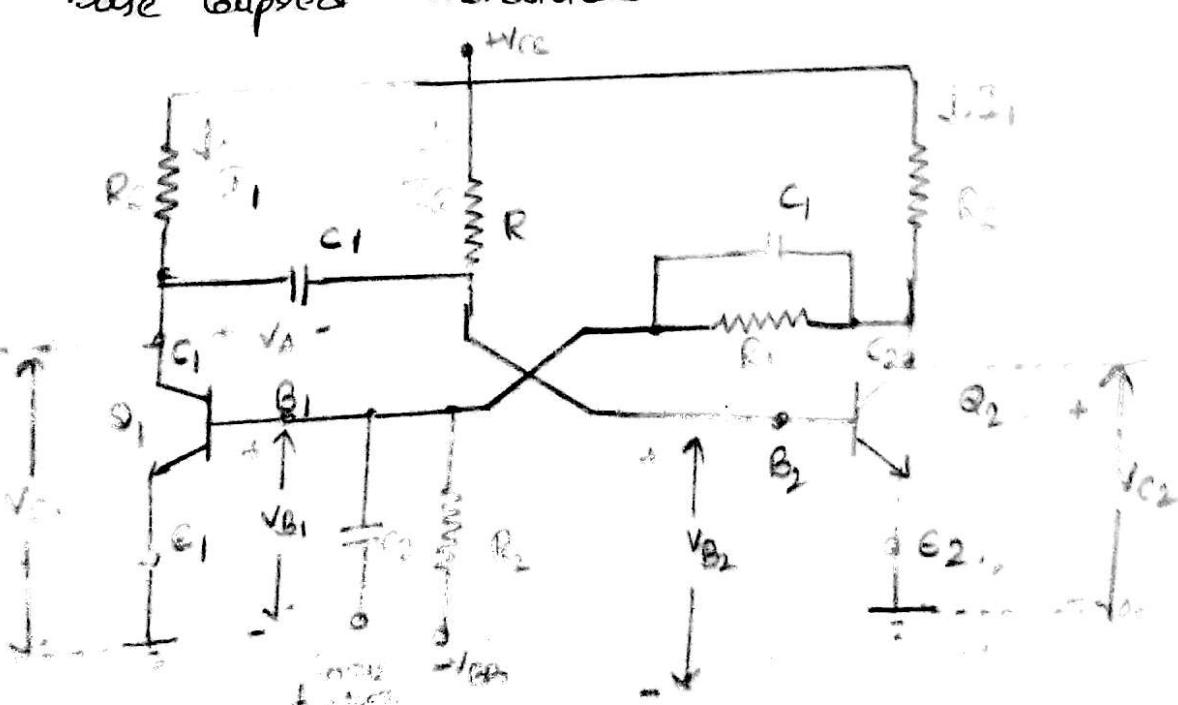The below figure shows the Collector Coupled monostable multivibrator circuit, which uses npn transistors. This circuit is also called Collector to base coupled monostable



- The Q_1 & Q_2 are identical npn transistors. The two collector resistances are equal to R_C .
- The output of Q_2 i.e., collector of Q_2 is coupled to the base of Q_1 , through a resistance R_1 , which is shunted by a same capacity C_1 .
- The capacitor C_1 is a speed-up capacitor required to make the transition fast & reduce the transition time. The collector of Q_1 is coupled to the base of Q_2 through a capacitor C .
- Thus a d.c. coupling in bistable multivibrator is replaced by a capacitive coupling.
- The resistance R at the input of Q_2 is returned to the supply voltage V_{CC} .
- The value of R_2 and $-V_{BB}$ are chosen such that the transistor Q_1 is off, by reverse biasing it.
- The transistor Q_2 is ON i.e., in saturation. This is possible by forward biasing Q_2 with the help of V_{CC} and resistance R . Thus Q_2 ON and Q_1 OFF is the normal stable state of the circuit.

- (10)
- The positive triggering pulse is to be applied to the base of Q_1 through Capacitor C_2 .
- It must be noted that the triggering is unsymmetrical and is to be applied to one transistor only and not to both simultaneously.
- When a positive trigger of sufficient magnitude and duration is applied to the base of Q_1 , the transistor Q_1 starts conducting.
- Due to this, voltage at its Collector V_{C1} decreases.
- This is coupled to base of Q_2 through C .
- But voltage across capacitor cannot change instantaneously.
- Hence decrease in V_{C1} directly cause a decrease in the base voltage of Q_2 . i.e., V_{B2} .
- The drop in voltage is about $I_1 R_C$. This decreases the forward bias of Q_2 and hence collector current I_2 decreases.
- Thus the collector voltage of Q_2 increases which is applied to the base of Q_1 , through R_1 .
- This further increases the base potential of Q_1 , if Q_1 is quickly driven in saturation and at the same time, the transistor Q_2 gets driven to

Q7

initially

Cutoff.

- This is quasi-stable of the circuit.
- The circuit will remain in this quasi-stable state which for only a finite time T .
- In the quasi-stable state, the capacitor C starts charging through the path V_{CC} , R and ON transistor Q_1 .
- As it starts charging towards V_{CC} , the base of Q_2 experiences rise in voltage.
- When this voltage becomes more than cut-in voltage V_T of Q_2 , the Q_2 starts conducting. And due to the regenerative action, Q_1 is turned OFF.
- Then the circuit returns back to its stable state.


Pulse width of collector coupled Monostable Multivibrator =
The pulse width of the time for which the circuit remains in the quasi-stable state. It is also called gate width and denoted by T .

Derivation of Pulse width

To derive its expression, consider the voltage variation at base of Q_2 .

11

Initially Q_2 is in saturation and hence $V_{B2} = V_{BE(Sat)} = V_T$, which is about 0.8V for silicon transistor. When the pulse is applied at $t=0^+$, then at $t=0^+$, as Capacitor voltage cannot change instantaneously, the voltage V_{B2} decreases by $I_c R_C$. Then Capacitor charges exponentially hence V_{B2} also increases exponentially, whose final value at $t \rightarrow \infty$ is V_{CC} . But when V_{B2} becomes equal to V_T then Q_2 starts conducting and circuit comes back to stable state. This by the time T at which transition occurs. The graph of V_{B2} against time.

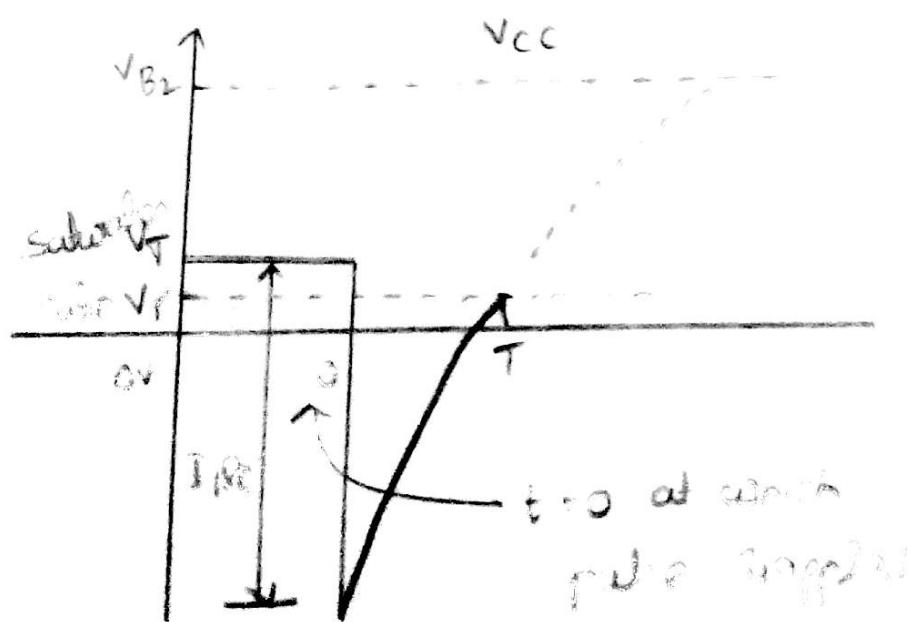

V_{B2} Vs t graph

To write equation for exponential charging of this capacitor we can write,

$$t=0^+, \quad v_i = V_T - I_1 R_C.$$

$$t=\infty, \quad v_f = V_{CC}$$

$$v_c = v_f - (v_i - v_f) e^{-t/\tau}$$

where

τ = Time constant

$$\therefore v_{B2} = V_{CC} - (V_{CC} - V_T + I_1 R_C) e^{-t/\tau} \rightarrow \textcircled{1}$$

$$\text{at } t=T, \quad v_{B2} = V_T \rightarrow \textcircled{2}$$

Substituting $\textcircled{2}$ into $\textcircled{1}$ & solving for T we get

$$T = \tau \ln \left[\frac{V_{CC} + I_1 R_C - V_T}{V_{CC} - V_T} \right] \rightarrow \textcircled{3}$$

where $V_T = 0.3V$ for germanium

$\Rightarrow 0.8V$ for silicon.

When Q_1 is in saturation under quasi-stable state

we can write,

$$v_{C1} = v_{CE(\text{sat})} \rightarrow \textcircled{4}$$

$$\therefore I_1 R_C = V_{CC} - v_{CE(\text{sat})} \rightarrow \textcircled{5}$$

Substituting in $\textcircled{3}$.

$$T = \tau \ln \left[\frac{V_{CC} + V_{CC} - v_{CE(\text{sat})} - v_{CE(\text{sat})}}{V_{CC} - V_T} \right] \rightarrow \textcircled{6}$$

This is before, $v_T = v_{BE}(\text{sat})$

$$T = \gamma \ln \left[\frac{2v_{CC} - v_{CE}(\text{sat}) - v_{BE}(\text{sat})}{v_{CC} - v_r} \right] \rightarrow ⑦$$

$$T = \gamma \ln \left[\frac{2 \left[v_{CC} - \left(\frac{v_{CE}(\text{sat}) + v_{BE}(\text{sat})}{2} \right) \right]}{v_{CE} - v_r} \right] \rightarrow ⑧$$

$$T = \gamma \ln(2) + \gamma \ln \left[\frac{v_{CC} - \left(\frac{v_{CE}(\text{sat}) + v_{BE}(\text{sat})}{2} \right)}{v_{CC} - v_r} \right] \rightarrow ⑨$$

At room temperature,

$$v_{CE}(\text{sat}) + v_{BE}(\text{sat}) \approx 2v_r$$

Substituting in eqn ⑨

$$T = \gamma \ln(2) + \gamma \ln(1)$$

$$\gamma \Rightarrow \gamma \ln(2) \rightarrow ⑩$$

The time constant γ for the charging path of

$$\text{Capacitor } C \quad \gamma = \frac{RC}{RC} \rightarrow ⑪$$

$$\gamma = 0.69 RC \rightarrow ⑫$$

Thus the gate width is dependent depends on temperature, on $V_{BE}(\text{Sat})$, $V_{CE}(\text{Sat})$ and V_s depend on the temperature.

One remedy for this temperature effect is to connect R not to V_{CE} but to source whose value decreases as the temperature decreases, thus compensating the effect of temperature.

Wave shapes of Monostable Multivibrator.

To obtain the waveform, let us assume that the external pulse is applied at $t=0$ & reverse transition from quasi-stable state occurs at $t=T$.

The stable state:-

The transistor Q_1 is OFF and Q_2 is ON in the stable state. The stable state currents and voltages can be obtained as shown earlier for bistable multivibrator circuit. The Q_2 is in saturation hence for Q_2 ,

$$\sqrt{P_2} = V_{BE}(\text{Sat}) = \sqrt{T} \quad \rightarrow (14)$$

$$\sqrt{C_2} = V_{CA}(\text{Sat}) \quad \rightarrow (15)$$

13

The Q_1 is OFF hence as current is zero we can write,

$$V_{C_1} = V_{CC} \rightarrow (16)$$

The base voltage of Q_1 can be obtained by superposition principle as shown by equation (2) in Ques (ii) ~~eqn~~

$$V_{B_1} = \left| \frac{-V_{BB}R_1}{R_1 + R_2} \right|_{V_{C_2}=0} + \left| \frac{V_{C_2}R_2}{R_1 + R_2} \right|_{V_{BB}=0} \approx V_f \rightarrow (17)$$

To have Q_1 OFF, $|V_f| \leq 0.1\text{V}$ for germanium transistor.


The quasi-stable state:- When pulse is applied at $t=0$ Q_2 becomes OFF and Q_1 becomes ON. The voltages at V_{C_1} & V_{B_2} drop instantaneously by the amount $I_1 R_C$ where I_1 is current drawn by Q_1 when it starts conducting. Then, Q_1 gets driven into saturation hence,

$$V_{B_1} = V_T \rightarrow (18)$$

$$V_{C_1} = V_{CE(\text{sat})} \rightarrow (19)$$

$$\therefore I_1 R_C = V_{CC} - V_{CE(\text{sat})} \rightarrow (20)$$

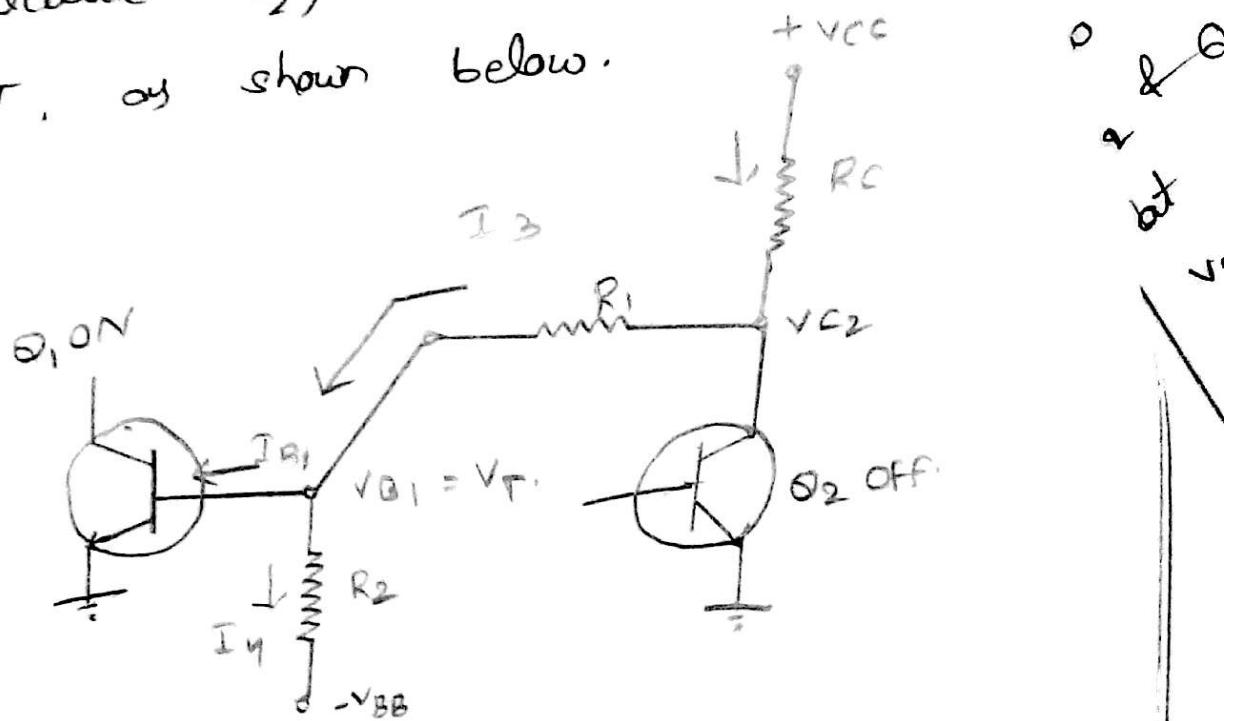To calculate V_{C_2} , consider the equivalent circuit to V_{CC} this Oct LT, as shown below.



By using the superposition principle we can write,

$$V_{C_2} = \frac{V_{CC}R_1}{R_1+RC} \Big|_{V_B=0} + \frac{V_f R_C}{R_1+RC} \Big|_{V_{CC}=0} \rightarrow ②$$

As capacity starts charging, the voltage at base of Q_2 rises exponentially as discussed earlier, towards V_{CC} . This continues till V_{B_2} becomes equal to cut-in voltage V_f at $t = T$.

Waveforms for $t \geq T$: At $t = T$, reverse transition occurs. Thus Q_1 is cutoff and Q_2 starts conducting at $t = T$. They V_{C_2} drops instantly to $V_{CE(sat)}$ & V_{B_1} returns to V_f . The voltage V_{C_1} rises abruptly as Q_1 becomes off. This rise is such that V_C becomes almost equal

5

14

 V_{CC}

With this sudden increase in V_C , it is applied to base of Q_2 & Q_2 suddenly gets driven into saturation. Hence at $t = T^+$ an overshoot occurs at base of Q_2 in V_{B2} . This overshoot decreases exponentially as the Capacitor C recharges back of base current.

Magnitude of the overshoot in V_{B2} :

The equivalent circuit at $t = T^+$ is shown in below figure. In the circuit, the input circuit of Q_2 is replaced by base spreading resistance r'_{bb} in series with base saturation voltage V_T .

The base current at $t = T^+$ is denoted as I_B' while current through R is neglected as $R \gg R_C$.

$$V_{B2}' = I_B' r'_{bb} + V_T \rightarrow 22$$

$$V_{C1} = V_C - I_B' R_C \rightarrow 23$$


Thus the overshoot at $t = T^+$ in the V_{CC} voltage V_{B2}' is now can be.

denoted as δ and is given by,

$$\delta = V_{B2}' - V_T = \text{Overshoot}$$

$$\therefore \delta = I_B' r'_{bb} + V_T - V_T \rightarrow 24$$

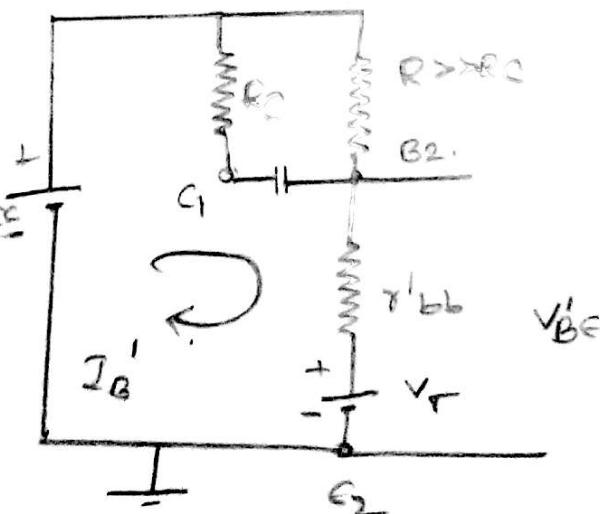While the overshoot in the collector voltage of Q_1 i.e., in V_C ,



is denoted as δ' and given by,

$$\delta' = v_C - v_{CE}(\text{sat})$$

$$\delta' = v_{CC} - I_B' R_C - v_{CE}(\text{sat}) \rightarrow 25$$

But the voltage v_C is applied to base of Q_2 .

Equating δ' $\&$ 24 & 25 we get

$$I_B' r'_{bb} + V_T - V_Y = v_{CC} - I_B' R_C - v_{CE}(\text{sat})$$

$$\therefore I_B'(R_C + r'_{bb}) = v_{CC} - v_{CE}(\text{sat}) - V_T + V_Y$$

$$I_B' = \frac{v_{CC} - v_{CE}(\text{sat}) - V_T + V_Y}{R_C + r'_{bb}} \rightarrow 26$$

After $t = T^+$, the v_{B2} decreases exponentially to its steady state value V_T . The time constant with which it decays is given by.

$$\tau' = (R_C + r'_{bb}) C \rightarrow 27$$


Note that if v_{CC} is large compared with the junction voltages, then

$$\therefore I_B' \approx \frac{V_T}{R_C} \text{ if } v_{CC} \text{ is large.} \rightarrow 28$$


Similar to overshoot in v_C & v_{B2} , there exists an undershoot in v_{C2} and v_{B1} at $t = T^+$ but these undershoots are very small & hence usually neglected & not shown in waveforms.

The complete waveforms considering above discussion are shown in


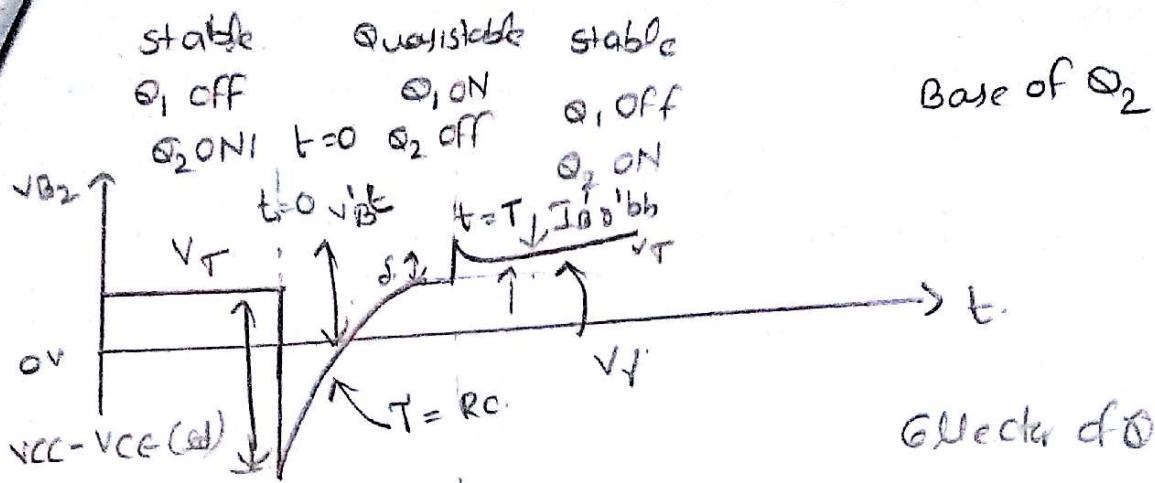
waveforms of collector coupled monostable multivibrator



Collector of Q_1

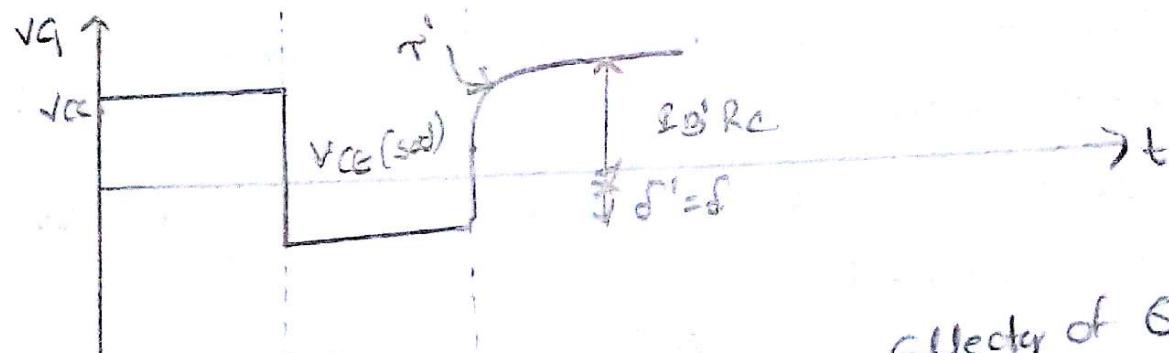

Collector of Q_2

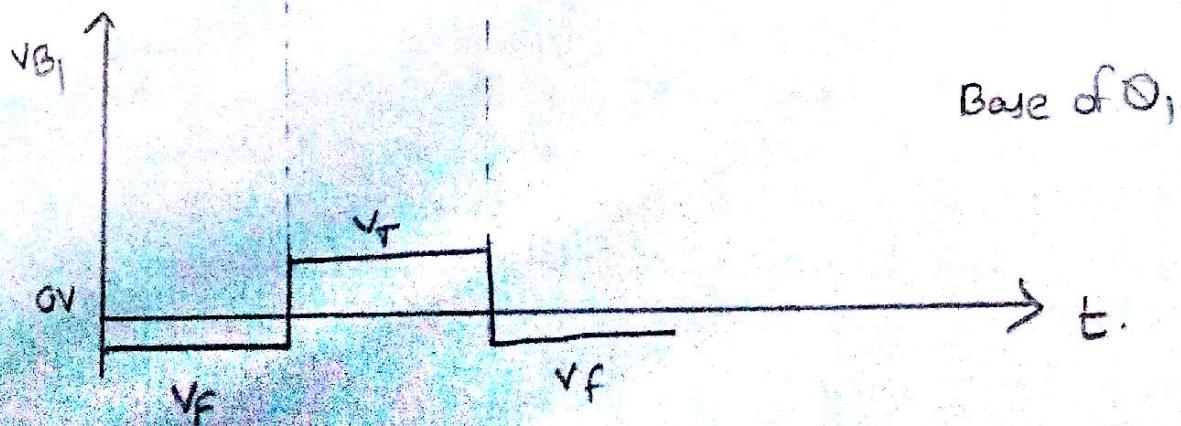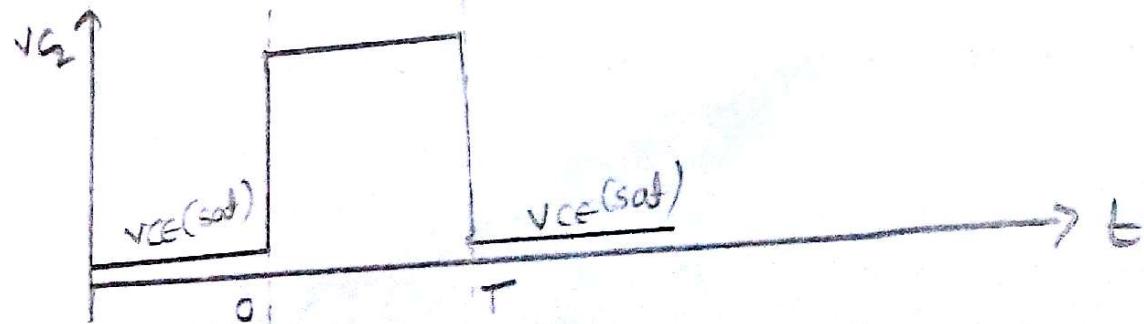

Base of Q_1

The typical npn transistor junction voltages at 25°C are given here. The table may be referred if the voltages are not given in problem. All the voltages are in volts.

	$V_{CE}(\text{sat})$	$V_{BE}(\text{sat}) = V_T$	$V_{BE}(\text{active})$	$V_{BE}(\text{cutin}) = V_T$	$V_{CE}(\text{cutoff})$
Si	0.3	0.7	0.6	0.5	0.0
Ge	0.1	0.3	0.2	0.1	-0.1


Applications

- Used to produce rectangular waveform & hence can be used as gating circuit.
- Used to introduce time delays as gate width is adjustable
- Used to generate uniform width pulses from a variable width input pulse train.

Transformer Coupled class A Amplifier:-

- * For maximum power transfer to the load, the impedance matching is necessary.
- * For loads like loudspeaker, having two impedance values, impedance matching is difficult using directly coupled amplifiers circuit.
- * This is because loudspeaker resistance is in the range of 3 to 4 ohms to 16 ohms while the output impedance of series fed directly coupled class A amplifier is very much high.
- * This problem can be eliminated by using transformer to deliver power to the load. The transformer is called an output transformer, and amplifier is called transformer coupled class A amplifier.

Properties of transformer:-

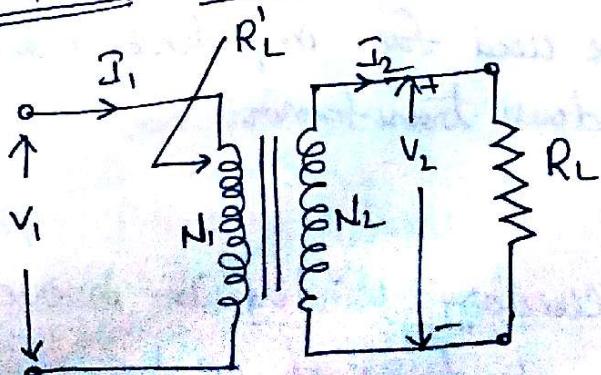

- * Consider a transformer as shown in the fig. which is connected to a load resistance R_L .
- * While analysing transformer, it is assumed that the transformer is ideal and there are no losses in transformer. Similarly the winding resistances are assumed to be zero.

N_1 = Number of turns on primary

N_2 = Number of turns on secondary

V_1 = Voltage applied to primary

V_2 = Voltage on secondary

I_2 = Primary Current.

10
Videne
As
Sel
U

1) Turns ratio:

The ratio of no. of turns on secondary to the no. of turns on primary is called turns ratio and is denoted by n .

$$n = \frac{N_2}{N_1}$$

* Sometimes it is specified as $\frac{N_2}{N_1} : 1$ (or) $\frac{N_1}{N_2} : 1$

2) Voltage transformation:

The transformer transforms the voltage applied on one side to other side proportional to turns ratio. The transformer can be step up or step down transformer.

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$

In amplifier analysis, load impedance is going to be small. And the transformer is to be used for impedance matching. Hence it has to be a step down transformer.

3) Current transformation:

The current in the secondary winding is inversely proportional to the number of turns of windings.

$$\frac{I_2}{I_1} = \frac{N_1}{N_2} = \frac{1}{n}$$

(10) Impedance transformation!

As current and voltage get transformed from primary to secondary, an impedance seen from either side also changes. The impedance of the load on secondary is R_L .

(11)

$$R_L = \frac{V_2}{I_2} \text{ and } R_L = \frac{V_1}{I_1}$$

$$V_1 = \frac{N_1}{N_2} V_2 \quad \text{and} \quad \frac{I_1}{I_2} = \frac{N_2}{N_1}$$

$$I_1 = \frac{N_2}{N_1} I_2$$

$$R_L' = \frac{\frac{N_1}{N_2} V_2}{\frac{N_2}{N_1} I_2} = \left[\frac{N_1}{N_2} \right]^2 \times \frac{V_2}{I_2}$$

$$\boxed{R_L' = \frac{R_L}{n^2}}$$

The R_L' is reflected impedance.

problem

The load of 4Ω is connected to the secondary of a transformer having primary turns of 200 and secondary turns of 20. Calculate the reflected load impedance on primary.

solution Given that


$$R_L = 4\Omega \quad N_1 = 200 \quad N_2 = 20$$

$$n = \frac{N_2}{N_1} = \frac{20}{200} = 0.1$$

$$R_L' = \frac{R_L}{n^2} = \frac{4}{(0.1)^2} = 400\Omega$$

Circuit diagram of transformer Coupled Amplifier

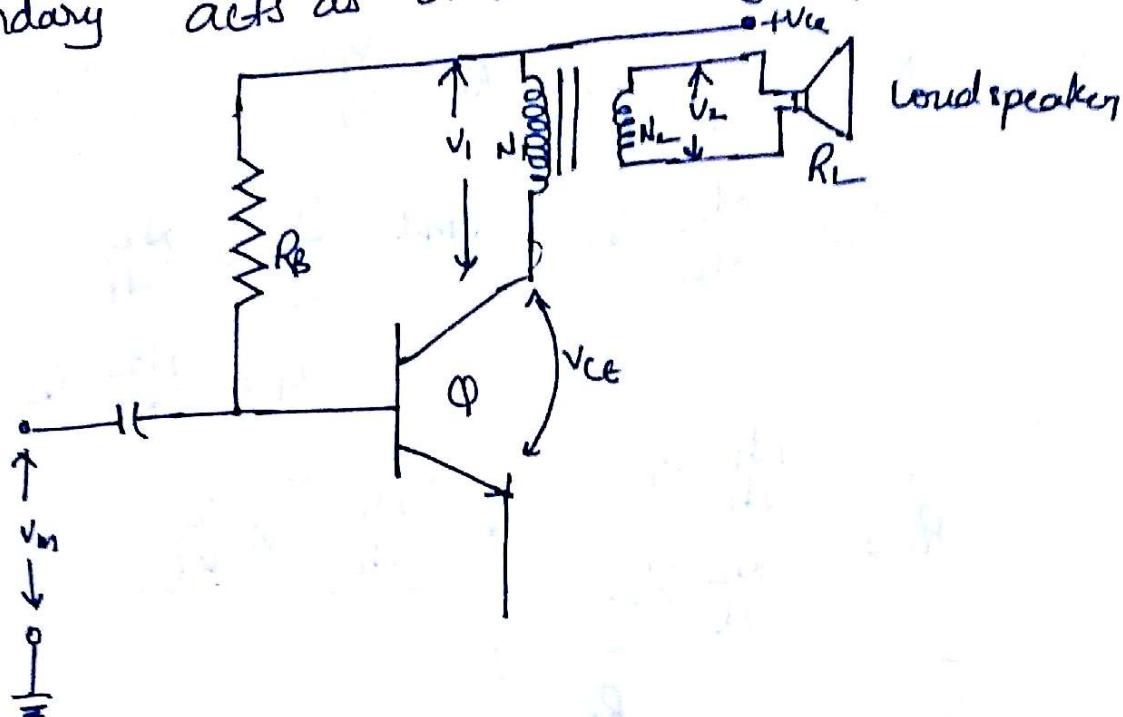The basic circuit of a transformer coupled amplifier shown in below fig. The loudspeaker connected to the fig. secondary acts as a load having impedance of R_L .



The transformer used is a step down transformer with turns ratio as $n = \frac{N_2}{N_1}$.

DC operation

- * It is assumed that winding resistances are zero. Hence for dc purposes the resistance is zero.
- * There is no voltage drop across the primary winding of the transformer.
- * The slope of the d-c load line is reciprocal of the d-c resistance in collector circuit, which is zero in this case.
- * Hence slope of d-c load line is ideally infinite. The d-c load line is vertically straight line.

Apply KVL at collector side

(13)

$$V_{CC} - V_{CE} = 0$$

$$V_{CC} = V_{CE}$$

This is dc bias voltage V_{CEQ} for the transistor

$$\therefore V_{CC} = V_{CEQ}$$

* The intersection of d-c load line and the base current set by the circuit is the Quiescent operating point. The d-c load line as shown in fig (1).

DC Power Input

The d-c power input is provided by supply voltage with no signal input. The dc current drawn is the collector bias current I_{CQ} .

$$P_{DC} = V_{CC} I_{CQ}$$

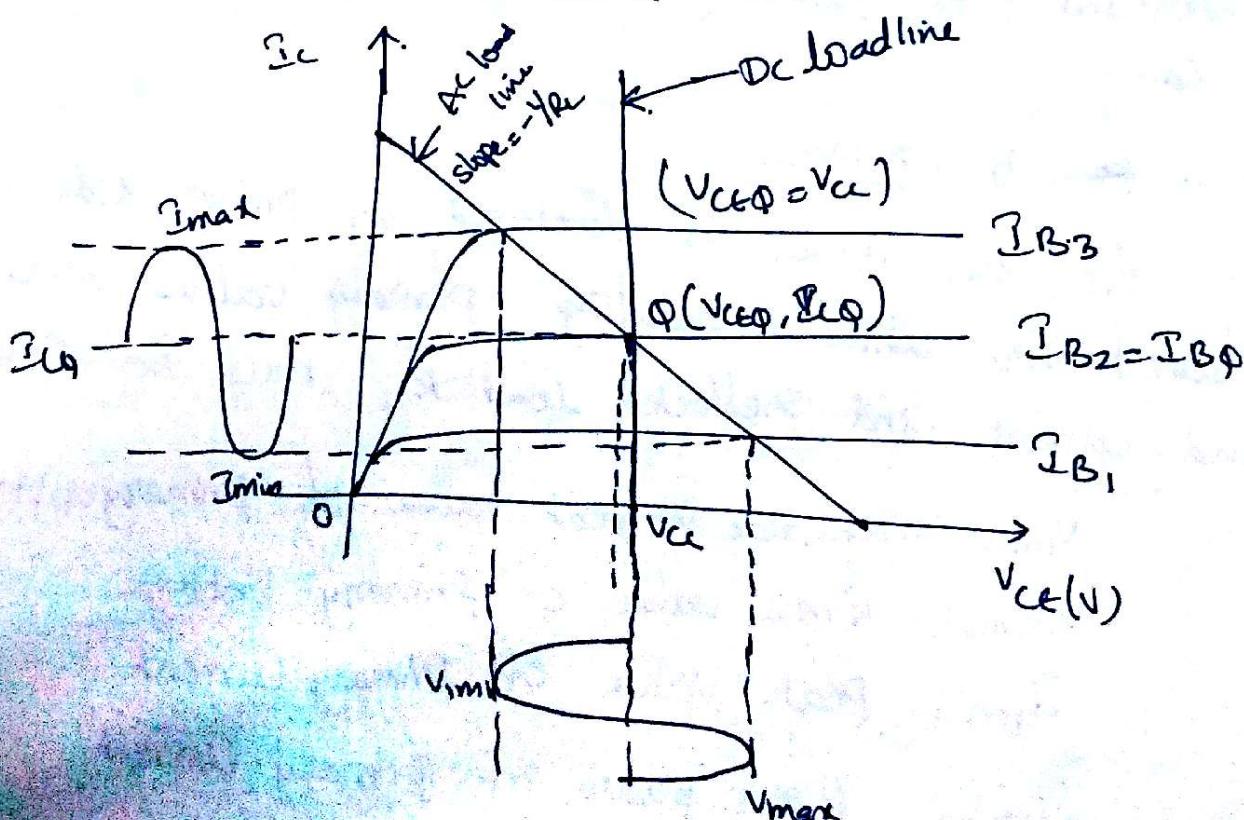


Fig (1).

power developed on primary

$$P_{ac} = V_{1rms} I_{1rms}$$

$$P_{ac} = I_{1rms}^2 R_L' \quad [\because V = IR \\ V_{1rms} = I_{1rms} R_L]$$

$$= \frac{V_{1rms}^2}{R_L'}$$

$$\boxed{P_{ac} = \frac{V_{1m} I_{1m}}{2} = \frac{I_{1m}^2 R_L'}{2} = \frac{V_{1m}^2}{2 R_L'}}$$

a.c power developed on secondary

$$P_{ac} = V_{2rms} I_{2rms} = I_{2rms}^2 R_L = \frac{V_{2rms}^2}{R_L}$$

$$\boxed{P_{ac} = \frac{V_{2m} I_{2m}}{2} = \frac{I_{2m}^2 R_L}{2} = \frac{V_{2m}^2}{2 R_L}}$$

- * power delivered on primary is same as power delivered to the load on secondary assuming ideal transformer.
- * for practical circuit, the transformer can not be ideal. Hence power delivered to load is slightly less than primary.

In class A amplifier


$$P_{ac} = \frac{(V_{max} - V_{min})(I_{max} - I_{min})}{8}$$

Efficiency!

$$\gamma \cdot \eta = \frac{P_{ac}}{P_{dc}} \times 100 = \frac{(V_{max} - V_{min})(I_{max} - I_{min})}{8 I_{CQ} V_{CC}} \times 100$$

maximum Efficiency

16

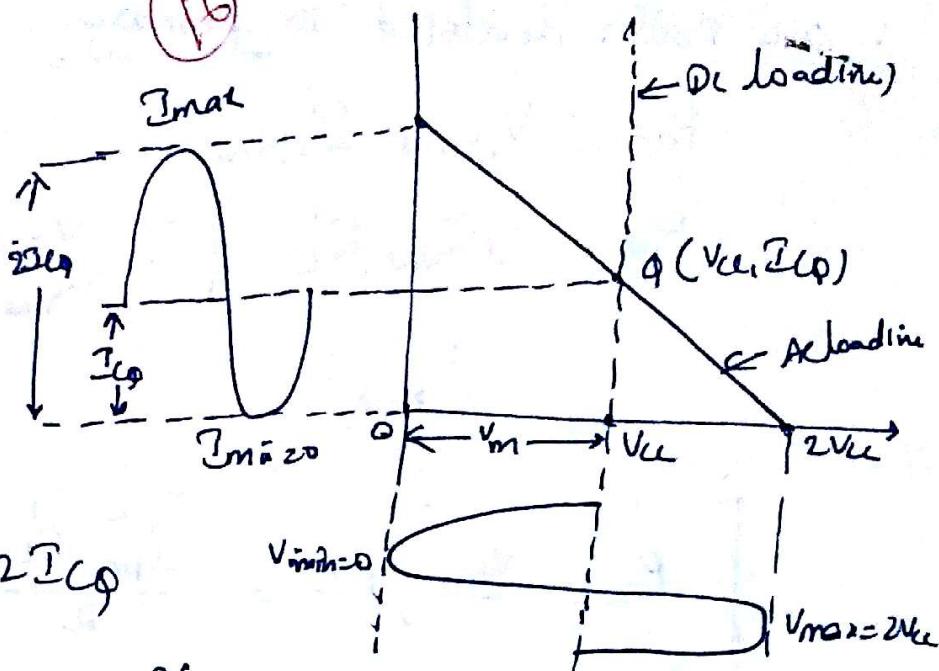

$$V_{m\min} = 0$$

$$V_{m\max} = 2V_{cc}$$

$$I_{m\min} = 0 \quad I_{m\max} = 2I_{CQ}$$

$$\text{Efficiency} = \frac{(2V_{cc} - 0)(2I_{CQ} + 0)}{8V_{ce}I_{CQ}} \times 100$$

$$= \frac{4V_{ce}I_{CQ}}{8V_{cc}I_{CQ}} \times 100$$

$$= 50\%$$

Power dissipation

Power dissipation is the difference between a-c power output and the d-c power input

$$P_d = P_{dc} - P_{ac}$$

Advantages

- 1) The efficiency of operation is higher than directly Coupled amplifier.
- 2) The impedance matching required for maximum power transfer is possible.

Disadvantages

- 3) Due to transformer, the circuit becomes bulkier, heavier and costlier compared to directly Coupled circuit
- 4) The response frequency of circuit is poor.


(17)

①

Class B Amplifier:

Class 'B' Amplifier:

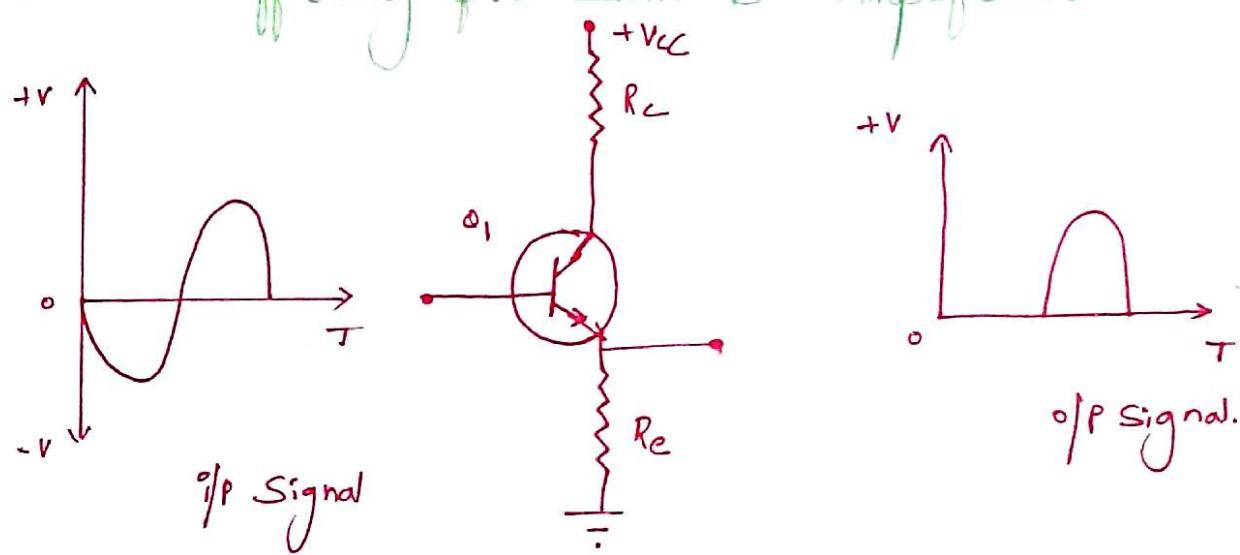Class B amplifier is a type of amplifier where the active device - transistor can conduct only for half cycle of the input signals - the conduction angle is 180° for a class B amplifier. The Quiescent point is fixed at zero (cutoff), hence it dissipates less power and efficiency is improved. The maximum efficiency of a class B amplifier is $\sim 78.5\%$




Advantages of class 'B' over class A

- In class B output has great power
- Efficiency is high
- negligible power loss at no o/p signal

(18)

Efficiency:

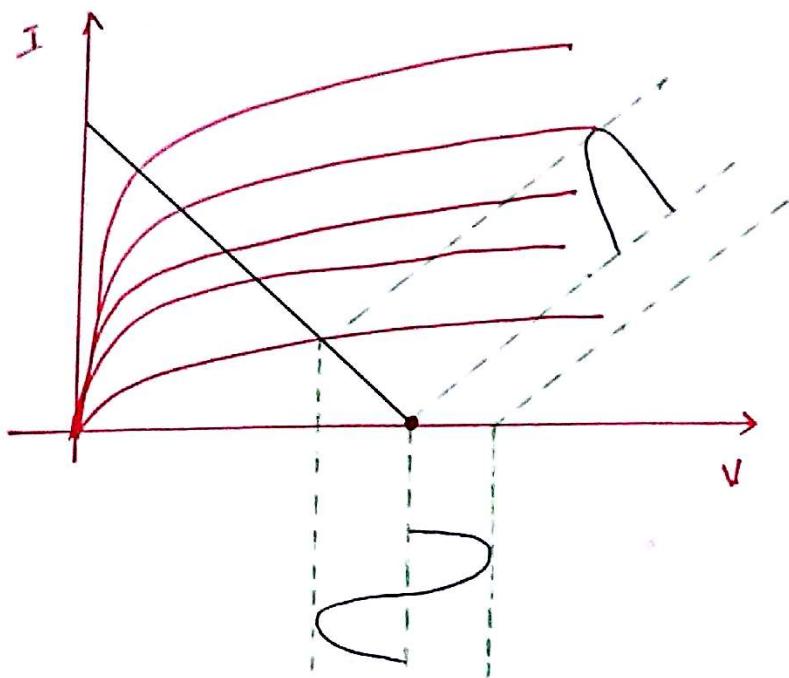

The effective load Resistance is $R_L = \left(\frac{N_1}{N_2}\right)^2 R_L$

N_1 → No. of primary turns

N_2 → No. of Secondary turns

for class B - the dissipation at collector is zero in Quiescent State and increases with excitation.

Advantages of class B - Amplifier:

→ High Efficiency when compared to the class A configuration

→ push-pull mechanism avoids even harmonics

→ No DC components in the o/p

(B)



②

Advantages of Class 'B' Amplifiers:

- The major disadvantage is cross-over distortion.
- Coupling transformer increases cost & size.
- It is difficult to find ideal transformer.
- Transformer coupling is not practical in case of huge load.

Cross-over distortion:

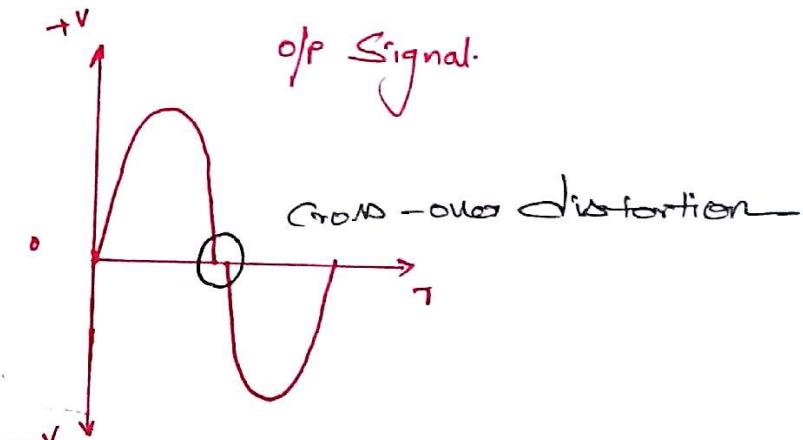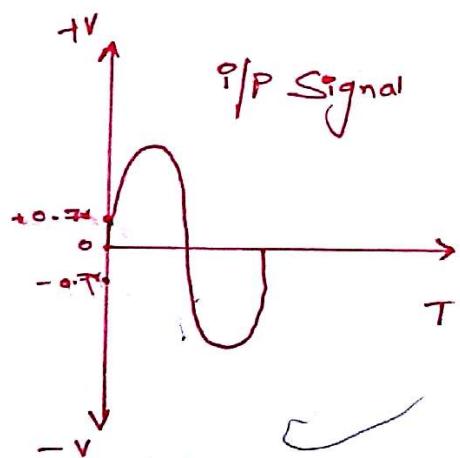
Since the active elements start conduction only after the input signal amplitude has risen above $0.7V$, the regions of the input signal where the amplitude is less than $0.7V$ will be missing in output signal & it is called as cross over distortion. The schematic representation is shown below:



$$\int f_a^a$$

(29)

Push-Pull class 'B' Amplifier:

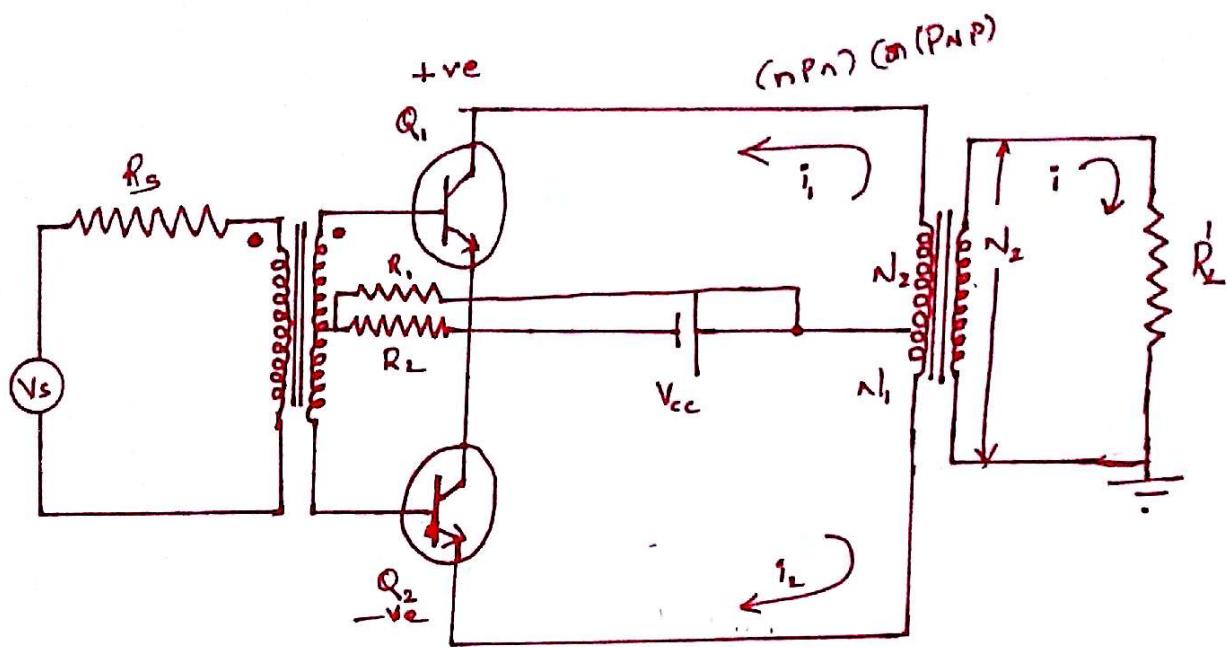


In Class B Amplifier - the c/p will be half of the Input Signal to obtain full wave - for we use push-pull class B Amplifier . It consists of two transistors Q_1 & Q_2 and full Center-tapped transistor one as Q.P. Transformer known as driver transformer one to Resistance load at the c.p. An V_{cc} Source is attached to the transistor in order to avoid the mismatching of transistor. The transistors may be NPN (Q1) PNP - transistor. The polarities on the transformer will be equal hence there is no phase shift. If the polarities are changed then a phase shift will occur.

(3)

(21)

Block diagram:

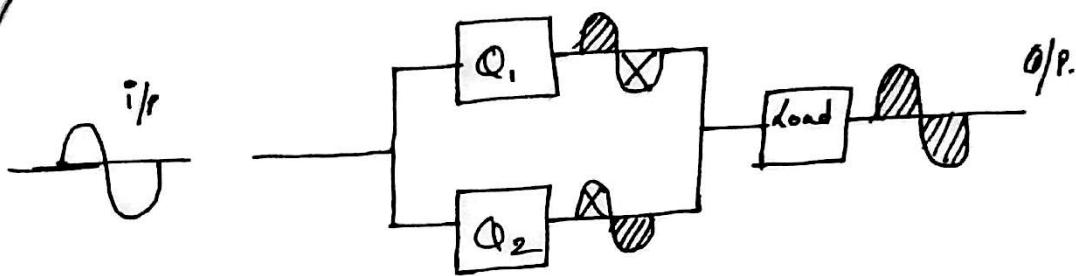

dc operation:

Each transistor acts as a half-wave rectifier.

If I_m is the peak current of the c/f then average value is $\frac{I_m}{\pi}$

$$\therefore I_{dc} = \frac{I_m}{\pi} + \frac{I_m}{\pi} = \frac{2I_m}{\pi}$$

The dc power is

$$\begin{aligned} P_{dc} &= V_{cc} \times I_{dc} \\ &= \frac{2}{\pi} V_{cc} \times I_m \end{aligned}$$

Ac operation:

When Ac signal is applied to driver-transistor


to Q_1 & connecting Q_1 & Q_2 to the load

$$R'_L = R_L/n^2$$

where $n = n_b/n_s$ the slope of the graph will be $-1/R'_L$

(22)

O/P wave form:

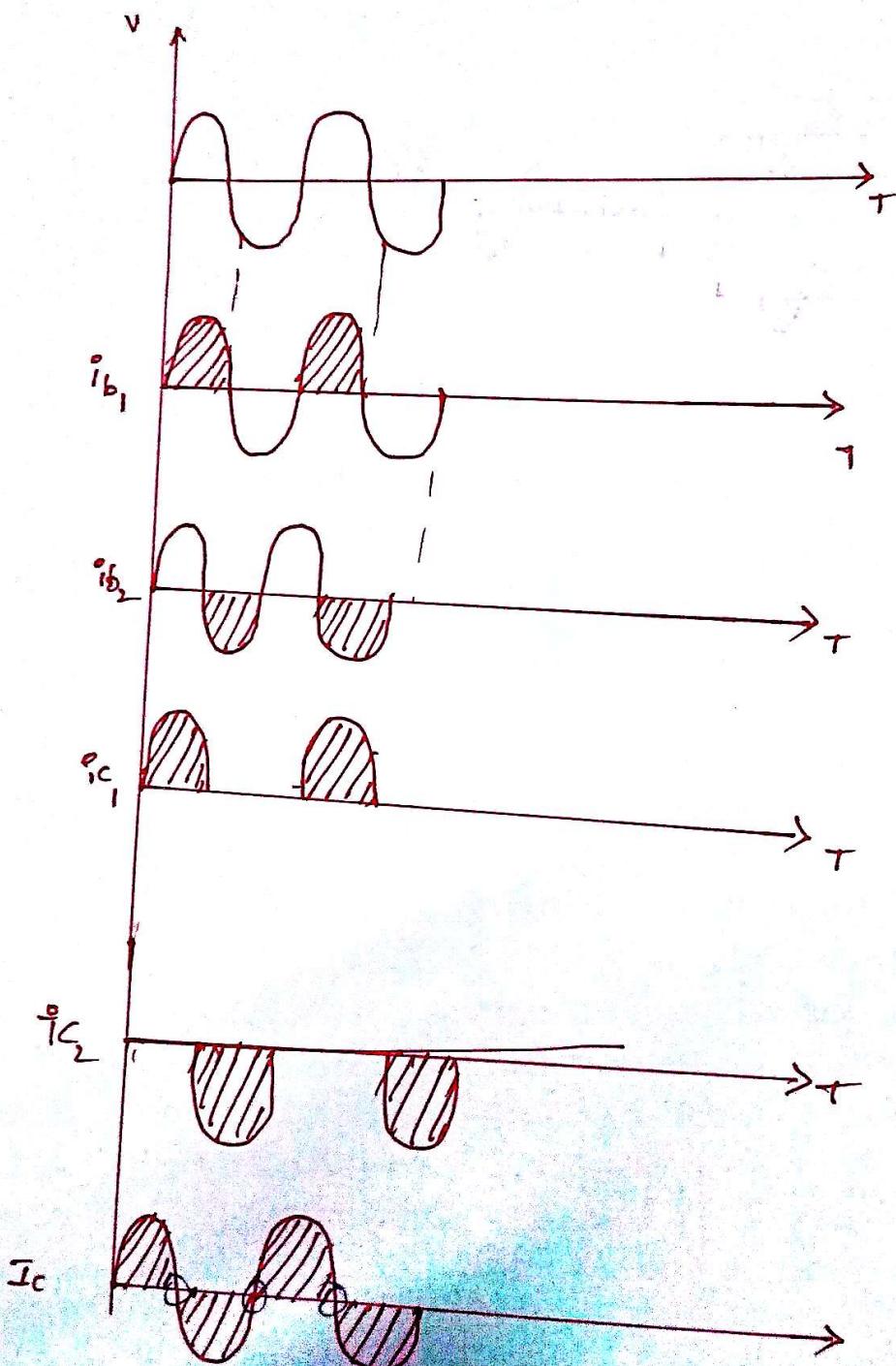

~~Dy~~



(4)

(23)

According to ohms law

$$V = IR$$

Slope in term of R_L

$$\frac{1}{R_L} = \frac{V_m}{I_m}$$

Ac power output:
we know that

$$V_{rms} = V_m / \sqrt{2} \quad (1)$$

$$I_{rms} = I_m / \sqrt{2} \quad (2)$$

$$P_{rms} \text{ (1)} P_{ac} = V_{rms} \cdot I_{rms} \\ = V_m I_m / 2$$

$$P_{ac} = V_m^2 / 2 R_L$$

Efficiency: %

$$\% \eta = \frac{P_{ac}}{P_{dc}} \times 100 \\ = \frac{V_m I_m}{\frac{2}{\pi} V_{dc} I_m} \times 100$$

$$= \frac{\pi}{4} \times 100 \times \frac{V_m}{V_{dc}}$$

($V_m = V_{dc}$)

$$= \frac{\pi}{4} \times 100$$

$$= -78.5 \%$$

(21)

Power dissipation:

It is equal to difference b/w output to dc power.

$$P_B = P_B - P_{ac}$$

$$= 2f_B V_{cc} I_m - V_m I_m / 2$$

$$= 2f_B V_{cc} - V_m / R_L' - \frac{V_m^2}{2R_L} = 0$$

by differentiating w.r.t. V_m

we get.

$$V_m = 2f_B V_{cc}$$

$$\text{Put } V_m \text{ in } 0$$

$$P_{ac(\max)} = 2f_B^2 \cdot \frac{V_{cc}^2}{R_L'}$$

For maximum efficiency $V_m = V_{cc}$

If D.C. $P_{ac(\max)}$ cannot be delivered simultaneously.

Power dissipated per transistor:

$$P_{ac} = V_m \cdot V_m / 2R_L = V_m^2 / 2R_L$$

$$(P_{ac})_{\max} = \frac{V_{cc}^2}{2R_L}$$

$$\frac{T_{ac(\max)}}{T} = \frac{2(P_{ac})_{\max}}{\pi^2}$$


$$\text{Now } P_{\max} = 2f_B^2 \frac{V_{cc}^2}{R_L}$$

$$= 4f_B^2 (P_{ac})_{\max}$$

(25)

(3)

Complementary Symmetry - Amplifier:

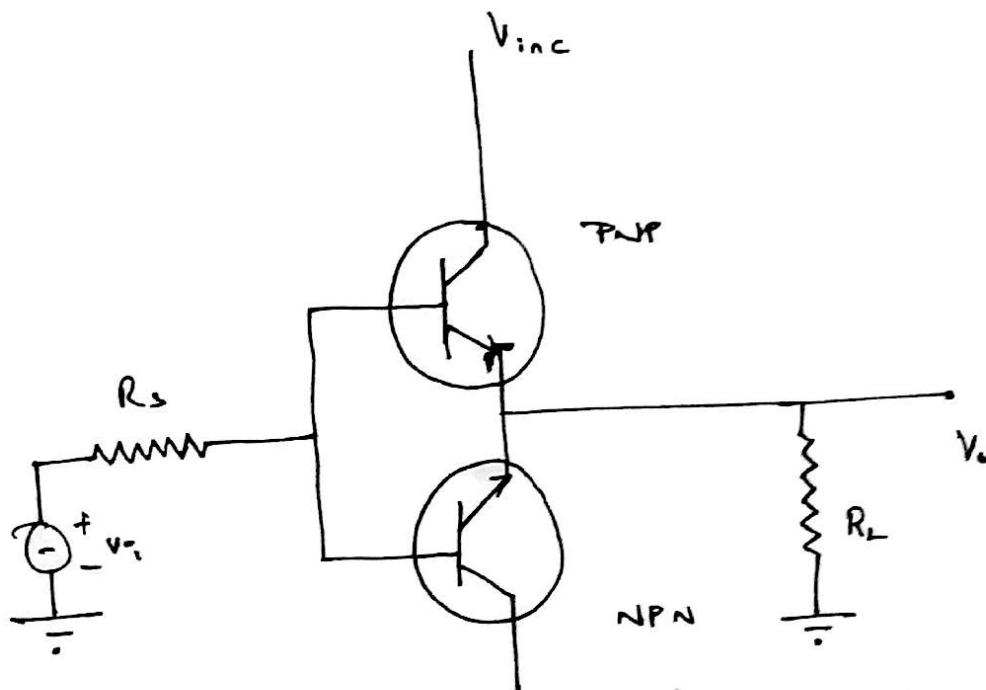

In Complementary Symmetry Amplifier there are two type of transistors are connected one is PNP & NPN transistors. Here no Centre-tapped transformer are connected when Voltage is Supplied Base Emitter of NPN-transistor is forward biased & PNP-transistor is reverse biased for the +ve half cycle. Then vice versa for negative half cycle.

Power Calculation:

$$P_{ac} = \frac{V_{cc}}{2} \cdot \frac{I_m}{R_L}$$

$$V_{cc} = R_L \cdot \frac{V_m}{2} \cdot I_m$$

$$T_{max} = \frac{V_m}{R_L} = V_{cc}/R_L$$

(29)

$$P_{ac} = \frac{V_{cc}^2}{R_L} V_{ac} I_m$$

$$= \frac{V_{cc}^2}{R_L} \times \frac{g_{\pi}}{2}$$

$$P_{ac} - P_a = 0.136 \frac{V_{ac}^2}{R_L}$$

Advantages:

- low cost
- Impedance matching is possible

Disadvantages:

- Two separate voltage supplies
- off is distorted → from over distortion

(27)

6

Q - Full Class B

Both should be PNP

(or) NPN

→ Transformer are used

→ Impedance matching is due to off - transformer

+ Frequency response is poor

→ Bulky, costly

→ Single Supply

→ Efficiency is higher than

Class A

Complementary Symmetry class B

→ One is PNP & other is NPN

→ No transformer is used.

→ Impedance matching is due to common collector configuration

+ Frequency response is improved

+ Bulky, not costly

+ Double Supply is needed

+ Efficiency is higher than Push-Pull Amplifier.

CLASS-B : PUSH PULL AMPLIFIER

B.Bhanusree

I^Y, ECE - A sec.

* class B :-

(Introduction :-)


To improve the full power efficiency of the previous class A amplifier by reducing the wasted power in the form of heat, it is possible to design the power amplifier circuit with two transistors in its output stage producing what is commonly termed as a class B Amplifier also known as a push pull amplifier configuration.

* Push-pull amplifiers use two "complementary" or matching transistors, one being an NPN-type and the other being a PNP-type with both power transistors receiving the same input signal together that is equal in magnitude, but in opposite phase to each other. This results in one transistor only amplifying one half or 180° of the input waveform cycle while the other transistor amplifies the other half or remaining 180° of the input waveform cycle with the resulting "two-halves" being put back together again at the output terminal.

* Then the conduction angle for this type of amplifier circuit is only 180° or 50% of the i/p signal. This pushing and pulling effect of the alternating half cycles by the transistors gives this type

of CKT, its amusing "push-pull" name, but generally known as the "class B Amplifier".

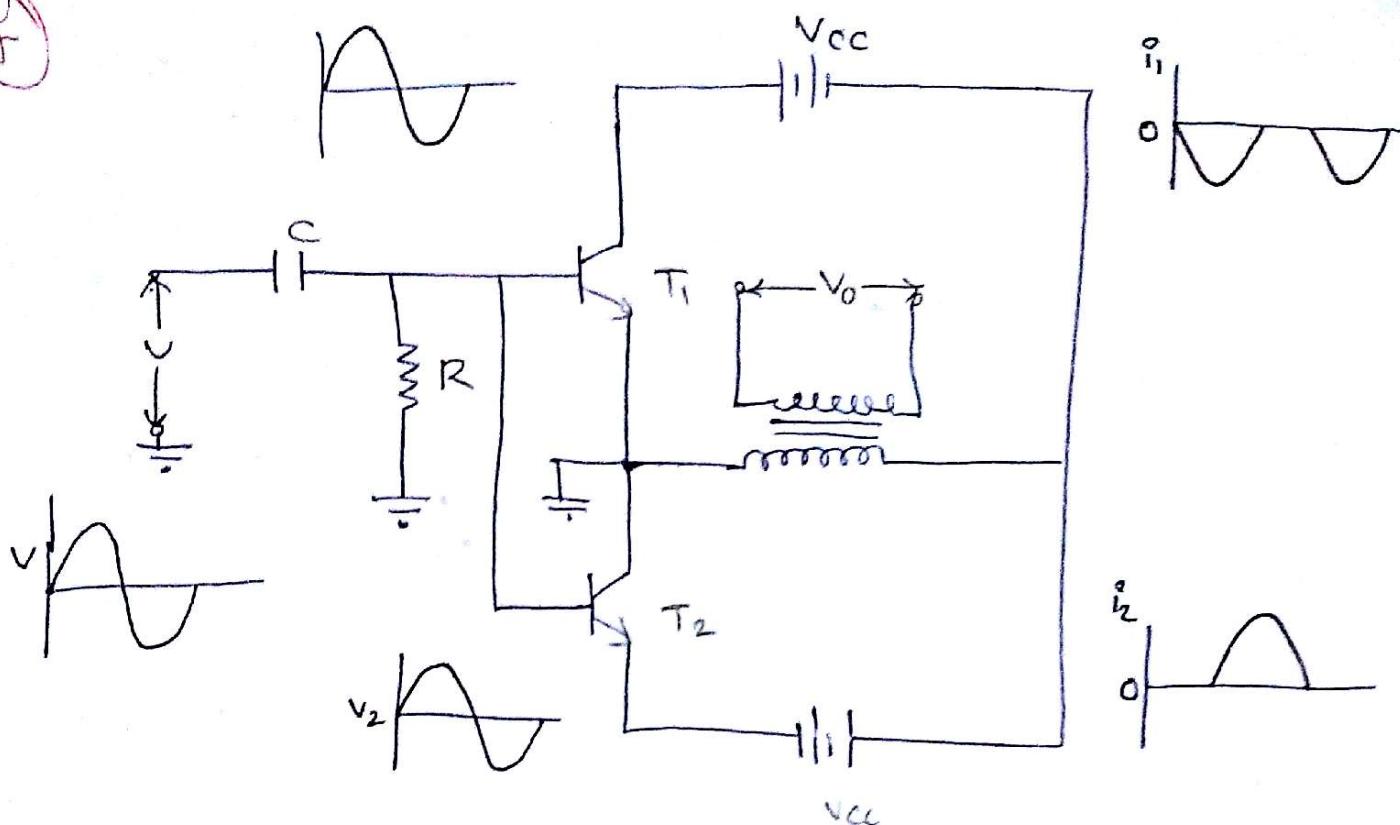Class B push pull Transformer ampr ckt :-



construction:-

- * It employs one NPN transistor (T_1)
- * It employs one PNP transistor (T_2)
- * Hence it is called as complementary push pull amplifier
- * It requires no centre tapped transformers.

Working:-

During positive half-cycle,

- * the NPN transistor (T_1) conducts and the PNP transistor (T_2) cut-off.
- * Thus collector current i_C flows through the primary side of the transformer.

(20)

negative half cycle.

→ NPN transistor (T1) conducts and the PNP transistors (T2) remains off.

Thus the collector current flows through the primary side of the transformer.

→ In this way NPN transistor amplifies the positive half cycle of the input signal.

→ The PNP transistor amplifies the negative half cycle of the input signal.

→ An output transformer is used for impedance matching.


Advantages :-

- * High AC output power is obtained.
- * This circuit does not require centre tapped transformers.
- * Less weight.
- * Low cost.

Disadvantages :-

- * It is difficult to get a pair of transistors that have similar characteristics.
- * This ckt requires two power supplies
 +Vcc for NPN
 -Vcc for PNP
- * Cross-coupling distortion occurs in the output wave form.

Output characteristics:

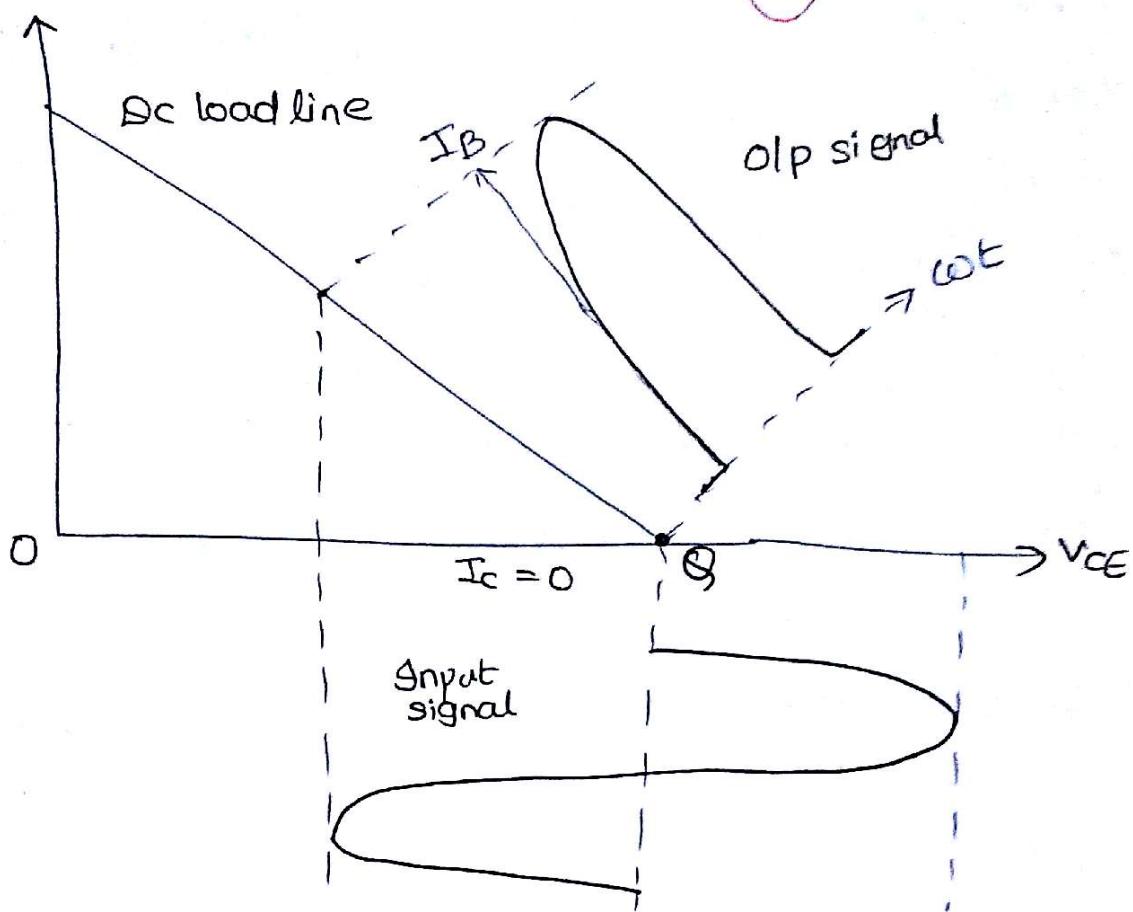


Class B Amps operation has zero DC bias as the transistors are biased at the cut off, so each transistor only conducts when the i/p signal is greater than the base emitter voltage.

∴ At zero i/p I_{CQ} is zero o/p and no power is being consumed. This then means that the actual Q-point of a Class B amp is on the Vce part of the load line as shown in graph.

Class C Amplifiers:

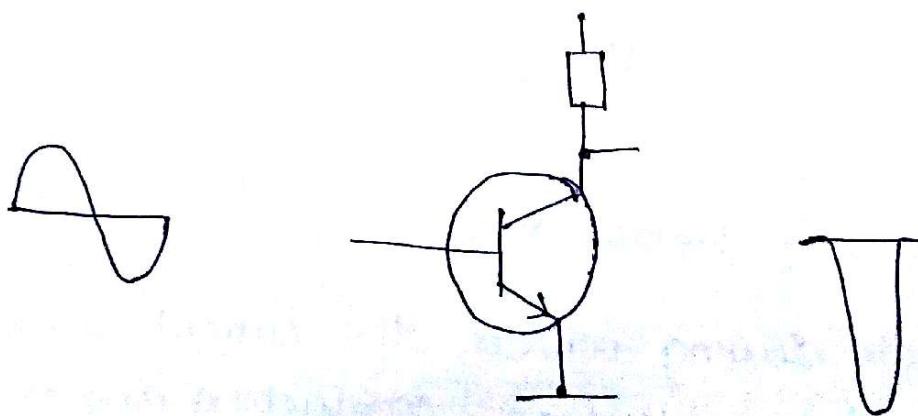(32)

- * Only half of the i/p signal is given, i.e. class C amplifiers conduct less than 50% of i/p signal.
- * Distortion at o/p is high
- * It has higher efficiencies i.e. 90%. when compared to Class A and Class B.
- * Applications:
 - RF transmitters.
 - Megaphones.
- * I/P signal is used to roughly switch the amplifying device on and off, which causes pulses of current to flow through a tuned circuit.




Definition:

A amplifier is said to be class C; if the o/p point and i/p signal selected such that o/p signal is obtained for less than half cycle, for a full i/p cycle.

* Due to selection of α point, only transistor remains active, for less than half cycle, so only that part is reproduced at o/p.

* for remaining part of i/p signal transistor is cut and no signal is produced at o/p.

Waveform of class C

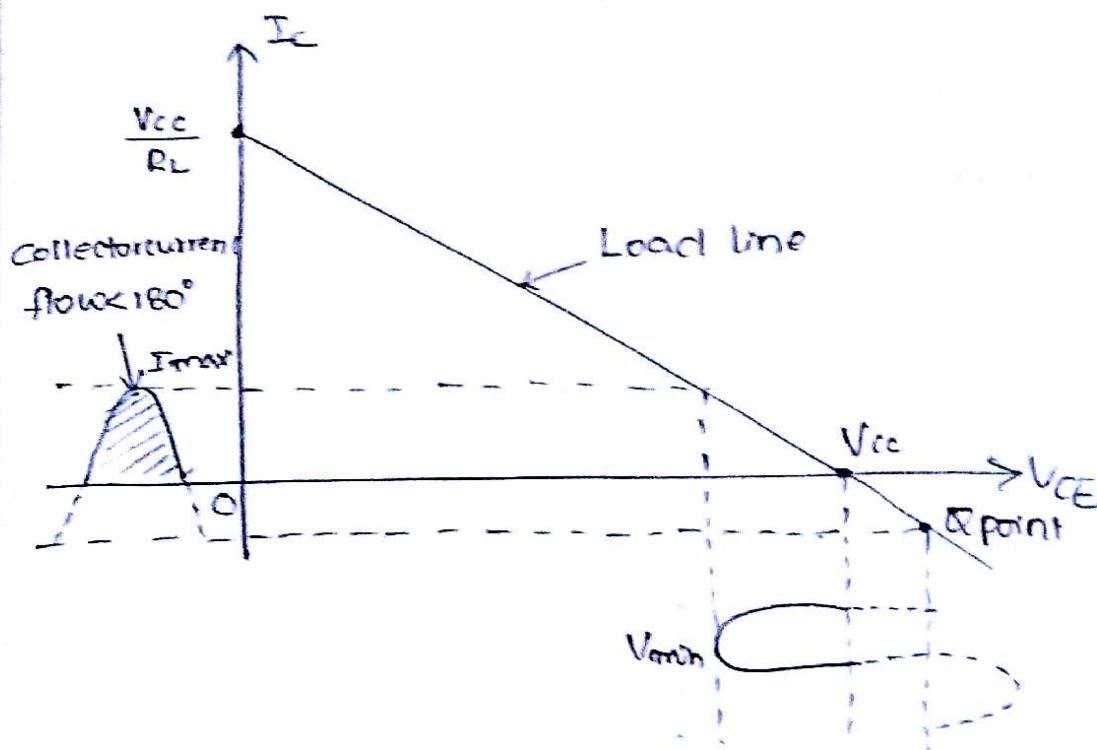


* Here Q point lies below X-axis.

* The total angle during which the current flows is less than 180° . So it called as conducting angle. (θ_c)

→ In class-C, π el resonant circuit acts as a load impedance.

→ Since collector current flows for less than half cycle, it consists of series of pulses with harmonics of i/p signal.

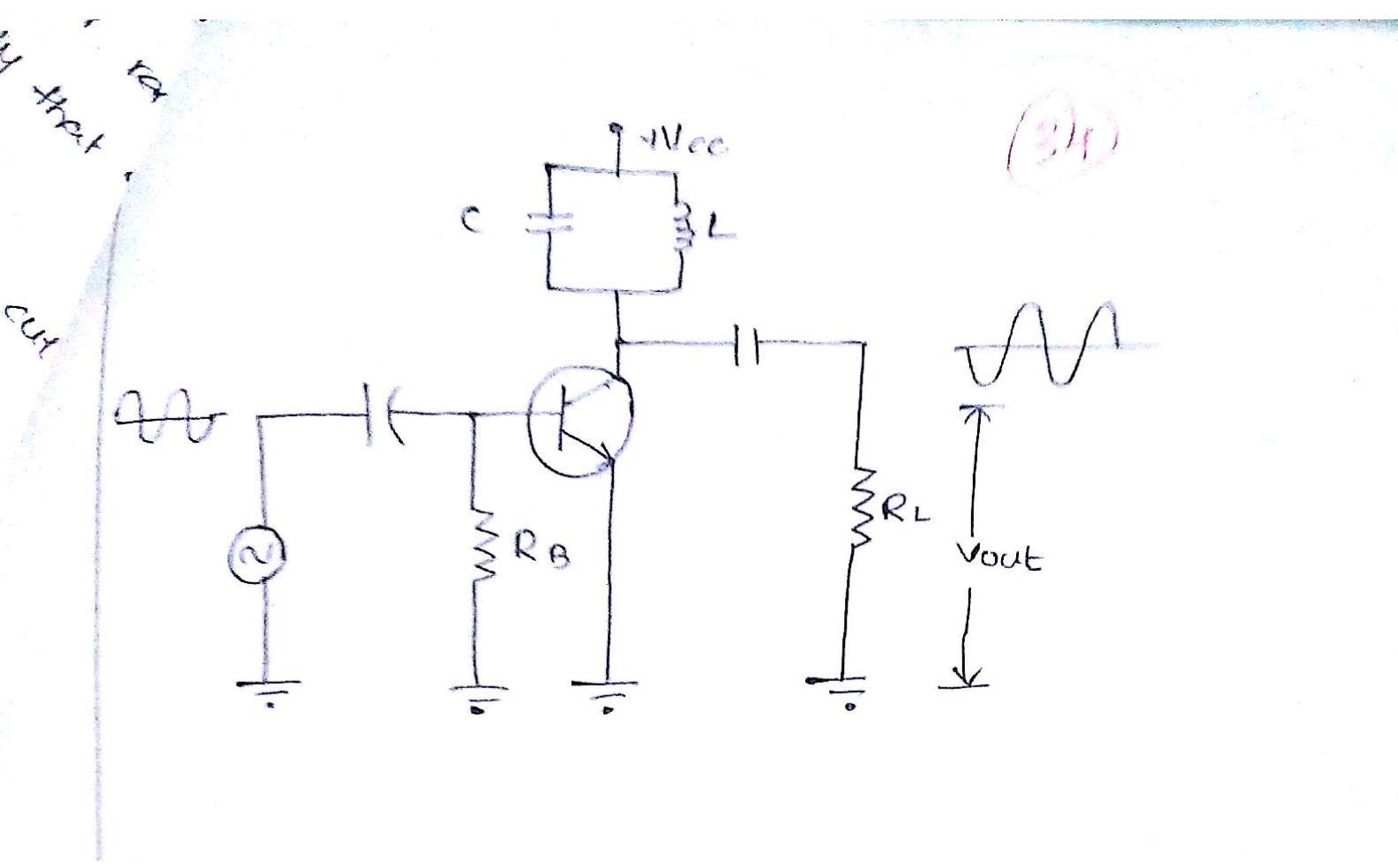→ A π el tuned circuit acting as a load impedance is tuned to i/p frequency. So it filters the harmonic frequencies and produces sinewave o/p with fundamental i/p signal component.




(13)

CLASS-A POWER AMPLIFIER:

In these power amplifiers if we plot a plot graph between I and v , as I on y axis and v on x axis we locate a point at the midpoint of active region

The output phase in the class A amplifier is 360°

we have.

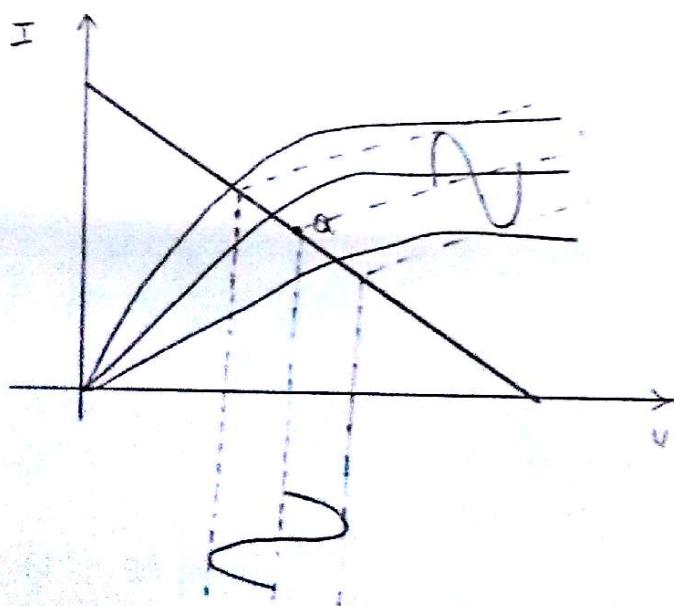



Q is at mid point on load line

CLASS A POWER AMPLIFIERS


The efficiency of class A power amplifier is 25-30%.

There will be no distortion in the output waveform of class A power amplifier.

Analysis of class A power Amplifier.

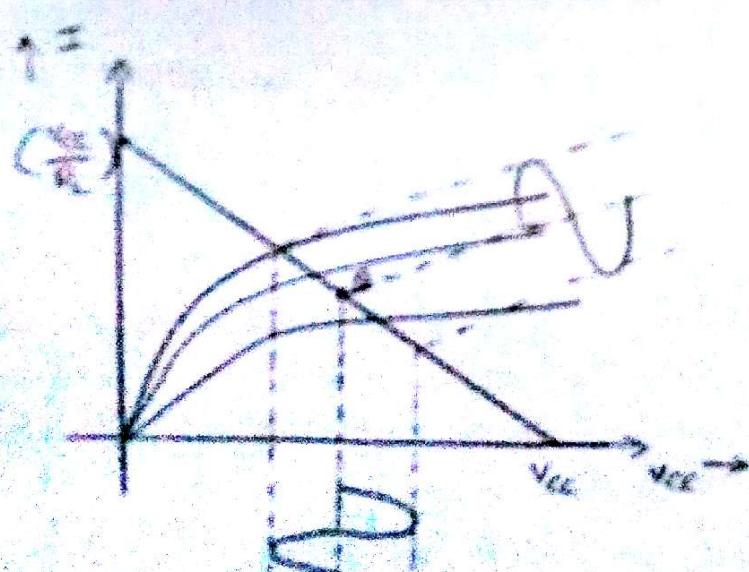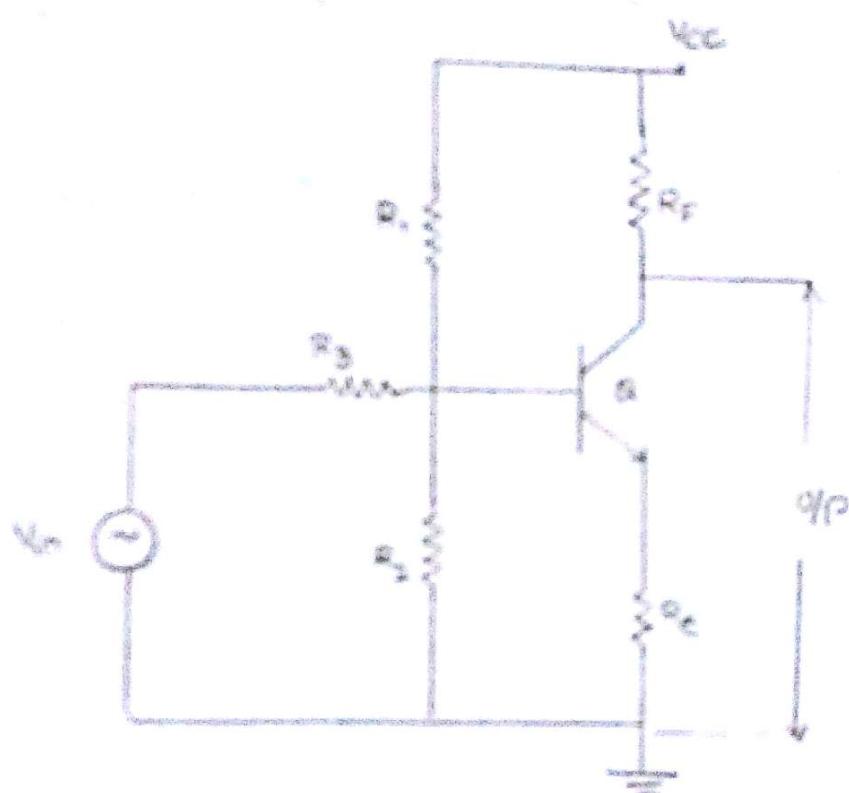

(45)

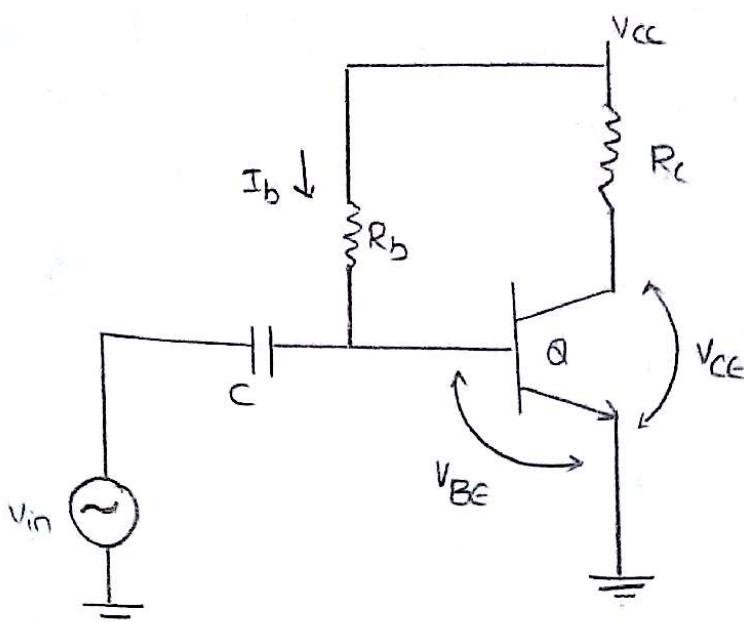

Dc Analysis:

Apply KVL, we have

$$V_{cc} = I_C R_L + V_{CE}$$

$$I_C R_L = V_{cc} - V_{CE}$$

$$I_C = \frac{V_{cc} - V_{CE}}{R_L}$$

$$I_C = \frac{V_{cc}}{R_L} - \frac{V_{CE}}{R_L}$$

$$I_C = \left(-\frac{1}{R_L}\right) \cdot V_{CE} + \frac{V_{cc}}{R_L}$$

we consider $y = mx + c$ the m is slope

Here slope is $\left(-\frac{1}{R_L}\right)$

(1x9)

DC operation:

$$I_{BQ} = \frac{V_{CE} - V_{BE}}{R_b}$$

$$I_{BQ} = \frac{V_{CE} - 0.7}{R_b}$$

$$I_{CQ} = \beta I_{BQ} \Rightarrow \beta = \frac{I_{CQ}}{I_{BQ}}$$

$$\beta = I_{CQ} \left(\frac{R_b}{V_{CE} - 0.7} \right)$$

$$I_{CQ} = \beta \left(\frac{V_{CE} - 0.7}{R_b} \right)$$

$$V_{CEQ} = V_{CC} + I_C R_C$$

Hence Q is defined at point Q(V_{CEQ}, I_{CQ})

DC power input:

when AC input signal is applied, the base current varies sinusoidally.

If current varies around its Quiescent point will the output voltage V_{CC} get varies. Varying current and output voltage delivers AC power to the load.