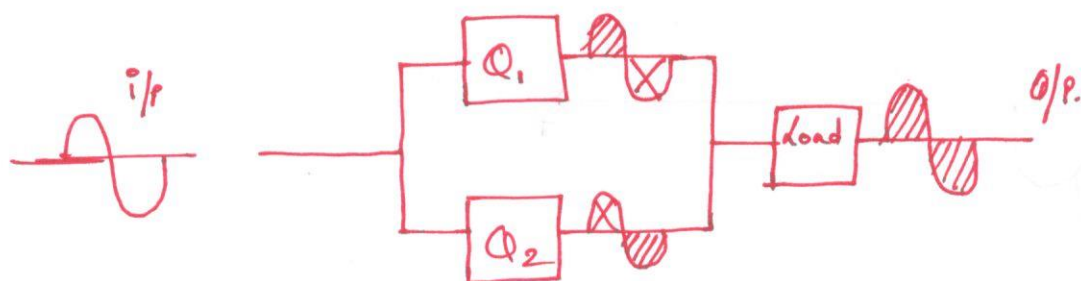


Block diagram:



dc operation:

Each transistor act as a half wave rectifier

If I_m is the peak current of the o/p then average value is $\frac{I_m}{\pi}$

$$\therefore I_{dc} = \frac{I_m}{\pi} + \frac{I_m}{\pi} = \frac{2I_m}{\pi}$$

The dc power is

$$\begin{aligned} P_{dc} &= V_{cc} \times I_{dc} \\ &= \frac{2}{\pi} V_{cc} \times I_m \end{aligned}$$

Ac operation:

When AC signal is applied to driver transformer to Q_1

& connecting Q_1 & Q_2 to the load

$$R'_L = R_L / n^2$$

where $n = N_2 / N_1$

The Slope of the graph will be $-1/R'_L$